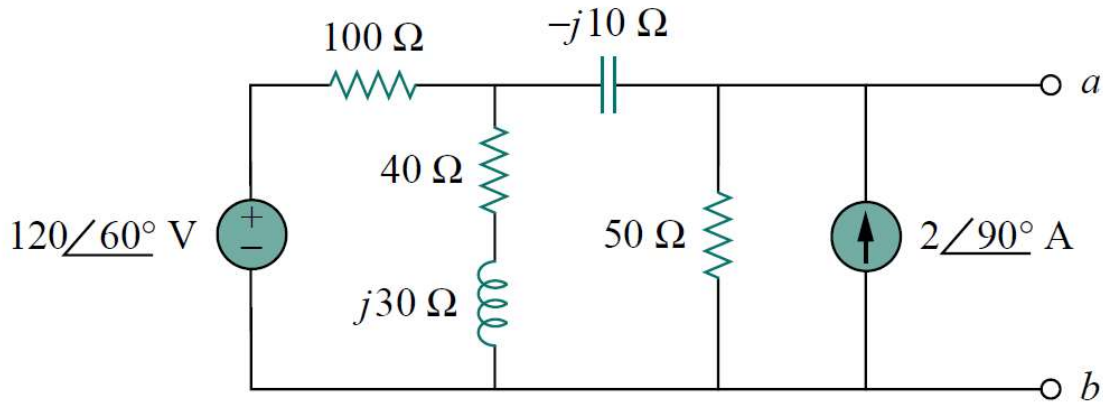


Assignment 2: Using MATLAB Simulink to find the voltage V_{ab} for the circuit shown in figure below, assume $\omega = 100\pi \text{ rad/sec}$.



Note the following;

- Prepare your file in **.slx** format and submit it before the due date.
- The maximum number of students per assignment is one.
- Name your **.slx** as **FirstName_MiddleName_LastName**.
- Sharing Matlab scripts among other groups is not allowed.