

Homework 02

Three stages of design need to be used for the following integrated current source circuit: schematic, PCB layout, and simulation.

