


Homework_3 next week: Design a PCB circuit for an 8/16 or 32-bit microcontroller containing more than four subcircuits. Some examples of these subcircuits are the oscillator, voltage regulator, and reset switch, as well as push-bottom switches (KEY) and a seven-segment display unit using a bus bar connection or LEDs for display signal.

Hierarchical Design (HD): Design a PCB circuit of Voltage regulator and oscillator using hierarchical design.


Hierarchical Design: Hierarchical design helps designers to organize large schematic designs into small functional blocks. It allows to abstract the complexity of the design and describe the design in simple blocks, also easier to read, explain the design circuit using block diagram.

Step 1: open new project / schematic (Hierarchical design) using new frame.

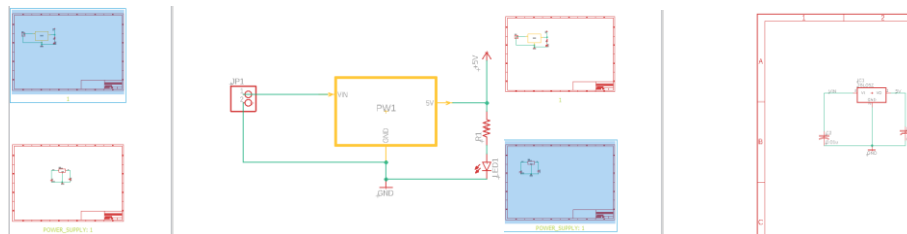This sheet contains the basic of HD of power supply mode as below.



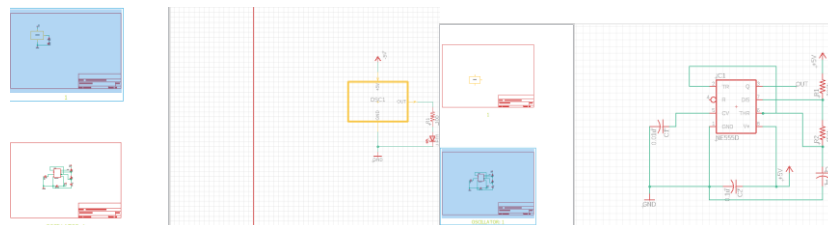Step 2: Repeat the same procedure to create oscillator model as below.



Step 3: Then create PCB design for both models.

