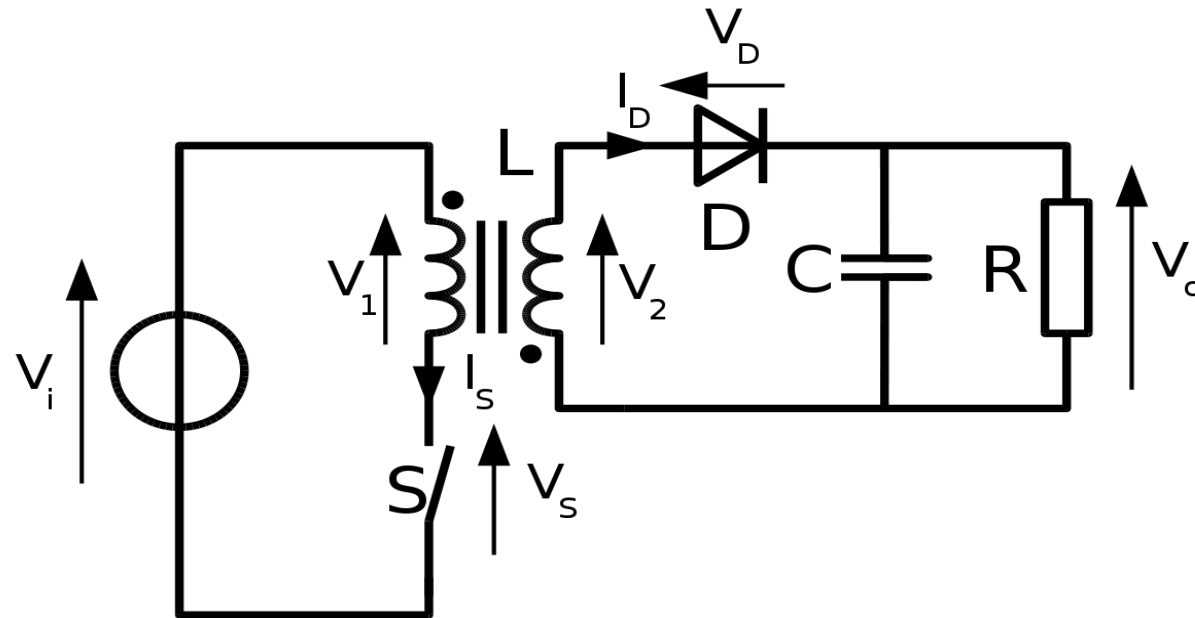


Flyback converter

Dc-Dc converter

What is a Flyback Converter?

The flyback converter is a power supply topology that uses mutually coupled inductor, to store energy when current passes through and releasing the energy when the power is removed. The flyback converters are similar to the booster converters in architecture and performance. However, the primary winding of the transformer replaces inductor while the secondary provides the output. In the flyback configuration, the primary and secondary windings are utilized as two separate inductors.




Applications of flyback converters

The flyback converter are used for a wide range of electronics applications such as:

- Television sets which consume small amount of power of up to about 250W
- Standby power supplies for computers
- Cell phone and mobile device chargers
- High-voltage supplies in TV and Monitor CRTs, Lasers, Xenon flashlights, copiers, etc.

Advantages of flyback converter

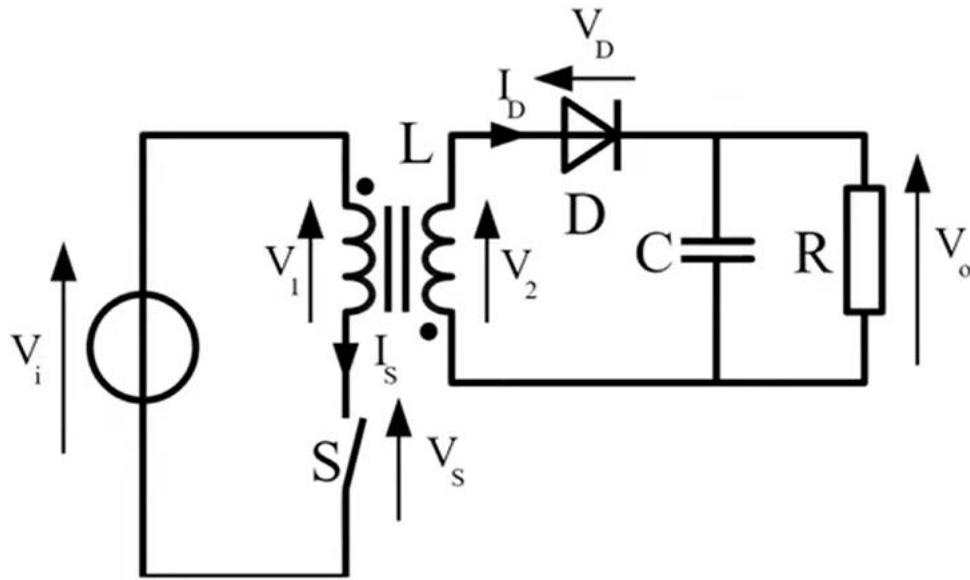- The primary is isolated from the output.
- Capable of supplying multiple output voltages, all isolated from the primary.
- Ability to regulate the multiple output voltages with a single control.
- Can operate on a wide range of input voltages
- The Flyback converters use very few components compared to the other types of SMPSs.



Parameters Provided

$V_o = 48\text{ V}$, $V_s = 24\text{ V}$, $P = 50\text{ W}$, $R = 50\text{ ohm}$, Switching Frequency = 250 kHz , $\Delta V_o = 0.3$

Duty Cycle


$$\frac{N_2}{N_1} = \frac{V_o}{V_s} * \frac{1 - D}{D}$$


The turns ratio is 4 so the duty will be 0.3

$$C = \frac{D * V_o}{R * f * \Delta V_o} :$$

Continuous

powergui

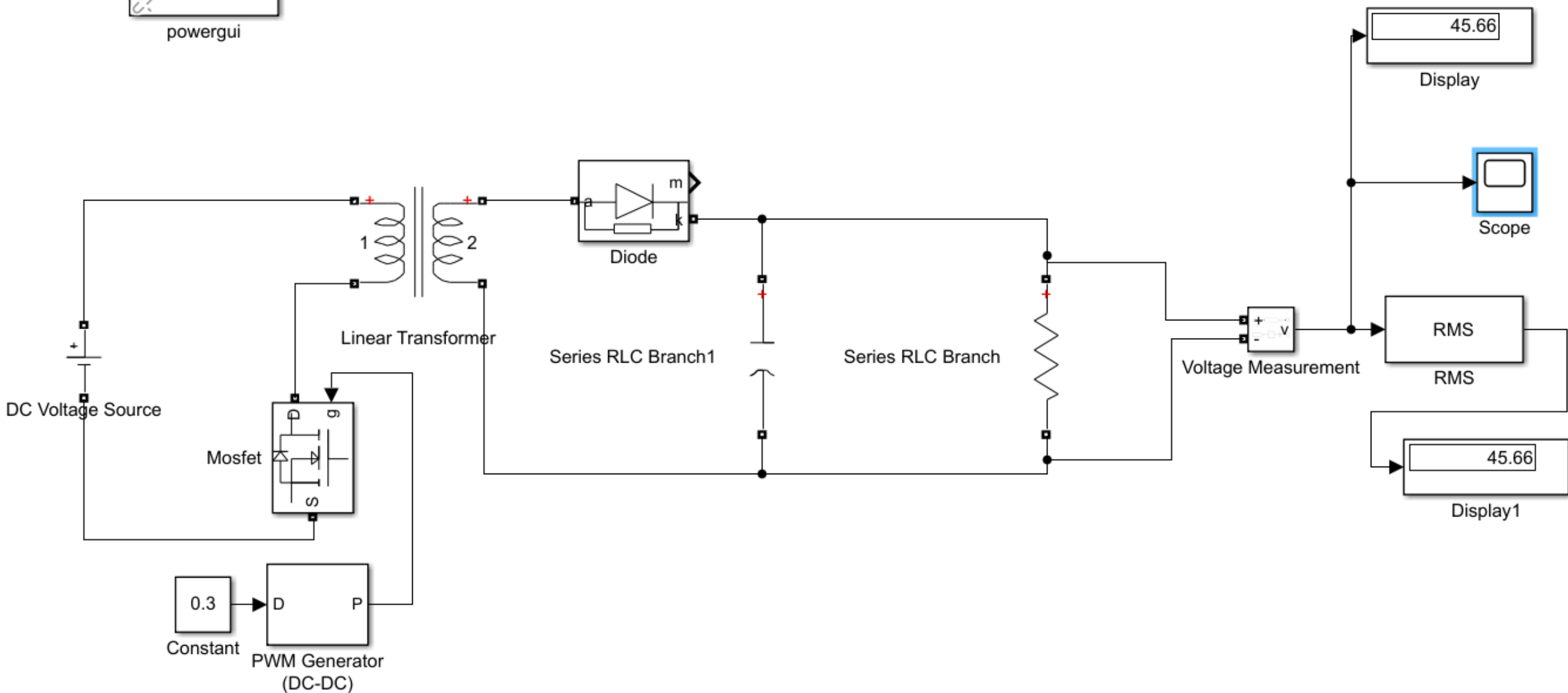

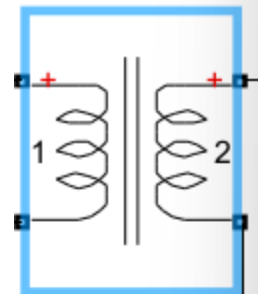

Linear Transformer

Block Parameters: Linear Transformer

Linear Transformer (mask) (link)

Implements a three windings linear transformer.

Click the Apply or the OK button after a change to the Units popup to confirm the conversion of parameters.

Parameters

Units SI

Nominal power and frequency [Pn(VA) fn(Hz)]:
[50 250e3]

Winding 1 parameters [V1(Vrms) R1(ohm) L1(H)]:
[24 0 0]

Winding 2 parameters [V2(Vrms) R2(ohm) L2(H)]:
[48 0 0]


☐ Three windings transformer

Winding 3 parameters [V3(Vrms) R3(ohm) L3(H)]:
[3.15e+05 0.7938 0.084225]

Magnetization resistance and inductance [Rm(ohm) Lm(H)]:
[1.0804e+06 2866]

Measurements None

OK Cancel Help Apply

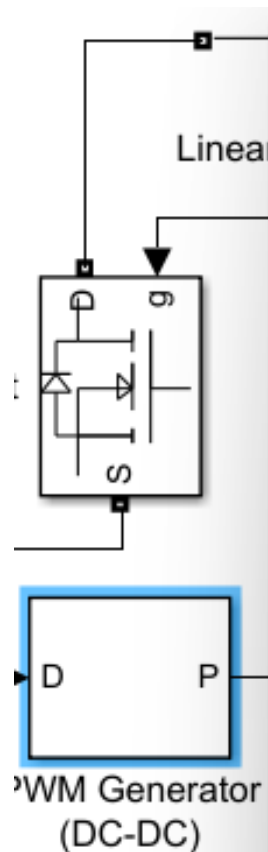

The diagram shows a Simulink model of a one-quadrant DC-DC converter. A 'PWM Generator (DC-DC)' block, which is a square block with inputs 'D' and 'P', is highlighted with a blue border. Its output 'P' is connected to the 'g' (gate) input of a power MOSFET switch block. The switch block also has a 'Linear' input, a 'D' (drain) input, an 'S' (source) input, and an 'S' (sense) output. The MOSFET symbol includes a diode in parallel with the switch. The 'PWM Generator (DC-DC)' block is labeled with 'D' and 'P' on its sides.

Block Parameters: PWM Generator (DC-DC)

PWM Generator (DC-DC) (mask) (link)

Output a pulse to the electronic switch of a one-quadrant DC to DC Converter.


The duty cycle (input D) determines the percentage of the pulse period that the output (P) is on.

Parameters

Switching frequency (Hz):
250e3

Sample time:
0

OK Cancel Help Apply

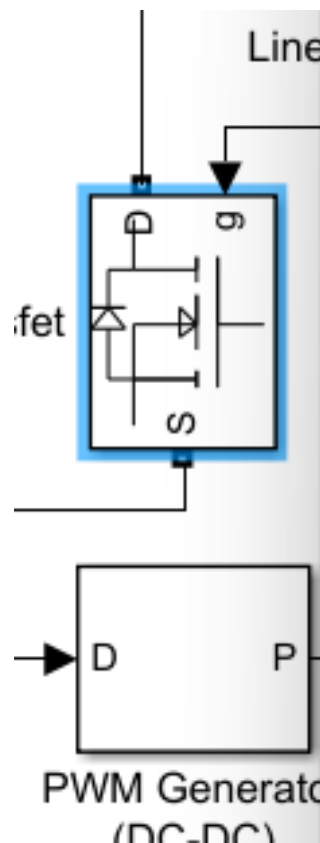

Internal diode forward voltage V_f	0
Initial current I_c (A) :	0
Snubber resistance R_s (Ohms) :	1e5
Snubber capacitance C_s (F) :	inf
☐ Show measurement port	