



Experiment Name	Timer 555
Student Name	
Grade (10%)	

Objectives

In this Lecture you will design multivibrator circuits that provide signals with particular waveforms.

→ Astable multivibrator

1. **Objective:** • Design an astable multivibrator to meet a set of specifications.
2. **Specifications:** : The circuit with the configuration shown in Figure below is to be designed to produce frequency of oscillation is **$f_o = 600$ Hz and duty cycle is 66 percent ,Then connected your design circuit to load (LED connected in a series with a resistance of $470\ \Omega$).**
3. **Design Approach:** The astable multivibrator configuration to be designed is shown in Figure 1.
4. **Choices:** Timer 555 are assumed to be available, choose $+V_{CC} = 9$ v.

5. **Solution (Analysis):** Considering the circuit in Figure 1, we have

let $c = 0.1\ \mu\text{f}$

- frequency of oscillation is

$$f = \frac{1}{T} = \frac{1}{T_C + T_D} = \frac{1}{0.693(R_A + 2R_B)C}$$

- duty cycle is $\frac{R_A + R_B}{R_A + 2R_B} \times 100\%$

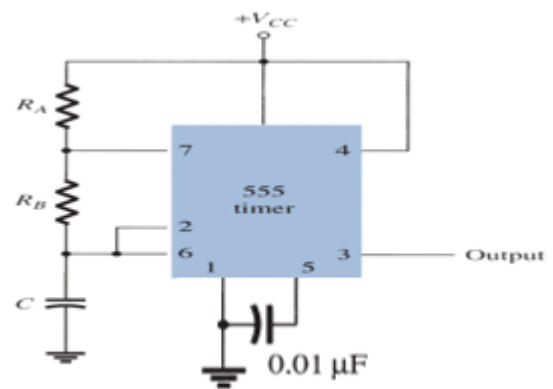
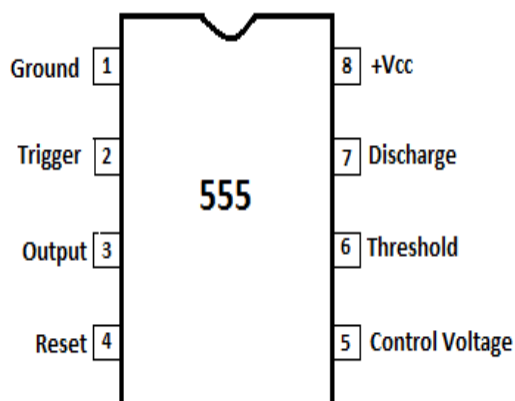


Figure 1: astable multivibrator for the design application

Write your comments.

What happens to the frequency of the waveform if V_{CC} is increased?

→ **monostable multivibrator**

1. **Objective:** • Design an astable multivibrator to meet a set of specifications.
2. **Specifications:** The circuit with the configuration shown in Figure below is to be designed to produce an output pulse width approximately 1m., **Then connected your design circuit to load (LED connected in a series with a resistance of $470\ \Omega$)**
3. **Design Approach:** The monostable multivibrator configuration to be designed is shown in Figure 1.
4. **Choices:** Timer 555 are assumed to be available, choose $+V_{CC} = 9V$.

5. **Solution (Analysis):** Considering the circuit in Figure 1, we have

- The width of the output pulse $T = RC \ln(3) = 1.1 RC$
If we set threshold voltage $v(t) = \left(\frac{2}{3}\right)V^+$

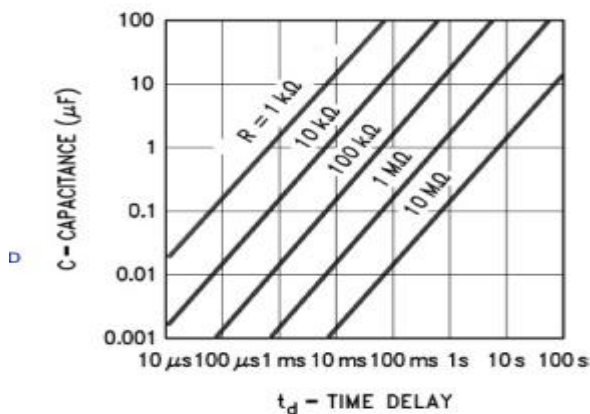


Chart 1

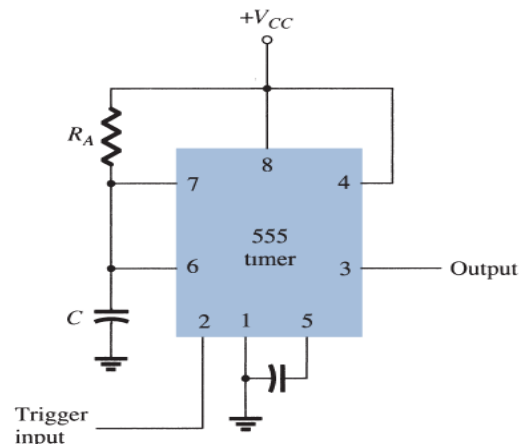


Figure 1: astable multivibrator for the design application

- Use the chart 1 to determine values for R and C to get a pulse that is 1m seconds.
- Use button create a negative pulse to trigger the circuit. When the button is on, the timer will start to charge the capacitor and output goes to high. Once the capacitor reaches a threshold level ($\frac{2}{3}$ of V_{CC}), the timer discharges the capacitor and output goes to low

