




Lect 02

Introduce active high pass filters


Instructor /Noor .H .Jabber



Introduce active high pass filter

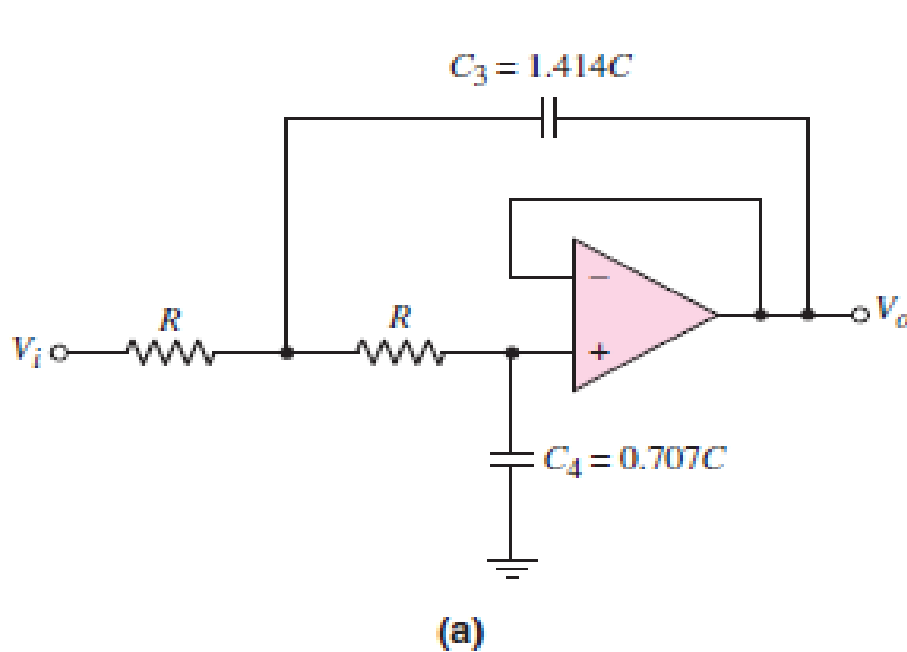

two-pole low-pass Butterworth filter

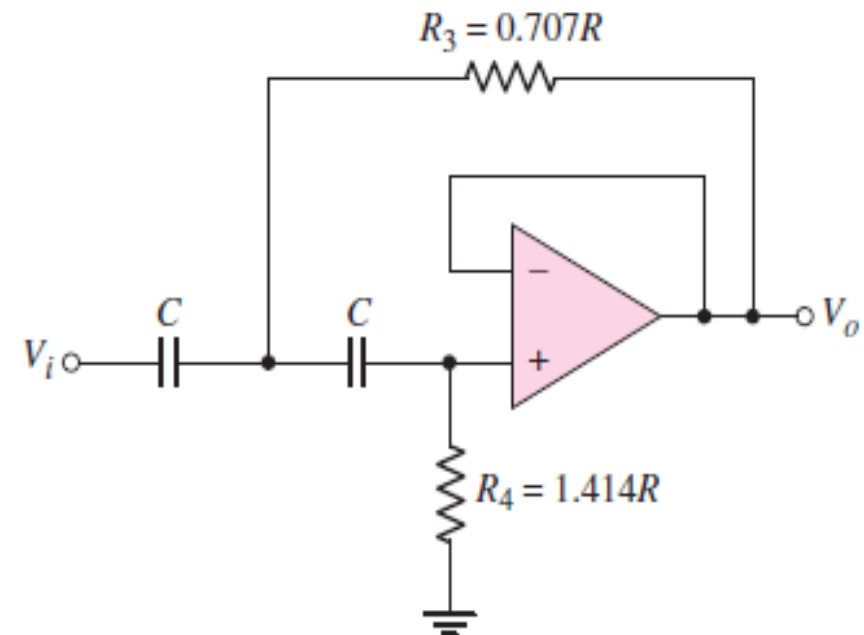

Introduce active high pass filter


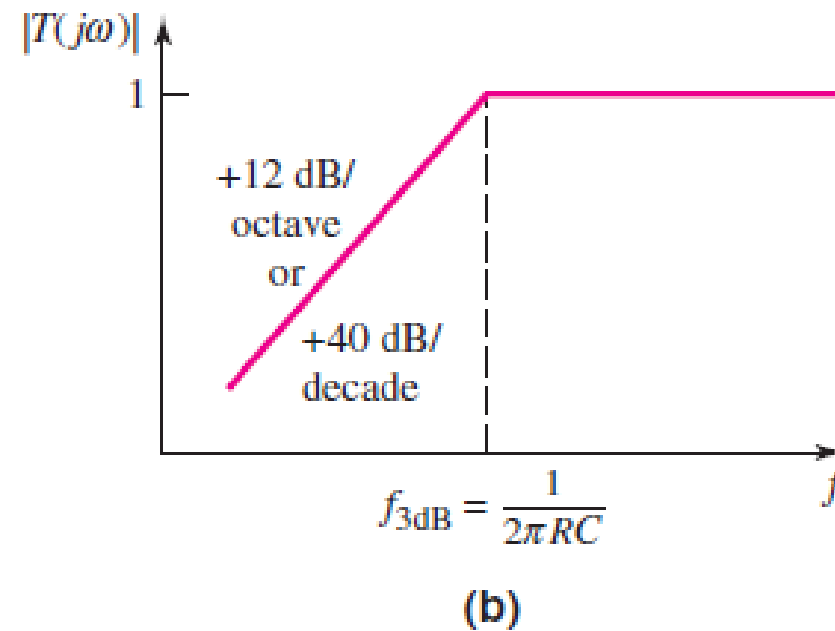


Figure 15.8 (a) Two-pole high-pass Butterworth filter and (b) Bode plot, transfer function magnitude

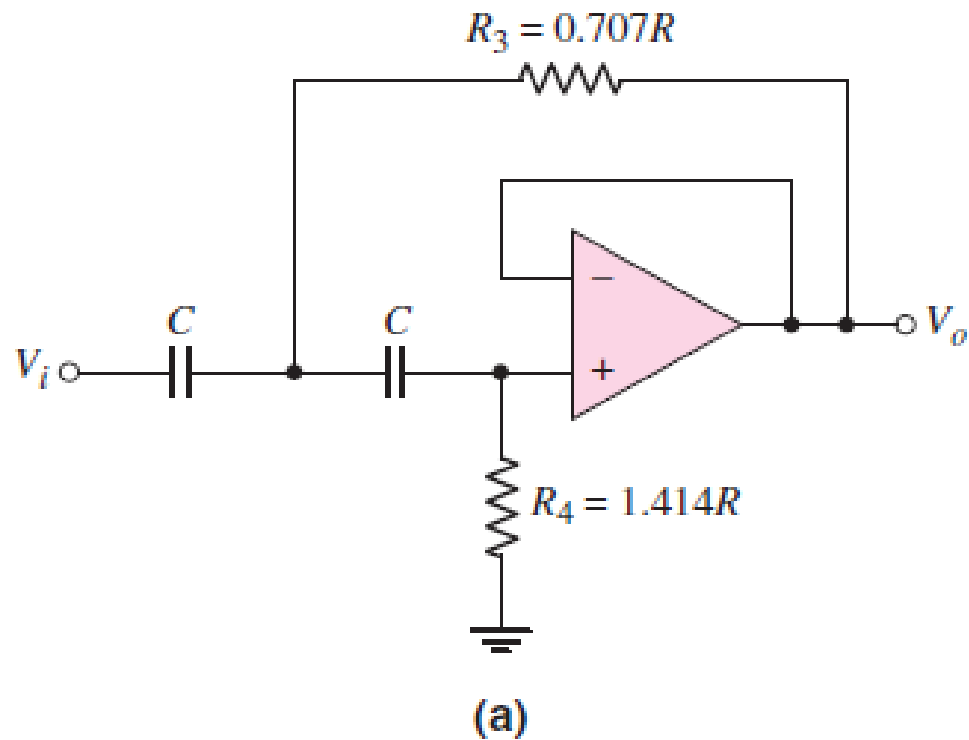


Introduce active high pass filter


For a Butterworth N th-order high-pass filter, the voltage transfer function magnitude is

$$|T| = \frac{1}{\sqrt{1 + \left(\frac{f_{3\text{ dB}}}{f}\right)^{2N}}}$$

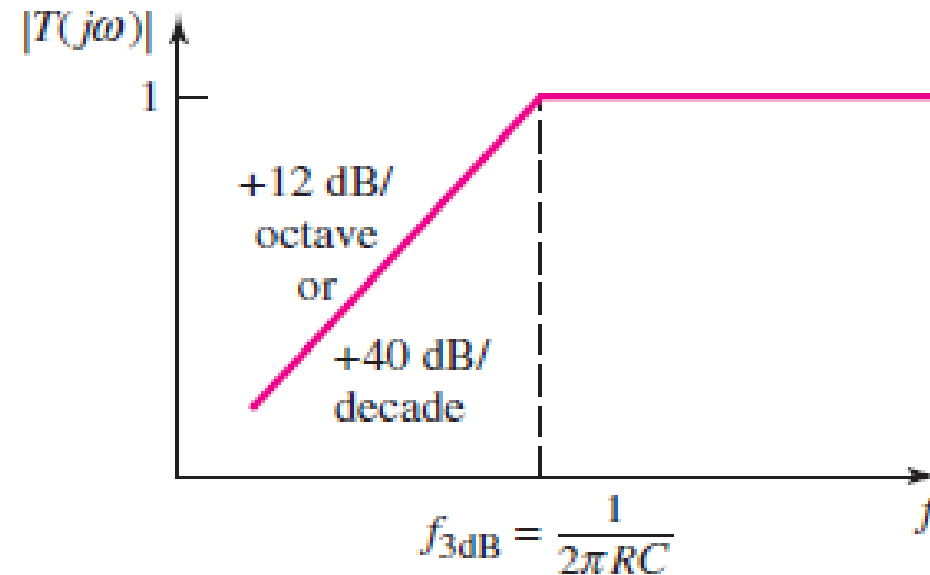
$$\omega_{3\text{ dB}} = 2\pi f_{3\text{ dB}} = \frac{1}{RC}$$



QUIZ

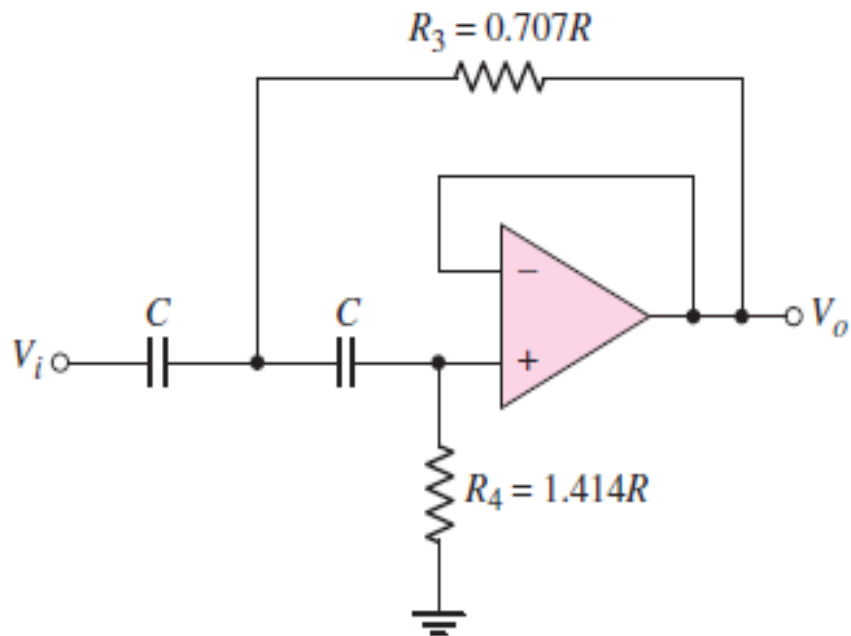

two-order high Butterworth filter

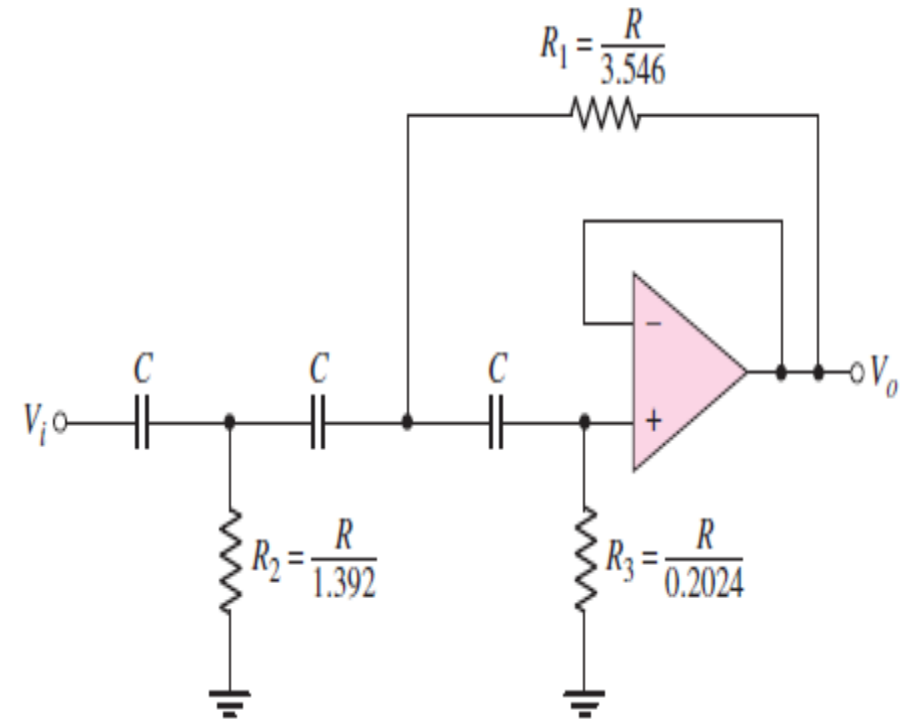


three-order high Butterworth filter



Analog Electronics Lab



H.W 1

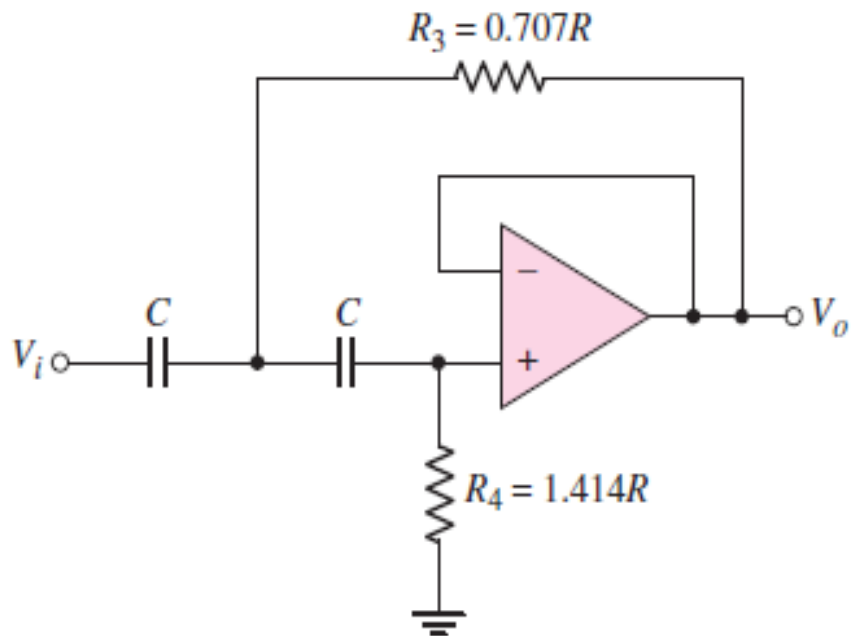

two-order high Butterworth filter




five-order high Butterworth filter

six-order high Butterworth filter

H.W 2

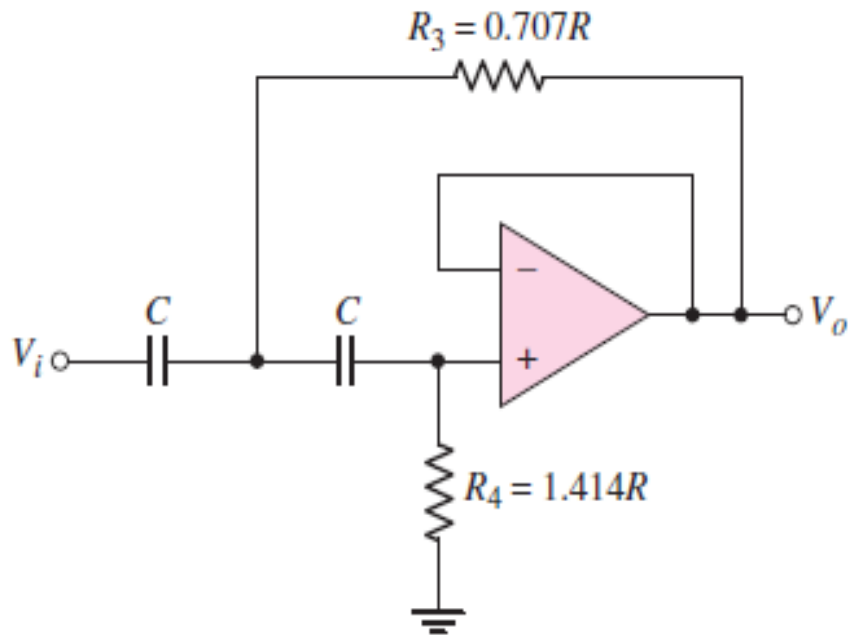Why is six order filter better than second order? enhance your answer with bode plot of transfer function for each order



five-order high Butterworth filter

six-order high Butterworth filter



Analog Electronics Lab



Assignments

Objective: Design a three-pole high-pass Butterworth active filter with a cutoff frequency at $f_{3dB} = 30$ kHz and a unity gain magnitude at high frequency.


Specifications: The circuit with the configuration shown in Figure below is to be designed such that the bandwidth is 30 kHz.


Choices: An ideal op-amp is available and standard-valued resistors and capacitors must be used.

Bode plot : Determine the magnitude of the gain at (i) $f = 25$ kHz, (ii) $f = 30$ kHz, and (iii) $f = 40$ kHz.

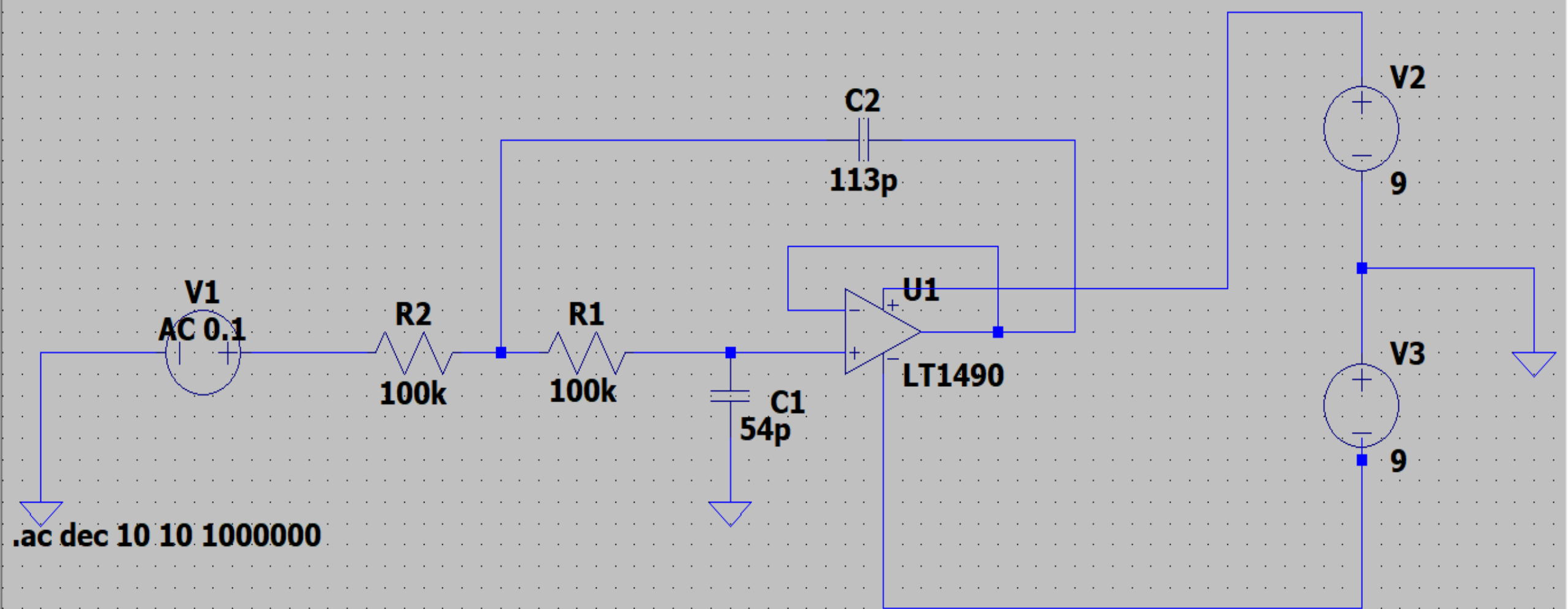computer simulation LTSPICE : Using a computer simulation, plot the magnitude of the voltage transfer function versus frequency and compare these results with your plot





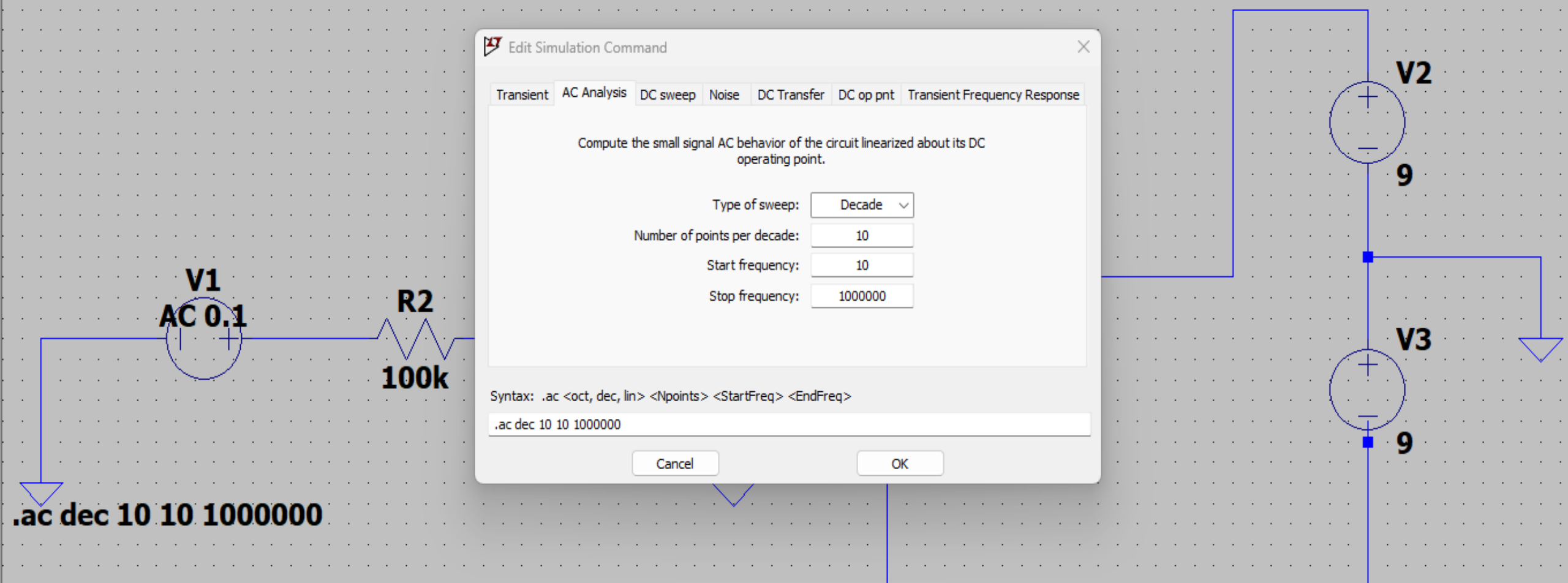

LTspice Edit Simulation Command

Transient AC Analysis DC sweep Noise DC Transfer DC op pnt Transient Frequency Response

Compute the small signal AC behavior of the circuit linearized about its DC operating point.

Type of sweep: Decade

Number of points per decade: 10


Start frequency: 10


Stop frequency: 1000000

Syntax: .ac <oct, dec, lin> <Npoints> <StartFreq> <EndFreq>

.ac dec 10 10 1000000

Cancel OK

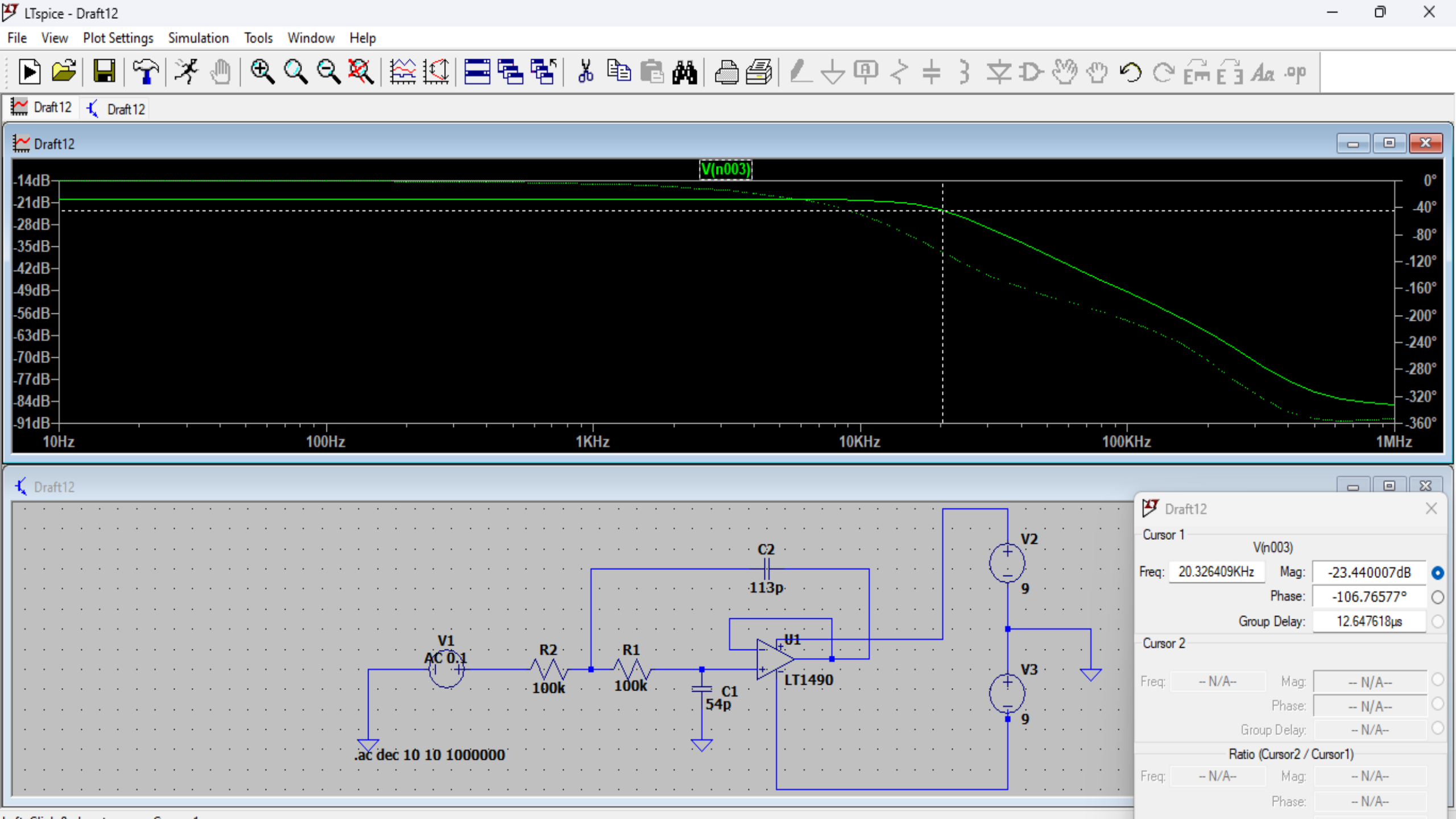

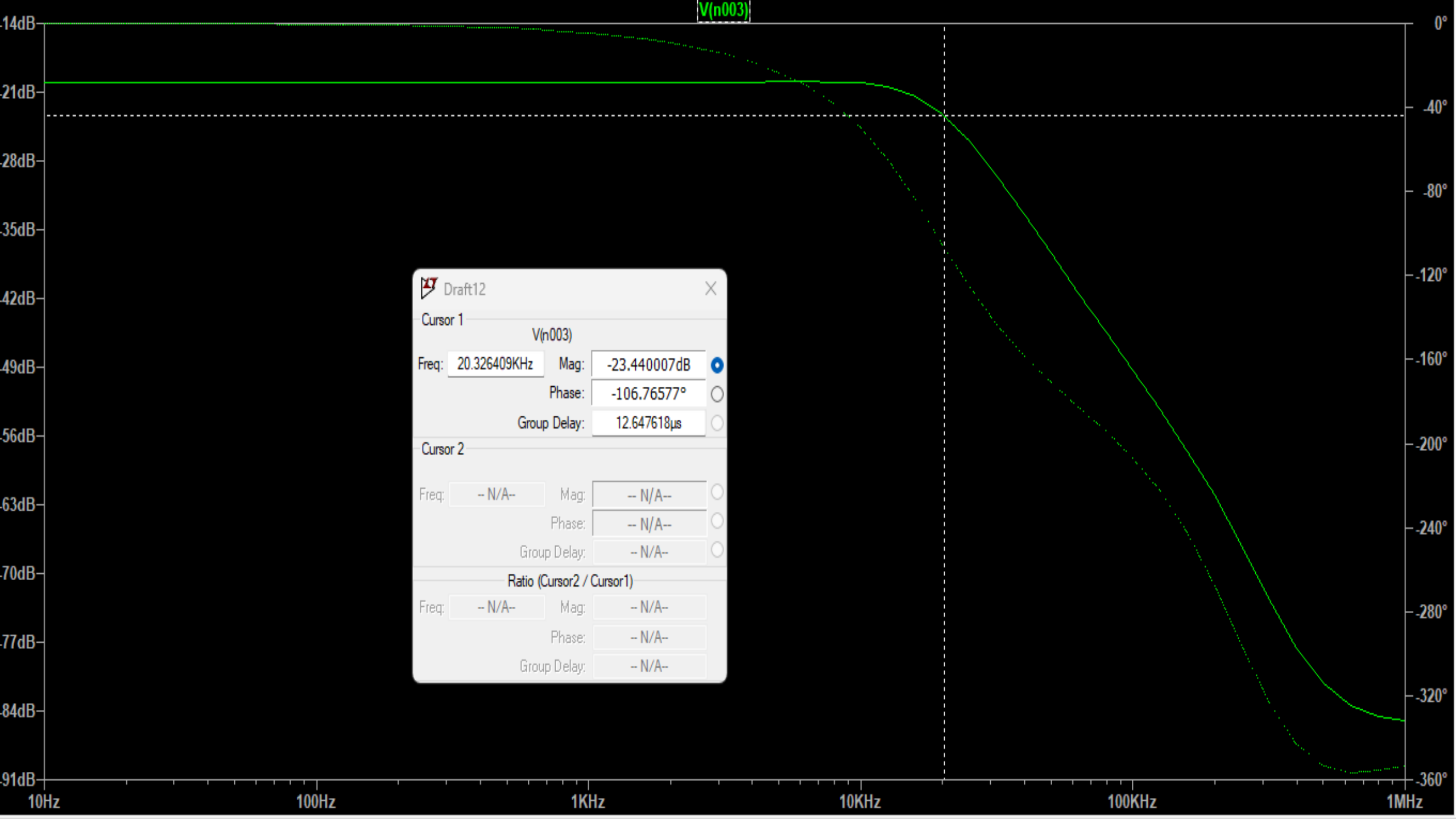

Draft12

Cursor 1

V(n003)

Freq: 20.326409KHzMag: -23.440007dB

Phase: -106.76577°

Group Delay: 12.647618μs

Cursor 2

Freq: -- N/A --Mag: -- N/A --

Phase: -- N/A --

Group Delay: -- N/A --

Ratio (Cursor2 / Cursor1)

Freq: -- N/A --Mag: -- N/A --

Phase: -- N/A --

Group Delay: -- N/A --