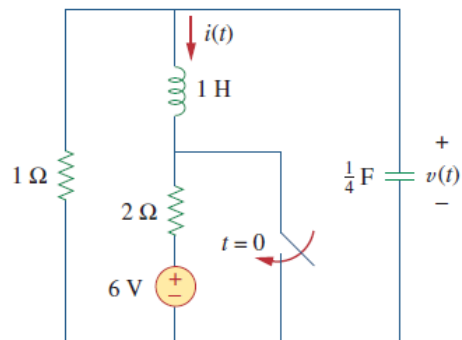


Answer all questions with detail steps.


Q1/

Given the circuit in , find $i(t)$ and $v(t)$ for $t > 0$.



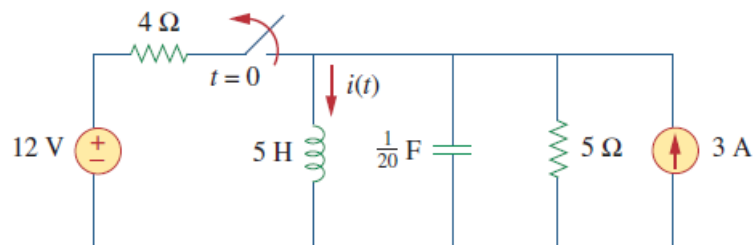
Q2/

Determine $i(t)$ for $t > 0$ in the circuit



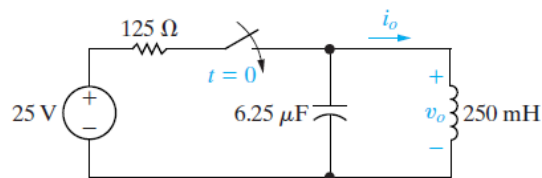Q3/

There is no energy stored in the circuit when the switch is closed at $t = 0$. Find $i_o(t)$ for $t \geq 0$.



Q4/

Design a series RLC circuit using component values from tables below, with a resonant radian frequency of 20,000 rad/s .

- 1- Choose a resistor or create a resistor network so that the response is critically damped. Draw your circuit. Calculate the roots of the characteristic equation.
- 2- Choose a resistor or create a resistor network so that the response is underdamped. Draw your circuit. Calculate the roots of the characteristic equation.
- 3- Choose a resistor or create a resistor network so that the response is overdamped. Draw your circuit. Calculate the roots of the characteristic equation.

Resistors (5% tolerance)[Ω]						Capacitors		
10	100	1.0 k	10k	100k	1.0 M	10 pF	22 pF	47 pF
	120	1.2 k	12 k	120 k		100 pF	220 pF	470 pF
15	150	1.5 k	15 k	150 k	1.5 M	0.001 μ F	0.0022 μ F	0.0047 μ F
	180	1.8 k	18 k	180 k		0.01 μ F	0.022 μ F	0.047 μ F
22	220	2.2 k	22 k	220 k	2.2 M	0.1 μ F	0.22 μ F	0.47 μ F
	270	2.7 k	27 k	270 k		1 μ F	2.2 μ F	4.7 μ F
33	330	3.3 k	33 k	330 k	3.3 M	10 μ F	22 μ F	47 μ F
	390	3.9 k	39 k	390 k		100 μ F	220 μ F	470 μ F
47	470	4.7 k	47 k	470 k	4.7 M			
	560	5.6 k	56 k	560 k				
68	680	6.8 k	68 k	680 k	6.8 M			