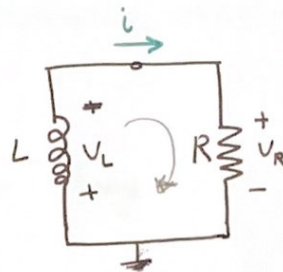


The Source-Free RL Circuits.

At $t=0$, assume the inductor has an initial current I_0 ;



Apply KVL

$$V_L + V_R = 0 \Rightarrow L \frac{di}{dt} + Ri = 0$$

$$\frac{di}{dt} = -\frac{R}{L}i \quad (\text{arranging variables for solving the differential equation using separation method})$$


$$\int_{I_0}^{i_t} \frac{di}{i} = \int_0^t -\frac{R}{L} dt \quad [\text{Integrate both side, } I_0 \rightarrow i_t, 0 \rightarrow t]$$

$$\ln i_t - \ln I_0 = -\frac{R}{L}t \Rightarrow \ln \frac{i}{I_0} = -\frac{R}{L}t \quad [\text{Power of } e]$$

$$\frac{i}{I_0} = e^{-\frac{R}{L}t} \Rightarrow \boxed{i = I_0 e^{-\frac{t}{L/R}} \quad \tau = \frac{L}{R}}$$

The natural Response of the RL circuit is an exponential decay of the initial current.

For the Resistor, to find V_R, P, W_R

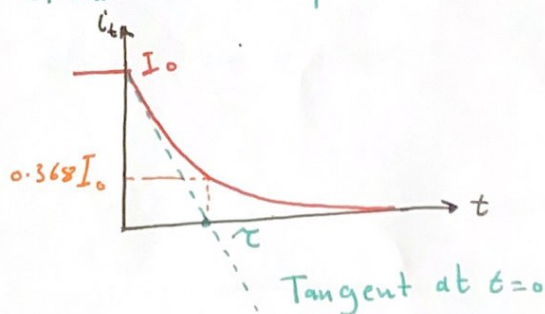

$$V_R = iR = I_0 R e^{-t/\tau}$$


$$P = V_R i = I_0^2 R e^{-2t/\tau}$$

$$W_R = \int_0^t P_R d\tau = \frac{1}{2} L I_0^2 (1 - e^{-2t/\tau})$$

As $t \rightarrow \infty$, $W_R(\infty) = \frac{1}{2} L I_0^2 = W_L(0)$, the energy initially stored in the inductor is eventually dissipated in the resistor.

Ex: The switch has been closed for a long time and is opened at $t=0$. Find

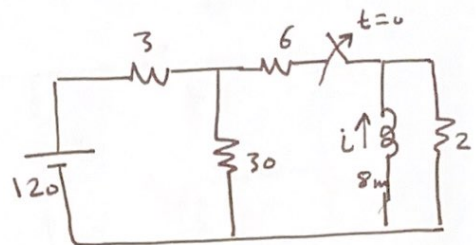- I_0
- $W_L(0)$
- $i(t)$
- Inductor energy dissipated in 2Ω after 5ms. percentage to the initial.




For $t < 0$, the inductor act as short circuit

1- Find I_{Total}

$$R_{6||30} = \frac{30 \cdot 6}{30 + 6} = 5 \Omega$$

$$I_T = \frac{120}{8} = 15 \text{ A}$$

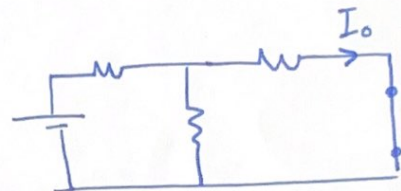

$$I_6 = I_L = \frac{30 \cdot 15}{30 + 6} = 12.5 \text{ A} \quad \text{or} \quad I_0 = -12.5 \text{ A (opposite direction)}$$

$$b) \quad W_L(0) = \frac{1}{2} L I_0^2 = \frac{1}{2} \cdot 8 \cdot 10^{-3} \cdot (-12.5)^2 = 0.625 \text{ J}$$

$$c) \quad i(t) = I_0 e^{-t/\tau} \quad , \quad \tau = \frac{L}{R} = \frac{8 \cdot 10^{-3}}{2} = 0.004 \quad , \quad \frac{1}{\tau} = 250$$

$$i(t) = -12.5 e^{-250t}$$

$$d) \quad i_5 = -12.5 e^{-250(0.005)} = -3.58 \text{ A}$$

$$W_5 = \frac{1}{2} L (-3.58)^2 = 51.3 \text{ mJ}$$


$$W_{dis} = 625 - 51.3 = 573$$

$$\% = \frac{573}{625} \cdot 100 = 91.8 \%$$

Ex: Find $i_L(t)$ for $t \geq 0$

1- Find the initial current for the inductor


$i_{12} = i_{0L}$, R_5 is short.

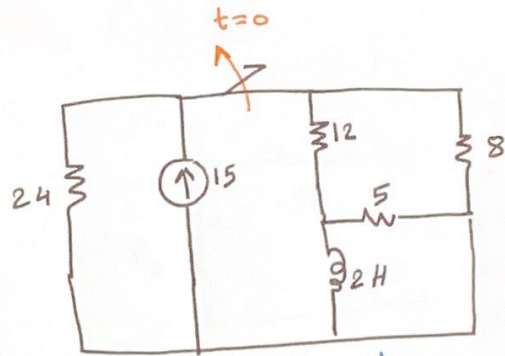

$$R_{24||8} = \frac{24 \cdot 8}{32} = 6$$

$$I_{12} = \frac{15 \cdot 6}{12 + 6} =$$
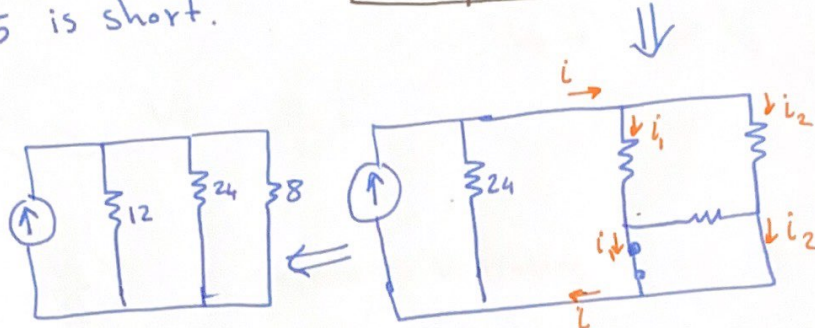
$$= \frac{15 \cdot 6}{18} = 5 \text{ A initial current}$$



2 For $t \geq 0$ $R_T = R_{5|| (12+8)} = \frac{5 \cdot 20}{25} = 4 \Omega$


$$\tau = \frac{L}{R} = \frac{2}{4} = \frac{1}{2}$$

$$i_L(t) = 5 e^{-t/0.5} = 5 e^{-2t} \text{ A}$$

The Step Response of an RL Circuit

Applying KVL

$$V_s = Ri + L \frac{di}{dt}$$

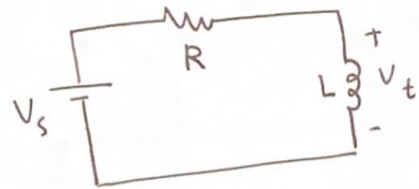

$$V_R + V_L = V_s$$

$$\frac{di}{dt} = \frac{V_s - Ri}{L} = \frac{V_s}{L} - \frac{R}{L} i$$

$$\frac{di}{dt} = -\frac{R}{L} \left(i - \frac{V_s}{R} \right) \quad \text{Separate Variables}$$


$$\int_{I_0}^i \frac{di}{\left(i - \frac{V_s}{R} \right)} = \int_0^t -\frac{R}{L} dt \quad \text{Integrate both side } I_0 \rightarrow i, 0 \rightarrow t$$

$$\ln \left(i - \frac{V_s}{R} \right) \Big|_{I_0}^i = -\frac{R}{L} t \Big|_0^t \Rightarrow \ln \left(i - \frac{V_s}{R} \right) - \ln \left(I_0 - \frac{V_s}{R} \right) = -\frac{R}{L} t$$

$$\ln \frac{\left(i - \frac{V_s}{R} \right)}{\left(I_0 - \frac{V_s}{R} \right)} = -\frac{R}{L} t \Rightarrow \frac{i - \frac{V_s}{R}}{I_0 - \frac{V_s}{R}} = e^{-R/L t}$$

$$i = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-(R/L)t}$$

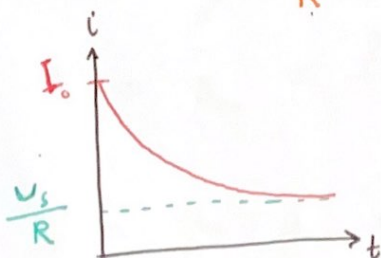
$$\frac{V_s}{R} = i_{s.s}, \quad \left(I_0 - \frac{V_s}{R} \right) e^{-(R/L)t} = \text{transient current}$$



$$i = i_{(\infty)} + (I_0 - i_{(\infty)}) e^{-t/\tau} \quad \tau = \frac{L}{R}$$

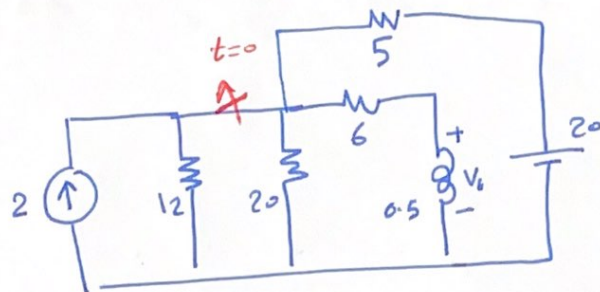7.56 Find $V(t)$ for $t > 0$

For $t < 0$ the switch is closed, and the inductor act as short circuit.



1- Find i through $R_6 = i_L$

Using KVL

$$\frac{V}{12} + \frac{V}{20} + \frac{V}{6} - \frac{V-20}{5} = 2$$


$$V \left(\frac{1}{12} + \frac{1}{20} + \frac{1}{6} + \frac{1}{5} \right) = +2 + \frac{20}{5}$$

$$V (0.0834 + 0.05 + 0.166 + 0.2) = \frac{10+20}{5}$$

$$0.5 V = 6 \Rightarrow V = 12 V$$

$$I_0 = \frac{V}{R_6} = \frac{12}{6} = 2 A$$

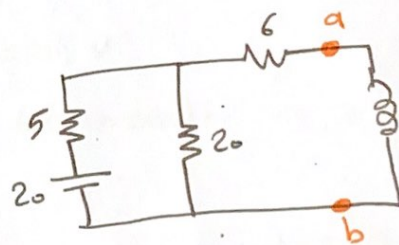2- After opening the switch
Find R_{Th} , V_{Th} across a, b




$$R_{Th} = (5 \parallel 20) + 6$$

$$\frac{5 \cdot 20}{5+20} + 6 = 10 \Omega$$

$$V_{Th} = V_{R_{20}} = \frac{20 \cdot 20}{25} = 16 V \quad (V. \text{ divider})$$
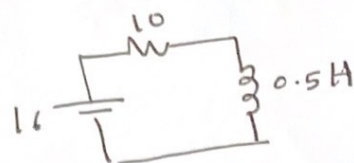
$$i = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau}$$



$$\tau = \frac{L}{R} = \frac{0.5}{10} = \frac{1}{20} = 0.05$$

$$\frac{V_s}{R} = \frac{16}{10} = 1.6 \text{ A}$$



$$i = 1.6 + (2 - 1.6)e^{-t/0.05}$$

$$i = 1.6 + 0.4e^{-20t}$$

$$V_t = L \frac{di}{dt} = 0.5 \left[0.4e^{-20t} \cdot -20 \right] = -4e^{-20t}$$

Ex: Find $i_o(t)$ and $V_o(t)$ at $t \geq 0$

At $t < 0$

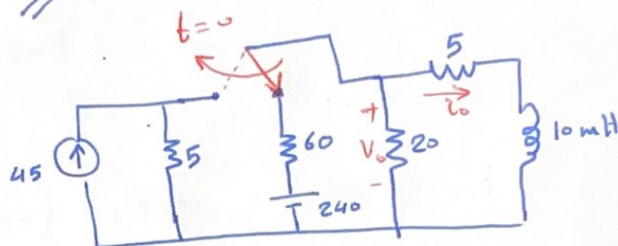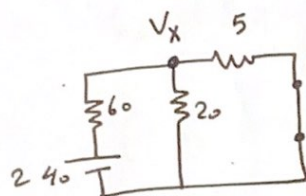

$$\frac{V_x - 240}{60} + \frac{V_x}{20} + \frac{V_x}{5} = 0 \Rightarrow \frac{V_x - 240 + 3V_x + 12V_x}{60} = 0$$

$$16V_x = 240 \quad \text{and} \quad V_x = \frac{240}{16} = 15 \text{ V}$$

$$i_o = \frac{V_x}{5} = \frac{15}{5} = 3 \text{ A} \quad \text{initial current on the inductor at } t \geq 0$$



at $t > 0$

1- Find R_{Th} on L

$$R_T = (5 \parallel 20) + 5 = \frac{5 \cdot 20}{25} + 5 = 9 \Omega$$

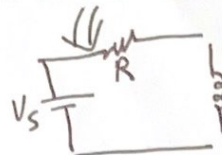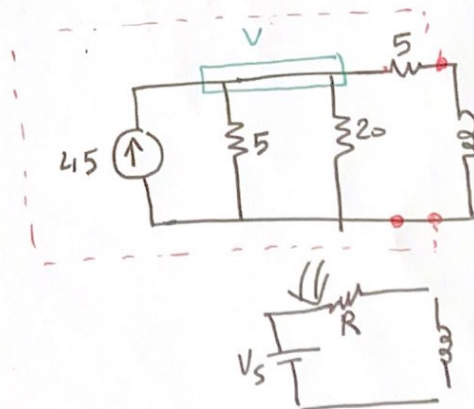
2. V is the voltage across L

$$\frac{V}{5} + \frac{V}{20} = 45 \Rightarrow \frac{4V + V}{20} = 45$$



$$\frac{15V}{\frac{20}{4}} = 45 \quad \text{and} \quad V = 180V$$
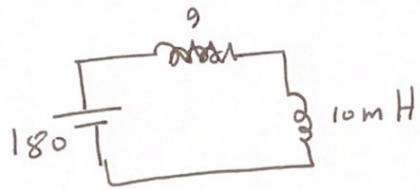
$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R}\right) e^{-t/\tau}$$



RL series circuit

$$\tau = \frac{L}{R} = \frac{10m}{9} = 1.112ms.$$

$$\frac{1}{\tau} = 900$$

$$i(t) = \frac{2}{9} + \left(3 - \frac{180}{9}\right) e^{-900t} \text{ A}$$

$$i_t = 20 - 17e^{-900t} \text{ A}$$

V_o = Voltage of $(5\Omega + \text{inductor})$ as they parallel

$$= 5i_o + L \frac{di}{dt}$$

$$= 5(20 - 17e^{-900t}) + 10 \times 10^{-3} (-17e^{-900t} \cdot -900)$$

$$= 100 - 85e^{-900t} + 153e^{-900t}$$

$$V_o = 100 + 68e^{-900t} \text{ V}$$