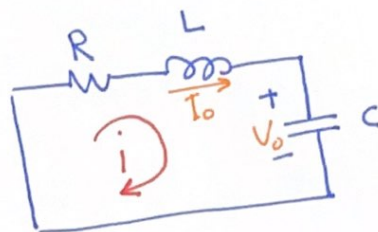


The Source-Free Series RLC

I_0, V_0 are the initial inductor current and the initial capacitor voltage that excite the circuit.



At time $t = 0$

$$i|_{t=0} = I_0, \quad V|_{t=0} = \frac{1}{C} \int_{-\infty}^{t=0} i dx = V_0$$

Apply KVL $V_R + V_L + V_C = 0$

$$V_R = iR$$

$$V_L = L \frac{di}{dt}$$

$$V_C = \frac{1}{C} \int i dt$$

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0 \quad \text{Differentiate}$$

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i = 0 \quad \text{Re arrange}$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0 \quad \text{Second-order D.E. (Linear, homogenous)}$$

Assume the solution is of form $i = e^{st}$ As an experience from the First-order.
to get the benefit of its derivatives

$$s^2 e^{st} + \frac{R}{L} s e^{st} + \frac{1}{LC} e^{st} = 0$$

$$e^{st} \left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right) = 0$$

quadratic equation.

$$\frac{di}{dt} = s e^{st}$$

$$\frac{d^2 i}{dt^2} = s^2 e^{st}$$

multiplier of the function

Only the quadratic equation can make the left hand side equal to zero for all t .

Using quadratic formula $ax^2 + bx + c = 0$

$$x_1, x_2 = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$s_1, s_2 = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2} = \frac{-R}{2L} \pm \frac{\sqrt{\left(\frac{2R}{2L}\right)^2 - \frac{4}{LC}}}{2}$$

$$s_1, s_2 = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{\sqrt{LC}}\right)^2}$$

$$\text{Let } \begin{cases} \alpha = \frac{R}{2L} \\ \omega_0 = \frac{1}{\sqrt{LC}} \end{cases}$$

$$\begin{aligned} s_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ s_2 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} \end{aligned} \quad (\text{general roots})$$

s_1, s_2 : natural frequencies / nepers per second Np/s

ω_0 : resonant frequency / radians Per second rad/s
Undamped
natural frequency

α : neper frequency / Nepers Per second Np/s
damping factor.

The quadratic equation can be re-arranged to:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad \underline{\underline{=}} \quad s^2 + 2\alpha s + \omega_0^2 = 0$$

Now because we have two roots for the quadratic equation, then we could have two possible solutions.

$$i_1 = e^{s_1 t}, \quad i_2 = e^{s_2 t}$$

 i_1 and i_2 are two linearly independent solutions of a linear, homogeneous second order D.E., then the general solution is

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

For two Real Roots

A_1, A_2 } arbitrary constants
determined from the
initial values -
 $i|_{t=0}, \quad \frac{di}{dt}|_{t=0}$

From the initial values

$$i|_{t=0} = I_0 \quad \text{----- (1)}$$

$$R i_{(0)} + L \frac{di_{(0)}}{dt} + \underbrace{\frac{1}{C} \int i_{(0)} dt}_{V_{(0)}} \Rightarrow L \frac{di_{(0)}}{dt} = -R i_0 - V_{(0)}$$

$$\left. \frac{di}{dt} \right|_{t=0} = -\frac{1}{L} (R I_0 + V_0) \quad \text{----- (2)}$$

From the general Roots, we can notice that there are three Solutions


1 - $\alpha > \omega_0$ (overdamped case)

2 - $\alpha = \omega_0$ (critically damped case)

3 - $\alpha < \omega_0$ (underdamped case)



Damping :- The gradual loss of the initial stored energy, as noticed by the continuous decrease in the amplitude of the response.

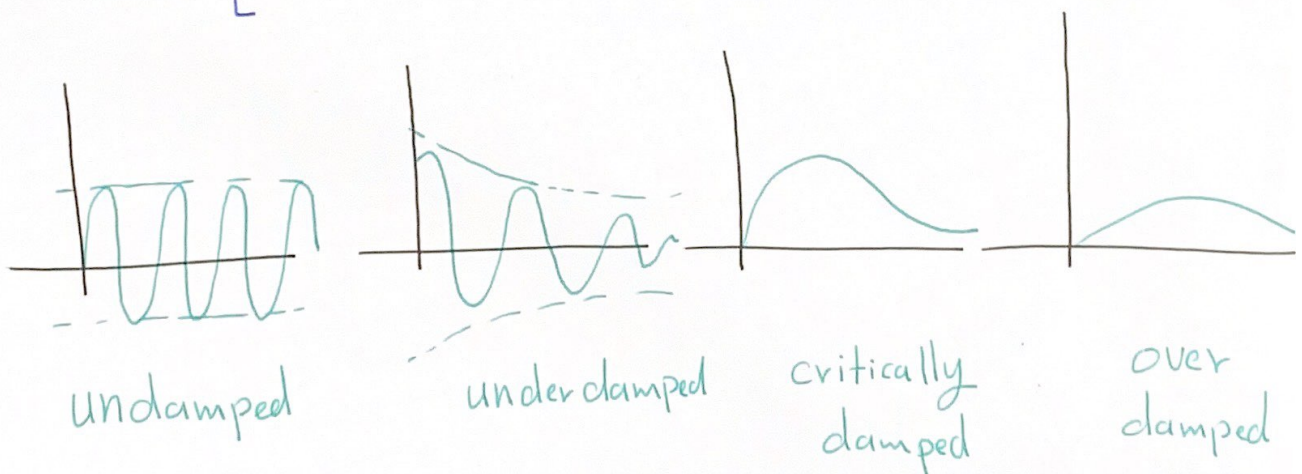- Damping is due to the presence of resistance R
- The damping factor α determines the rate at which the response is damped. $\alpha = \frac{R}{2L}$
- If $R=0$, then $\alpha=0$, $\Rightarrow$ LC circuit (loss-less).
The response is undamped and oscillatory.
(infinite oscillation).
- By adjusting the value of R , the response can be made [



Ex: The switch moves from Position A to Position B at $t=0$
 let $V_0=0$, find V_t for $t>0$.

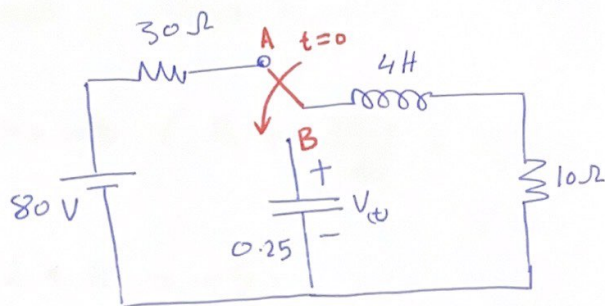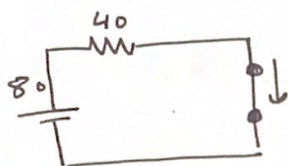In Position A we have RL circuit in steady state mode



$i_L = \frac{V}{R} = \frac{80}{40} = 2A$ and as $i_0^- = i_0$ this current will be initial current at B.

In Position B

We have a source Free series RLC circuit.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad \text{Np/s}$$

$$\alpha = \frac{R}{2L} = \frac{10}{2 \cdot 4} = 1.25 \quad \text{Np/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4} \cdot 4}} = 1 \quad \text{rad/s}$$

$$s_{1,2} = -1.25 \pm \sqrt{(1.25)^2 - 1^2} = -1.25 \pm 0.75$$


$$s_1 = -2$$

$$s_2 = -0.5$$

As two Real Roots, the general solution is

$$i = A e^{-2t} + B e^{-0.5t}$$

(Next we have to find A and B)

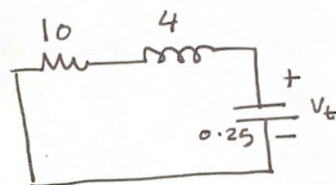

We use the initial conditions to find A and B

$$i_0 = 2 \text{ A} \quad V_{C(0)} = 0 \quad \text{and} \quad V_R + V_L + V_C = 0$$

$$iR + L \frac{di}{dt} + V_C = 0 \quad \text{at } t=0 \Rightarrow i_0 R + L \frac{di_0}{dt} + V_{C(0)} = 0$$

$$\frac{di_0}{dt} = -\frac{1}{L} (i_0 R) = -\frac{1}{4} \times 2 \times 10 = -5$$

Now Back to our current equation.

$$i = A e^{-2t} + B e^{-0.5t}$$

$$\textcircled{1} \text{ at } t=0 \quad i|_{t=0} = 2$$

$$\Rightarrow i_0 = A + B = 2 \quad \text{--- (1)}$$

$$\textcircled{2} \quad \frac{di}{dt} = -2A e^{-2t} - \frac{B}{2} e^{-0.5t} \quad \text{and} \quad \frac{di_0}{dt} = -5$$

$$-2A - \frac{B}{2} = -5 \quad \text{--- (2)}$$

from 1 and 2

$$\begin{aligned} A + B &= 2 \\ -2A - \frac{1}{2}B &= -5 \end{aligned} \Rightarrow \begin{aligned} B &= -0.666 \\ A &= 2.666 \end{aligned}$$

$$i(t) = 2.666 e^{-2t} - 0.666 e^{-0.5t}$$

$$V_R + V_L + V_C = 0 \quad \text{and} \quad V_C = V_t = V_R + V_L$$

$$R = 10 \Omega \quad \quad \quad = iR + L \frac{di}{dt}$$

$$iR = 26.66 e^{-2t} - 6.66 e^{-0.5t}$$

$$L \frac{di}{dt} = 4 \left[-5.332 e^{-2t} + 0.333 e^{-0.5t} \right]$$

$$= - \frac{21.332}{1.332} e^{-2t} + \frac{0.333}{1.332} e^{-0.5t}$$

$$V_t = iR + L \frac{di}{dt} = 5.328 e^{-2t} - 5.32 e^{-0.5t}$$

OR

$$V_t = A e^{-2t} + B e^{-0.5t}$$

$$V_0 = 0 \Rightarrow A + B = 0 \dots \textcircled{1}$$

$$i_c = \frac{c dv}{dt} \Rightarrow \frac{dv}{dt} = \frac{i_c}{c} \text{ and } \frac{dv}{dt} = \frac{I_0}{c} = \frac{-2}{0.25}$$

$$\frac{dv}{dt} = -8$$

$$\frac{dV}{dt} = -2A e^{-2t} - \frac{1}{2} B e^{-0.5t} \text{ and } -2A e^{-2t} - \frac{1}{2} B e^{-0.5t} = -8$$

$$-2A - \frac{1}{2} B = -8 \dots \textcircled{2}$$


From 1 and 2

$$A = 5.33$$

$$B = -5.33$$

$$V_t = 5.33 e^{-2t} - 5.33 e^{-0.5t}$$

EX: Find $V_{(t)}$ for $t \geq 0$

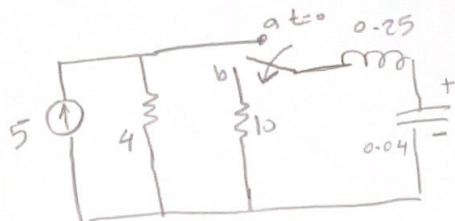

$$I_0 = 0, V_0 = 20$$

$$i(t) = 2.309 (e^{-37.32t} - e^{-2.67t})$$

$$V_t = 21.55 e^{-2.67t} - 1.55 e^{-37.32t}$$

(7)