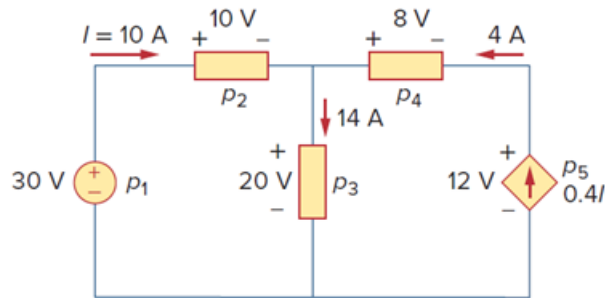


Problem

Find the power absorbed by each of the elements in Fig. 1.29.

Figure 1.29:



Step-by-step solution

Step 1 of 4

The following is the given circuit diagram:

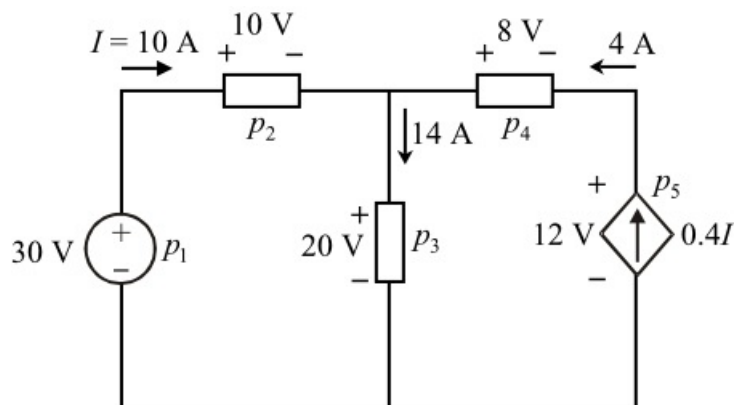


Figure 1

Step 2 of 4

If the current is entering into positive terminal, the power absorbed is positive (+ve). If the current is entering into negative terminal, the power absorbed is negative (-ve).

The power absorbed by the 30 V source is,

$$p_1 = (-30)(10) \\ = -300 \text{ W}$$

Therefore, the power absorbed by 30 V source, p_1 is $\boxed{-300 \text{ W}}$.

The power absorbed by the element 2 is,

$$p_2 = (10)(10) \\ = 100 \text{ W}$$

Therefore, the power absorbed by element 2, p_2 is $\boxed{100 \text{ W}}$.

Step 3 of 4

The power absorbed by the element 3 is,

$$\begin{aligned} p_3 &= (20)(14) \\ &= 280 \text{ W} \end{aligned}$$

Therefore, the power absorbed by element 3, p_3 is .

The power absorbed by the element 4 is,

$$\begin{aligned} p_4 &= (-8)(4) \\ &= -32 \text{ W} \end{aligned}$$

Therefore, the power absorbed by element 4, p_4 is .

Step 4 of 4

The power absorbed by the current dependent current source is,

$$\begin{aligned} p_5 &= (-12)(0.4I) \\ &= (-12)(0.4 \times 10) \\ &= -48 \text{ W} \end{aligned}$$

Therefore, the power absorbed by the current dependent current source, p_5 is .