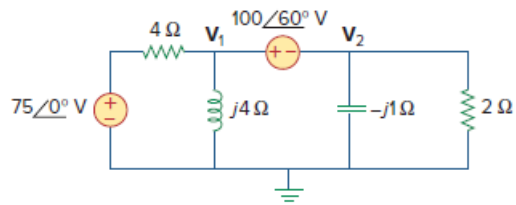


Problem

Calculate V_1 and V_2 in the circuit shown in Fig. 10.6.

Figure 10.6:



Step-by-step solution

Step 1 of 3

Consider the following circuit diagram:

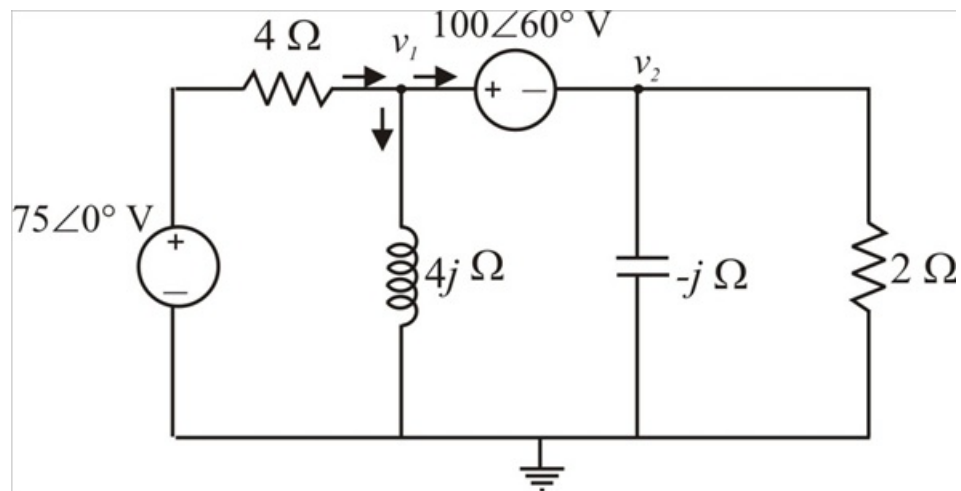


Figure 1

Step 2 of 3

Apply Kirchhoff's current law at node 1 of circuit in Figure 1.

$$\frac{V_1 - 75\angle 0^\circ \text{ V}}{4 \Omega} + \frac{V_1}{j4 \Omega} + \frac{V_2}{-j1 \Omega} + \frac{V_2}{2 \Omega} = 0$$

$$V_1 - 75\angle 0^\circ - jV_1 + j4V_2 + 2V_2 = 0$$

$$V_1(1 - j) + V_2(2 + j4) = 75 \dots\dots (1)$$

From Figure 1, write the following expression:

$$\begin{aligned} V_1 &= V_2 + 100\angle 60^\circ \\ &= V_2 + (50 + j86.60) \end{aligned}$$

Substitute the value of V_1 in equation (1).

$$\begin{aligned} 75 &= (V_2 + 50 + j86.60)(1 - j) + V_2(2 + j4) \\ &= V_2 - jV_2 + (50 + j86.60) - j(50 + j86.60) + 2V_2 + j4V_2 \end{aligned}$$

$$\begin{aligned} V_2 &= \frac{-61.60 - j36.60}{3 + j3} \\ &= 16.88\angle 165.72^\circ \text{ V} \end{aligned}$$

Therefore, the value of voltage V_2 is $\boxed{16.88\angle 165.72^\circ \text{ V}}$.

Step 3 of 3

Calculate the value of V_1 .

$$\begin{aligned} V_1 &= V_2 + 100\angle 60^\circ \\ &= 16.88\angle 165.72^\circ + 100\angle 60^\circ \\ &= 96.8\angle 69.66^\circ \text{ V} \end{aligned}$$

Therefore, the value of voltage V_1 is $\boxed{96.8\angle 69.66^\circ \text{ V}}$.

Therefore, the voltages V_1 and V_2 values are calculated.