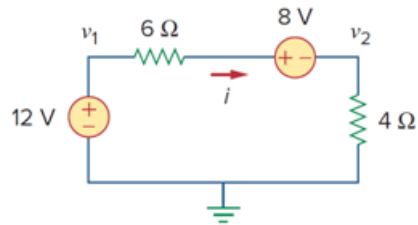


Problem

For the circuit in Fig. 3.47, v_1 and v_2 are related as:

- (a) $v_1 = 6i + 8 + v_2$
- (b) $v_1 = 6i - 8 + v_2$
- (c) $v_1 = -6i + 8 + v_2$
- (d) $v_1 = -6i - 8 + v_2$

Figure 3.47



Step-by-step solution

Step 1 of 3

Consider the following circuit:

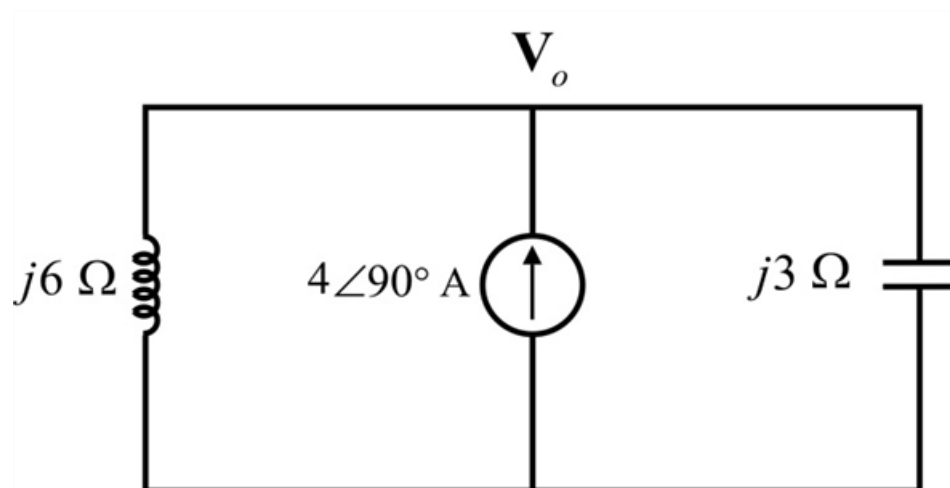


Figure 1

Step 2 of 3

Apply Kirchhoff's current law at the node of voltage $\mathbf{V}_o$.

$$\frac{\mathbf{V}_o}{j6} - 4\angle 90^\circ + \frac{\mathbf{V}_o}{-j3} = 0$$

$$\mathbf{V}_o \left(\frac{1}{j6} - \frac{1}{j3} \right) = 4\angle 90^\circ$$

$$\mathbf{V}_o \left(\frac{-j3}{(j6)(j3)} \right) = j4$$

$$\mathbf{V}_o \left(\frac{-1}{j6} \right) = j4$$

Simplify further,

$$\begin{aligned}\mathbf{V}_o &= -(j4)(j6) \\ &= 24 \text{ V}\end{aligned}$$

Step 3 of 3

Therefore, the value of voltage $\mathbf{V}_o$ is 24 V.

Hence, the correct option is **(d)**.