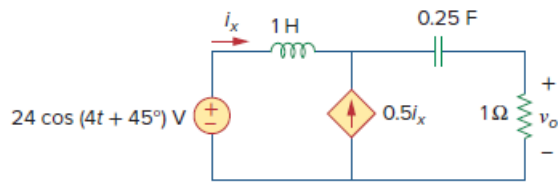


Problem

Compute $v_o(t)$ in the circuit of Fig. 10.53.

Figure 10.53:



Step-by-step solution

Step 1 of 3

Refer to circuit diagram in Figure 10.53 in the textbook.

Calculate the impedance value of inductor.

$$\begin{aligned} X_L &= j\omega L \\ &= j(4)(1) \\ &= j4 \, \Omega \end{aligned}$$

Calculate the impedance value of capacitor.

$$\begin{aligned} X_C &= \frac{1}{j\omega C} \\ &= \frac{1}{j(4)(0.25)} \\ &= -j \, \Omega \end{aligned}$$

Step 2 of 3

The frequency domain equivalent circuit is shown in Figure 1.

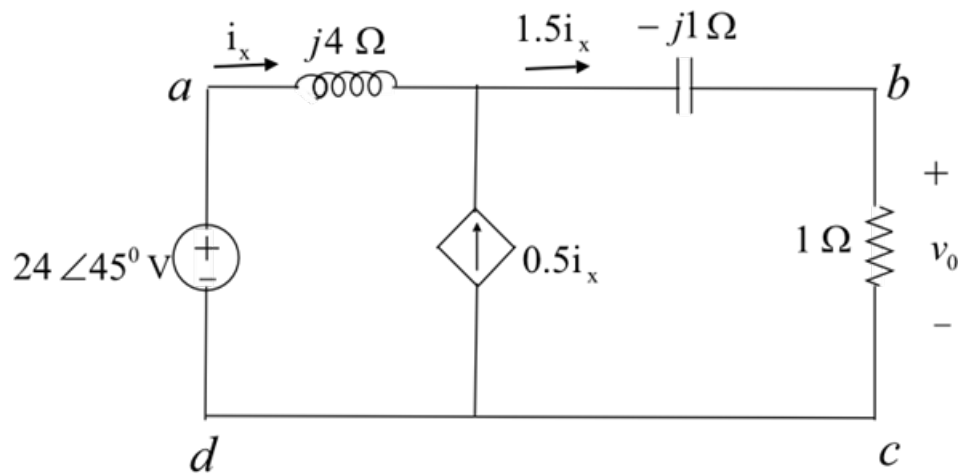


Figure 1

Step 3 of 3

Apply Kirchhoff's voltage law to outer loop of the circuit.

$$(j4)i_x + (-j+1)(1.5i_x) - 24\angle 45^\circ = 0$$

$$(-j1.5 + 1.5 + j4)i_x = 24\angle 45^\circ$$

$$(1.5 + j2.5)i_x = 24\angle 45^\circ$$

$$i_x = \frac{24\angle 45^\circ}{2.915\angle 59^\circ}$$
$$= 8.23\angle -14^\circ \text{ A}$$

Calculate the output voltage using ohm's law.

$$v_o = (1\ \Omega)(1.5i_x)$$

Substitute $8.23\angle -14^\circ \text{ A}$ for i_x .

$$v_o = (1\ \Omega)(1.5)(8.23\angle -14^\circ \text{ A})$$
$$= 12.3\angle -14^\circ \text{ V}$$

The output voltage in time domain form is,

$$v_o(t) = 12.3\cos(4t - 14^\circ) \text{ V}$$

Therefore, the output voltage, $v_o(t)$ in the circuit is $\boxed{12.3\cos(4t - 14^\circ) \text{ V}}$.