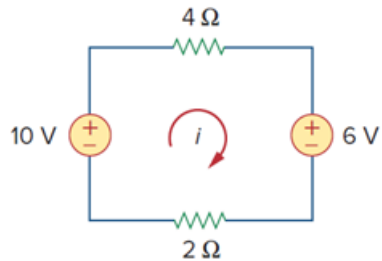


Problem

The current i in the circuit of Fig. 3.48 is:

- (a) -2.667 A
- (b) -0.667 A
- (c) 0.667 A
- (d) 2.667 A

Figure 3.48



Step-by-step solution

Step 1 of 2

If a circuit contains sources of different frequencies, then we have to find the current i_x due to the source $\sin(2t)$ individually and the current i_x due to the source $\sin(10t)$ individually then add both the responses.

Step 2 of 2

So, when the sources are different frequencies then we have to use the superposition theorem.

Therefore, the correct option is (b) .