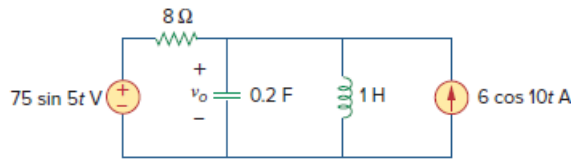


## Problem

Calculate  $v_o$  in the circuit of Fig. 10.15 using the superposition theorem.

**Figure 10.15:**



## Step-by-step solution

## Step 1 of 11

Consider the following circuit diagram:

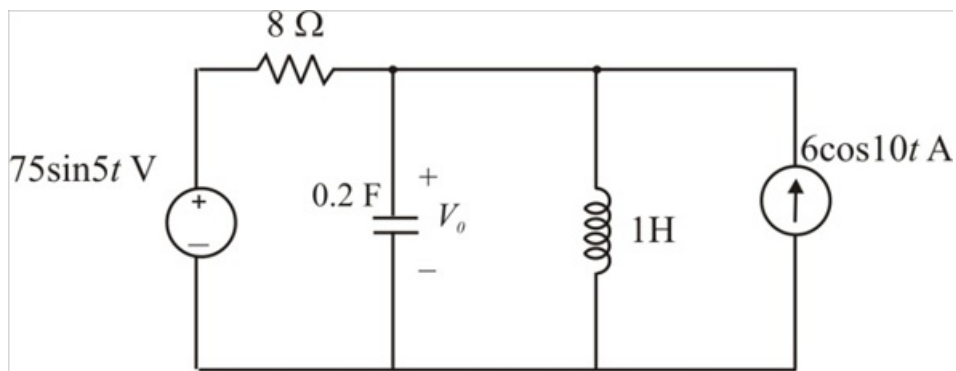


Figure 1

## Step 2 of 11

Let us assume that  $V_o = V_o' + V_o''$ .

According to superposition theorem  $V_o'$  and  $V_o''$  are the voltages due to voltage and current sources respectively.

Consider the following circuit in which current source is kept open circuit to find  $V_o'$ .

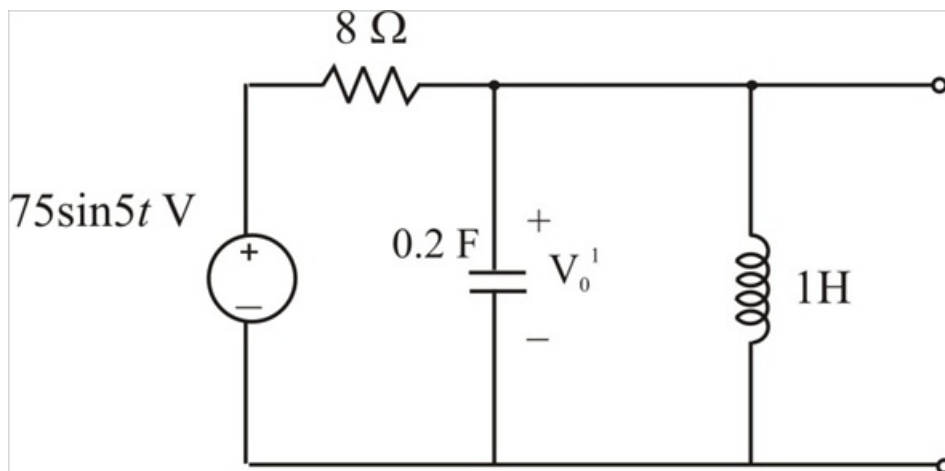


Figure 2

## Step 3 of 11

Convert the circuit to frequency domain.

$$75\sin 5t = 75\angle -90^\circ$$

And

$$\omega = 5 \text{ rad/s}$$

Convert the inductance value.

$$L = 1 \text{ H}$$

$$\begin{aligned} j\omega L &= j(5 \text{ rad/s})(1 \text{ H}) \\ &= j5 \Omega \end{aligned}$$

Convert the capacitance value.

$$C = 0.2 \text{ F}$$

$$\begin{aligned} \frac{1}{j\omega C} &= \frac{1}{j(5 \text{ rad/s})(0.2 \text{ F})} \\ &= \frac{1}{j1} \Omega \\ &= -j1 \Omega \end{aligned}$$

**Step 4** of 11

Draw the equivalent frequency domain circuit:

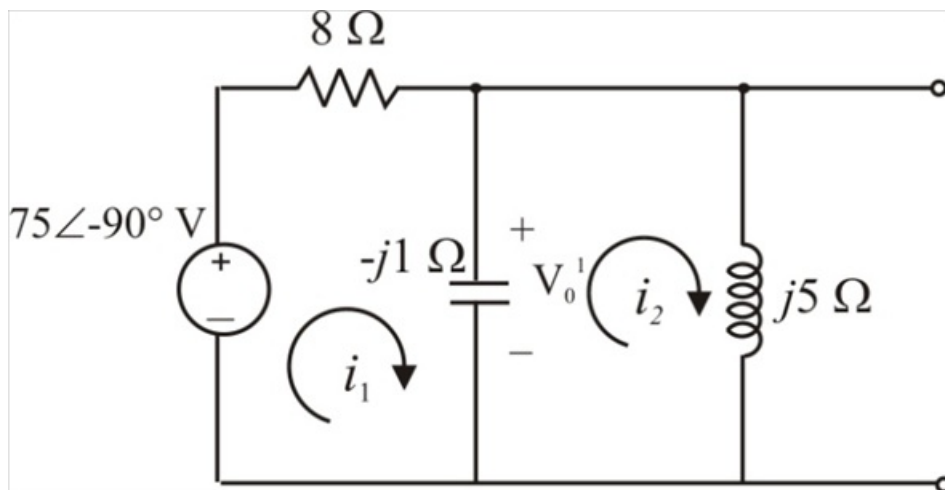


Figure 3

**Step 5** of 11

Assume that the currents  $\mathbf{I}_1$  and  $\mathbf{I}_2$  are flowing in the circuit.

Apply Kirchhoff's voltage law to mesh 1.

$$8\mathbf{I}_1 - j(\mathbf{I}_1 - \mathbf{I}_2) = 75\angle -90^\circ$$

$$(8 - j)\mathbf{I}_1 + j\mathbf{I}_2 = -j75 \dots\dots (1)$$

Apply Kirchhoff's voltage law to mesh 2.

$$-j(\mathbf{I}_2 - \mathbf{I}_1) + j5\mathbf{I}_2 = 0$$

$$j\mathbf{I}_1 + j4\mathbf{I}_2 = 0 \dots\dots (2)$$

Write equations (1) and (2) in the matrix form.

$$\begin{bmatrix} 8-j & j \\ j & j4 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} -j75 \\ 0 \end{bmatrix}$$

Calculate the determinant values of matrices to find  $\mathbf{I}_1$  and  $\mathbf{I}_2$ .

$$\begin{aligned} \Delta &= \begin{vmatrix} 8-j & j \\ j & j4 \end{vmatrix} \\ &= (8-j)(j4) - (j)(j) \\ &= j32 + 4 + 1 \\ &= 5 + j32 \end{aligned}$$

$$\begin{aligned} \Delta_1 &= \begin{vmatrix} -j75 & j \\ 0 & j4 \end{vmatrix} \\ &= (-j75)(j4) - (j)(0) \\ &= 300 \end{aligned}$$

$$\begin{aligned} \Delta_2 &= \begin{vmatrix} 8-j & -j75 \\ j & 0 \end{vmatrix} \\ &= (8-j)(0) - (-j75)(j) \\ &= -75 \end{aligned}$$

#### Step 6 of 11

Calculate the current  $\mathbf{I}_1$  in mesh 1:

$$\begin{aligned} \mathbf{I}_1 &= \frac{\Delta_1}{\Delta} \\ &= \frac{300}{5 + j32} \\ &= 9.26\angle -81.11^\circ \text{ A} \end{aligned}$$

Calculate the current  $\mathbf{I}_2$  in mesh 2:

$$\begin{aligned} \mathbf{I}_2 &= \frac{\Delta_2}{\Delta} \\ &= \frac{-75}{5 + j32} \\ &= 2.31\angle 98.88^\circ \end{aligned}$$

Calculate the value of voltage  $\mathbf{V}'_o$ :

$$\begin{aligned} \mathbf{V}'_o &= (\mathbf{I}_1 - \mathbf{I}_2)(-j1 \Omega) \\ &= (9.26\angle -81.11^\circ - 2.31\angle 98.88^\circ)(1\angle -90^\circ) \\ &= 11.57\angle -171.11^\circ \end{aligned}$$

Convert the voltage value  $\mathbf{V}'_o$  to time domain.

$$\begin{aligned} \mathbf{V}'_o &= 11.57\cos(5t - 171.11^\circ) \\ &= 11.57\sin(5t - 81.11^\circ) \end{aligned}$$

The value of voltage  $v'_o$  is  $11.57\sin(5t - 81.11^\circ) \text{ V}$ .

Consider the following circuit in which voltage source is kept short circuit to find  $V_o''$ .

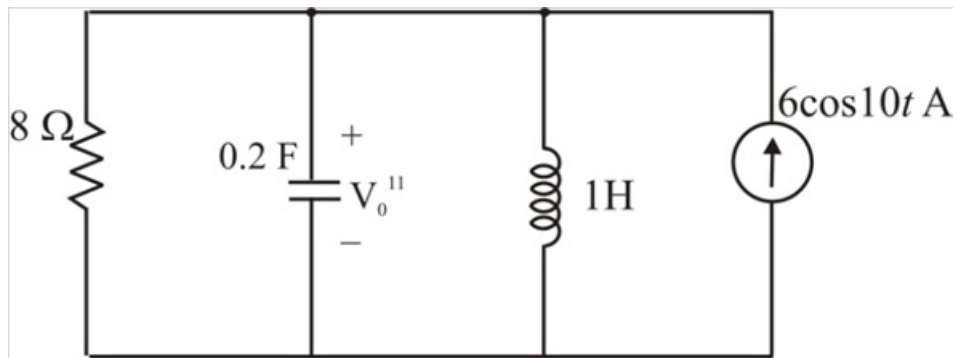


Figure 4

## Step 8 of 11

Convert the circuit to frequency domain.

$$6 \cos 10t = 6 \angle 0^\circ$$

And

$$\omega = 10 \text{ rad/s}$$

Convert the inductance value.

$$L = 1 \text{ H}$$

$$\begin{aligned} j\omega L &= j(10 \text{ rad/s})(1 \text{ H}) \\ &= j10 \Omega \end{aligned}$$

Convert the capacitance value.

$$C = 0.2 \text{ F}$$

$$\begin{aligned} \frac{1}{j\omega C} &= \frac{1}{j(10 \text{ rad/s})(0.2 \text{ F})} \\ &= \frac{1}{j2} \Omega \\ &= -j0.5 \Omega \end{aligned}$$

## Step 9 of 11

Draw the equivalent frequency domain circuit:

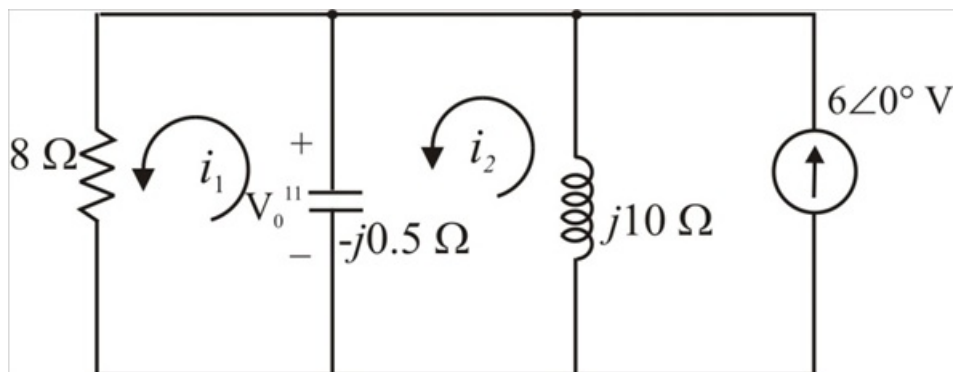


Figure 5

Assume that the currents  $\mathbf{I}_1$  and  $\mathbf{I}_2$  are flowing in the circuit.

Apply Kirchhoff's voltage law to mesh 2.

$$(\mathbf{I}_2 - 6)(j10) - j0.5(\mathbf{I}_2 - \mathbf{I}_1) = 0$$

$$(j10 - j0.5)\mathbf{I}_2 + j0.5\mathbf{I}_1 = j60$$

$$j9.5\mathbf{I}_2 + j0.5\mathbf{I}_1 = j60 \dots\dots (1)$$

Apply Kirchhoff's voltage law to mesh 1.

$$8\mathbf{I}_1 - j0.5(\mathbf{I}_1 - \mathbf{I}_2) = 0$$

$$(8 - j0.5)\mathbf{I}_1 + j0.5\mathbf{I}_2 = 0 \dots\dots (2)$$

Represent the equations (1) and (2) in matrix form.

$$\begin{bmatrix} j0.5 & j9.5 \\ 8 - j0.5 & j0.5 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} j60 \\ 0 \end{bmatrix}$$

Calculate the determinant values of matrices to find  $\mathbf{I}_1$  and  $\mathbf{I}_2$ .

$$\begin{aligned} \Delta &= \begin{vmatrix} j0.5 & j9.5 \\ 8 - j0.5 & j0.5 \end{vmatrix} \\ &= (j0.5)(j0.5) - (j9.5)(8 - j0.5) \\ &= -5 - j76 \end{aligned}$$

$$\begin{aligned} \Delta_1 &= \begin{vmatrix} j60 & j9.5 \\ 0 & j0.5 \end{vmatrix} \\ &= (j60)(j0.5) - (j9.5)(0) \\ &= -30 \end{aligned}$$

$$\begin{aligned} \Delta_2 &= \begin{vmatrix} j0.5 & j60 \\ 8 - j0.5 & 0 \end{vmatrix} \\ &= (j0.5)(0) - (j60)(8 - j0.5) \\ &= -30 - j480 \end{aligned}$$

Calculate the current  $\mathbf{I}_1$  in mesh 1:

$$\begin{aligned}\mathbf{I}_1 &= \frac{\Delta_1}{\Delta} \\ &= \frac{-30}{-5-j76} \\ &= 0.393\angle -86.23^\circ \text{ A}\end{aligned}$$

Calculate the current  $\mathbf{I}_2$  in mesh 2:

$$\begin{aligned}\mathbf{I}_2 &= \frac{\Delta_2}{\Delta} \\ &= \frac{-30-j480}{-5-j76} \\ &= 6.31\angle 0.187^\circ \text{ A}\end{aligned}$$

Calculate the value of voltage  $\mathbf{V}_o''$ :

$$\begin{aligned}\mathbf{V}_o'' &= (\mathbf{I}_1 - \mathbf{I}_2)(-j0.5 \Omega) \\ &= (0.393\angle -86.23^\circ \text{ A} - 6.31\angle 0.187^\circ \text{ A})(0.5\angle -90^\circ) \\ &= (6.302\angle -176.24^\circ)(0.5\angle -90^\circ) \\ &= 3.15\angle 93.75^\circ\end{aligned}$$

Convert the voltage value  $\mathbf{V}_o''$  to time domain.

$$\begin{aligned}\mathbf{V}_o'' &= 3.15\cos(10t - 180^\circ + 93.75^\circ) \\ &= 3.15\cos(10t - 86.25^\circ)\end{aligned}$$

The value of voltage  $v_o''$  is  $3.15\cos(10t - 86.25^\circ) \text{ V}$ .

#### Step 11 of 11

Calculate the value of required voltage  $v_o$ :

$$\begin{aligned}\mathbf{V}_o &= \mathbf{V}_o' + \mathbf{V}_o'' \\ &= 11.57\sin(5t - 81.11^\circ) \text{ V} + 3.15\cos(10t - 86.25^\circ) \text{ V}\end{aligned}$$

Hence, the following is the required voltage value  $v_o$ .

$$\boxed{(11.57\sin(5t - 81.11^\circ) + 3.15\cos(10t - 86.25^\circ)) \text{ V}}.$$