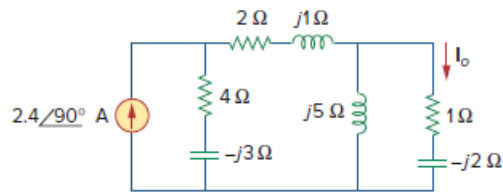


Problem

Find I_o in the circuit of Fig. 10.19 using the concept of source transformation.

Figure 10.19:



Step-by-step solution

Step 1 of 5

Refer the figure 10.19 in the text book.

First transform the current source into a voltage source. Determine the value of voltage source.

$$\begin{aligned} V_s &= (2.4\angle 90^\circ)(4 - j3) \\ &= (2.4\angle 90^\circ)(5\angle -36.87^\circ) \\ &= 12\angle 53.13^\circ \text{ V} \end{aligned}$$

Re-draw the circuit diagram:

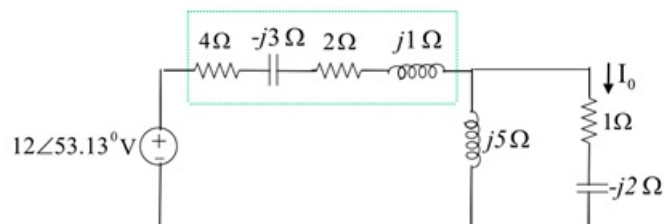


Figure 1

Step 2 of 5

Determine the series combination of $4 - j3$ and $2 + j$ impedances.

$$\begin{aligned} Z_1 &= 4 - j3 + 2 + j \\ &= (6 - j2) \Omega \end{aligned}$$

Convert the voltage source to a current source. Determine the value of current source.

$$\begin{aligned} I_s &= \frac{V_s}{Z_1} \\ &= \frac{12 \angle 53.13^\circ}{6 - j2} \\ &= 1.9 \angle 71.56^\circ \text{ A} \end{aligned}$$

Re-draw the circuit diagram.

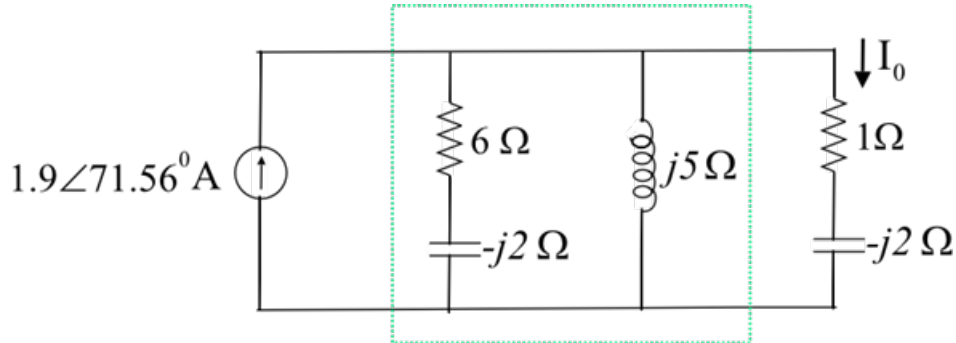


Figure 2

Step 3 of 5

Determine the parallel combination of $6 - j2$ and $j5$ impedances.

$$\begin{aligned} Z_2 &= \frac{(6 - j2)j5}{6 - j2 + j5} \\ &= \frac{10 + j30}{6 + j3} \\ &= 4.71 \angle 45^\circ \\ &= 3.33 + j3.33 \Omega \end{aligned}$$

Step 4 of 5

Re-draw the simplified circuit as shown in figure 3.

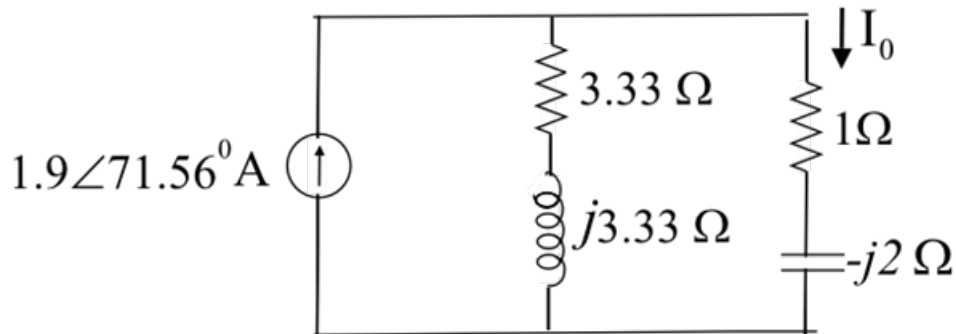


Figure 3

Step 5 of 5

From Figure 3, apply current division rule and determine the value of I_0 .

$$\begin{aligned} I_0 &= 1.9 \angle 71.56^\circ \times \frac{3.33 + j3.33}{3.33 + j3.33 + 1 - j2} \\ &= 1.9 \angle 71.56^\circ \times \frac{3.33 + j3.33}{4.33 + j1.33} \\ &= 1.9 \angle 71.56^\circ \times \frac{4.71 \angle 45^\circ}{4.53 \angle 17.07^\circ} \\ &= 1.97 \angle 99.49^\circ \text{ A} \end{aligned}$$

Therefore, the value of current I_0 is $1.97 \angle 99.49^\circ \text{ A}$.