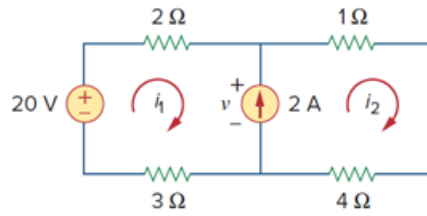


Problem

In the circuit of Fig. 3.49, current i_1 is:

- (a) 4 A
- (b) 3 A
- (c) 2 A
- (d) 1 A

Figure 3.49:



Step-by-step solution

Step 1 of 1

Answer: (a)

$$3.535 \angle -45^\circ \text{ V}$$