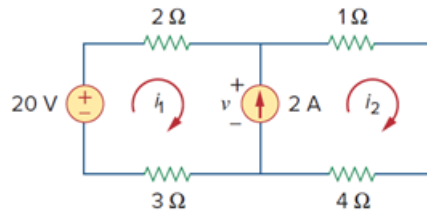


Problem

The voltage v across the current source in the circuit of Fig. 3.49 is:

- (a) 20 V
- (b) 15 V
- (c) 10 V
- (d) 5 V

Figure 3.49:



Step-by-step solution

Step 1 of 1

Answer: (a)

$$-j4 \, \Omega$$