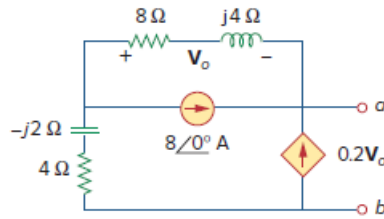


Problem

Determine the Thevenin equivalent of the circuit in Fig. 10.27 as seen from the terminals a - b .

Figure 10.27:



Step-by-step solution

Step 1 of 7

Refer to Figure 10.27 in the textbook.

Replace the current source by the open circuit to calculate the Thevenin's impedance, Z_{Th} .

Place a test current source to calculate the Thevenin's impedance, Z_{Th} .

Calculate the Thevenin's impedance in Figure 1.

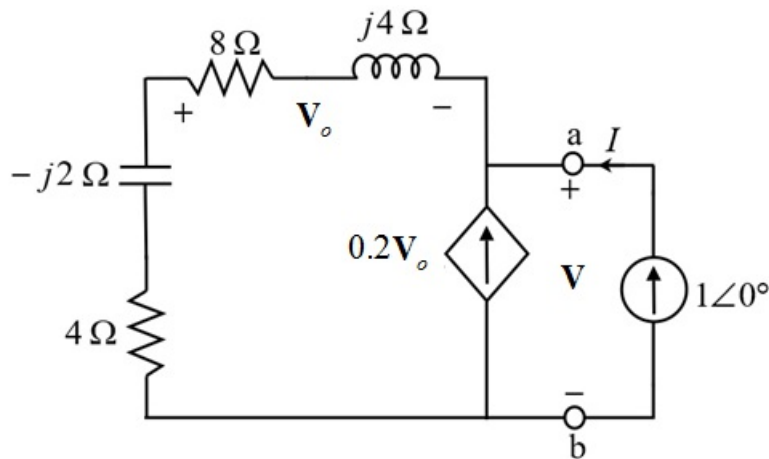


Figure 1

Step 2 of 7

Apply the voltage division and calculate the voltage, V_o .

$$\begin{aligned} V_o &= -\frac{V(8 + j4)}{(8 + j4 + 4 - j2)} \\ &= -(0.702 + j0.216)V \end{aligned}$$

Apply the nodal analysis at node a in Figure 1.

$$0.2V_o + 1 = \frac{V}{(8 + j4 + 4 - j2)}$$

Substitute $V(0.735 \angle -162.89^\circ)$ for V_o .

$$-0.2(0.702 + j0.216)V + 1 = \frac{V}{(8 + j4 + 4 - j2)}$$

$$V(0.081 - j0.0135 + 0.1405 + j0.0432) = 1$$

$$\begin{aligned} V &= \frac{1}{(0.2216 + j0.0296)} \\ &= 4.43 - j0.594 \end{aligned}$$

Step 3 of 7

Calculate the value of the Thevenin's impedance.

$$\begin{aligned} Z_{th} &= \frac{V}{I} \\ &= \frac{4.43 - j0.594}{1 \angle 0^\circ} \Omega \\ &= 4.47 \angle -7.64^\circ \Omega \end{aligned}$$

Thus, the Thevenin's impedance is $4.47 \angle -7.64^\circ \Omega$.

Step 4 of 7

Draw the circuit to calculate the Thevenin's voltage.

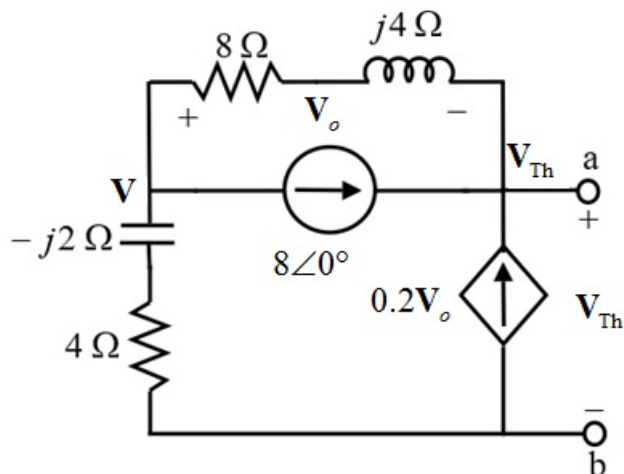


Figure 2

Step 5 of 7

Apply the nodal analysis at node, $\mathbf{V}$.

$$\frac{\mathbf{V} - \mathbf{V}_{Th}}{8 + j4} + 8\angle 0^\circ + \frac{\mathbf{V}}{4 - j2} = 0$$

$$\mathbf{V} \left(\frac{1}{4 - j2} + \frac{1}{8 + j4} \right) - \mathbf{V}_{Th} \left(\frac{1}{8 + j4} \right) + 8 = 0$$

$$\mathbf{V} (0.3 + j0.05) - \mathbf{V}_{Th} (0.1 - j0.05) + 8 = 0$$

$$\mathbf{V} = \left(\frac{0.1 - j0.05}{0.3 + j0.05} \right) \mathbf{V}_{Th} - \frac{8}{0.3 + j0.05}$$

$$\mathbf{V} = (0.297 - j0.216) \mathbf{V}_{Th} - (25.94 - j4.32) \dots\dots (1)$$

Step 6 of 7

Apply the nodal analysis at the node, $\mathbf{V}_{Th}$.

$$\frac{\mathbf{V}_{Th} - \mathbf{V}}{8 + j4} - 8 - 0.2\mathbf{V}_o = 0$$

Substitute $\mathbf{V} - \mathbf{V}_{Th}$ for $\mathbf{V}_o$.

$$\frac{-\mathbf{V}_o}{8 + j4} - 8 - 0.2\mathbf{V}_o = 0$$

$$\mathbf{V}_o \left(0.2 + \frac{1}{8 + j4} \right) = -8$$

$$\mathbf{V}_o (0.3 - j0.05) = -8$$

$$\mathbf{V}_o = -25.945 - j4.324 \text{ V}$$

Step 7 of 7

Consider the expression for $\mathbf{V}_o$.

$$\mathbf{V}_o = \mathbf{V} - \mathbf{V}_{Th}$$

$$\mathbf{V} = \mathbf{V}_{Th} + \mathbf{V}_o$$

$$\mathbf{V} = \mathbf{V}_{Th} - 25.945 - j4.324$$

Calculate the value of Thevenin's voltage from equation (1).

$$\mathbf{V} = (0.297 - j0.216) \mathbf{V}_{Th} - (25.94 - j4.32)$$

$$\mathbf{V}_{Th} - 25.945 - j4.324 = (0.297 - j0.216) \mathbf{V}_{Th} - (25.94 - j4.32)$$

$$\mathbf{V}_{Th} (1 - 0.297 + j0.216) = (25.945 + j4.324) - (25.94 - j4.32)$$

$$\mathbf{V}_{Th} (1 - 0.297 + j0.216) = 5.945 \times 10^{-3} + j8.644$$

$$\mathbf{V}_{Th} = \frac{5.945 \times 10^{-3} + j8.644}{0.703 + j0.216}$$

$$= 3.46 + j11.23$$

$$= 11.754 \angle 72.88^\circ \text{ V}$$

Thus, the Thevenin's voltage is $11.754 \angle 72.88^\circ \text{ V}$.