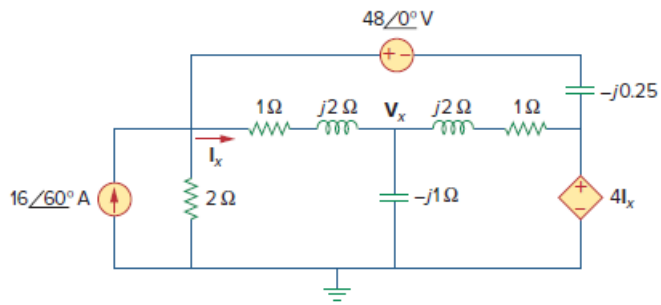


Problem

Obtain V_x and I_x in the circuit depicted in Fig. 10.40.

Figure 10.40:



Step-by-step solution

Step 1 of 4

Refer to Figure 10.30 in the textbook.

Consider the value of the angular frequency.

$$\omega = 1 \text{ rad/s}$$

Calculate the values of the inductor, L_1 .

$$X_{L1} = j2$$

$$j\omega L_1 = j2$$

$$j(1)L_1 = j2$$

$$L_1 = 2 \text{ H}$$

Calculate the values of the inductor, L_2 .

$$X_{L2} = j2$$

$$j\omega L_2 = j2$$

$$j(1)L_2 = j2$$

$$L_2 = 2 \text{ H}$$

Step 2 of 4

Calculate the values of the capacitor, C_1 .

$$X_{C1} = -j$$

$$\frac{-j\omega}{C_1} = -j$$

$$\frac{-j(1)}{C_1} = -j$$

$$C_1 = 1 \text{ F}$$

Calculate the values of the capacitor, C_2 .

$$X_{C2} = -j$$

$$\frac{-j\omega}{C_2} = -j0.25$$

$$\frac{-j(1)}{C_2} = -\frac{j}{4}$$

$$C_2 = 4 \text{ F}$$

Calculate the frequency, f .

$$f = \frac{\omega}{2\pi}$$

$$= \frac{1}{2\pi}$$

$$= 0.15915$$

Step 3 of 4

Draw the circuit in PSPICE schematics.

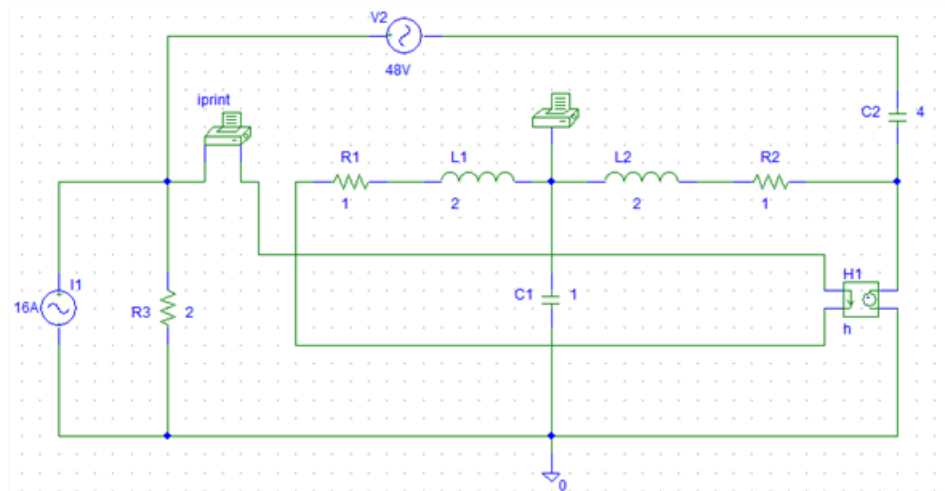


Figure 1

Step 4 of 4

The magnitude and phase of V_x and I_x are required. So, set the attributes of IPRINT and VPRINT1 each to AC = yes, MES = yes, PHASE = yes.

Go to 'Analysis' menu open setup / AC sweep and enter total pts as 1, start frequency as 0.15915 and Final frequency as 0.15915

Save the Schematic and simulate it by selecting analysis/simulate. The output file includes the source frequency in addition to the attributes checked for the pseudo components IPRINT and VPRINT1 as follows:

The outputs of the circuit are,

FREQ VM(\$N_0003) VP(\$N_0003)

1.592E-01 3.409E+01 4.955E+01

FREQ IM(V_PRINT10) IP(V_PRINT10)

1.592E-01 8.945E+00 1.627E +02

Therefore, the value of the voltage V_x is $34.09 \angle 49.55^\circ \text{ V}$ and the current, I_x is

$8.945 \angle 162.7^\circ \text{ A}$.