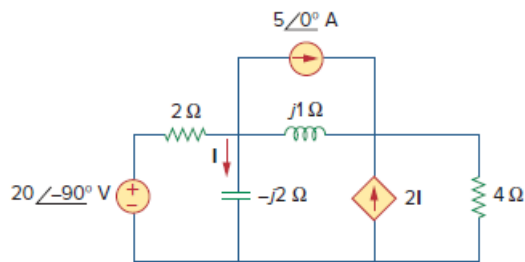


Problem

Solve for the current I in the circuit of Fig. 10.64 using nodal analysis.


Figure 10.64:



Step-by-step solution

Step 1 of 5

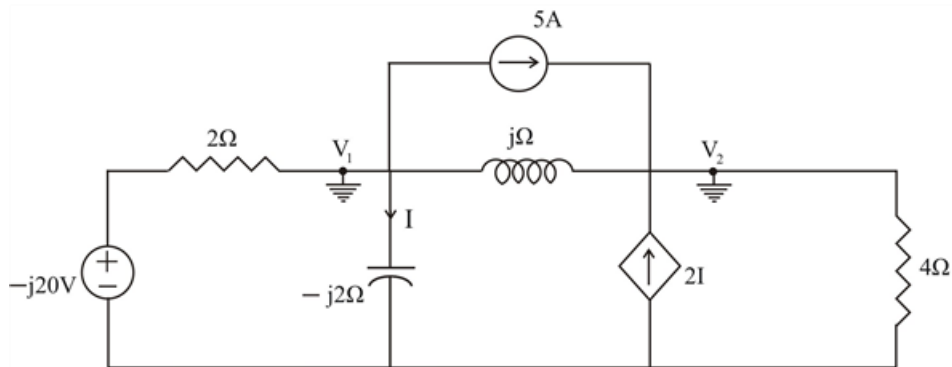We apply Nodal analysis to the circuit shown below.



Step 2 of 5

At node 1,

$$\frac{-j20 - V_1}{2} = 5 + \frac{V_1}{-j2} + \frac{V_1 - V_2}{j}$$

$$\frac{-j20 - V_1}{2} = 5 + \frac{jV_1}{2} - j(V_1 - V_2)$$

$$-j20 - V_1 = 10 + jV_1 - j2(V_1 - V_2)$$

$$-j20 = 10 + V_1(j + 1 - j2) - j2(-V_2)$$

$$-j20 = 10 + V_1(1 - j) + j2V_2$$

$$-5 - j10 = (0.5 - j0.5)V_1 + jV_2 \dots\dots\dots (1)$$

Step 3 of 5

At node 2,

$$5 + 2I + \frac{V_1 - V_2}{j} = \frac{V_2}{4}$$

Where,

$$I = \frac{V_1}{-j2}$$

Hence,

$$5 + 2\left(\frac{V_1}{-j2}\right) + \frac{V_1 - V_2}{j} = \frac{V_2}{4}$$

$$5 + jV_1 - j(V_1 - V_2) = \frac{V_2}{4}$$

$$20 + j4V_1 - j4(V_1 - V_2) = V_2$$

$$20 + V_1(j4) - j4V_1 + j4V_2 = V_2$$

$$20 + j4V_2 = V_2$$

$$20 = V_2(1 - j4)$$

$$V_2 = \frac{20}{(1 - j4)} \dots\dots\dots (2)$$

Step 4 of 5

Substituting (2) into (!),

$$-5 - j10 = (0.5 - j0.5)V_1 + j\left(\frac{20}{(1 - j4)}\right)$$

$$-45 + j10 = (-1.5 - j2.5)V_1 + 20j$$

$$-45 - j10 = (-1.5 - j2.5)V_1$$

$$\frac{-45 - j10}{(-1.5 - j2.5)} = V_1$$

$$V_1 = 10.8823 - j11.4706$$

Or,

$$V_1 = 15.811 \angle -46.51^\circ \text{ V}$$

Step 5 of 5

Therefore,

$$I = \frac{V_2}{-j2}$$

$$I = \frac{15.811 \angle -46.51^\circ}{-j2}$$

$$I = \frac{15.811 \angle -46.51^\circ}{2 \angle -90^\circ}$$

$$\therefore \boxed{I = 7.906 \angle 43.49^\circ \text{ A}}$$