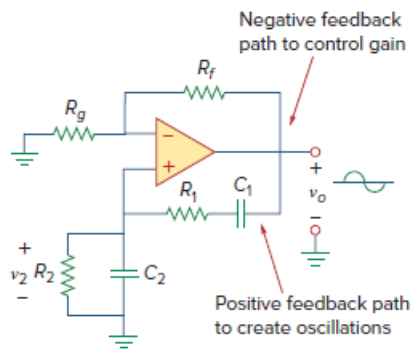


Problem

In the Wien-bridge oscillator circuit in Fig. 10.42, let $R_1 = R_2 = 2.5 \text{ k}\Omega$, $C_1 = C_2 = 1 \text{ nF}$. Determine the frequency f_o of the oscillator.


Figure 10.42: Wien-bridge oscillator.



Step-by-step solution

Step 1 of 5

Given circuit can be represented as,

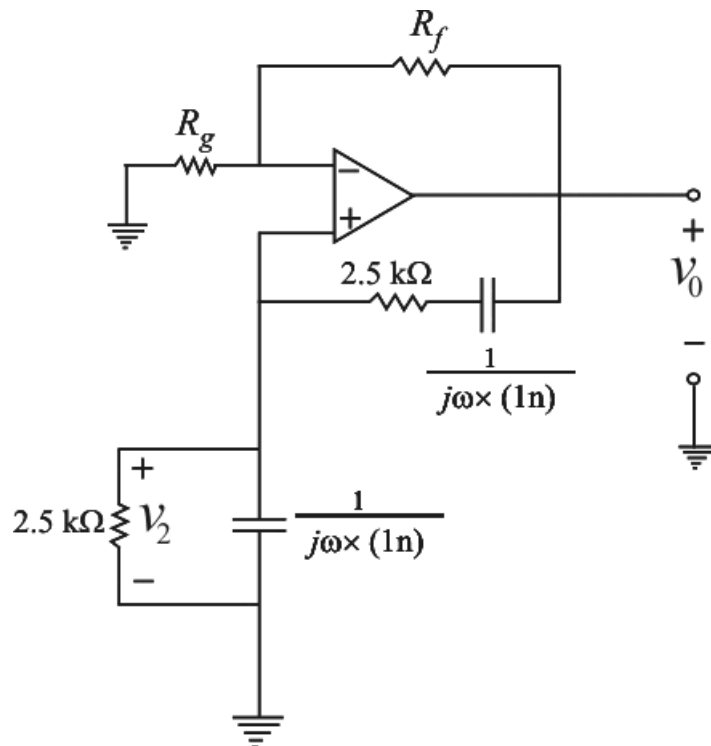

Step 2 of 5

By using voltage division to above circuit,

$$v_2 = v_0 \times \left[\frac{\left((2.5 \times 10^3) \parallel \frac{1}{j\omega \times (1 \times 10^{-9})} \right)}{\left((2.5 \times 10^3) \parallel \left(\frac{1}{j\omega \times (1 \times 10^{-9})} \right) \right) + \left[(2.5 \times 10^3) + \frac{1}{j\omega \times (1 \times 10^{-9})} \right]} \right]$$

$$v_2 = v_0 \left[\frac{\frac{\left(\frac{2.5 \times 10^3}{j\omega \times (1 \times 10^{-9})} \right)}{2.5 \times 10^3 + \frac{1}{j\omega \times (1 \times 10^{-9})}}}{\left(\frac{\frac{2.5 \times 10^3}{j\omega \times (1 \times 10^{-9})}}{2.5 \times 10^3 + \frac{1}{j\omega \times (1 \times 10^{-9})}} \right) + \left[(2.5 \times 10^3) + \frac{1}{j\omega \times (1 \times 10^{-9})} \right]} \right]$$

Step 3 of 5

$$\frac{v_2}{v_0} = \left[\frac{\left(\frac{2.5 \times 10^3}{(2.5 \times 10^3) \times (j\omega \times 1 \times 10^{-9}) + 1} \right)}{\left(\frac{2.5 \times 10^3}{(2.5 \times 10^3) \times (j\omega \times 1 \times 10^{-9}) + 1} \right) + \frac{(2.5 \times 10^3) \times (j\omega \times 10^{-9}) + 1}{(j\omega \times 1 \times 10^{-9})}} \right]$$

$$\frac{v_2}{v_0} = \left[\frac{2.5 \times 10^3}{(2.5 \times 10^3) \times (j\omega \times 1 \times 10^{-9}) + \left[(2.5 \times 10^3) \times (j\omega \times 10^{-9}) + 1 \right] \times \left[(2.5 \times 10^3) \times (j\omega \times 1 \times 10^{-9}) + 1 \right]} \right]$$

$$\frac{v_2}{v_0} = \left[\frac{(2.5 \times 10^3) \times (j\omega \times 1 \times 10^{-9})}{\left[(2.5 \times 10^3) \times (j\omega \times 1 \times 10^{-9}) \right] + \left[(2.5 \times 10^3) \times (j\omega \times 10^{-9}) + 1 \right]^2} \right]$$

Step 4 of 5

$$\frac{v_2}{v_0} = \left[\frac{(2.5 \times 10^3) \times (j\omega \times 1 \times 10^{-9})}{\left[(2.5 \times 10^3) \times (j\omega \times 1 \times 10^{-9}) \right] + \left\{ \left[(2.5 \times 10^3) \times (j\omega \times 1 \times 10^{-9}) \right]^2 + \left[2(2.5 \times 10^3) \times (j\omega \times 1 \times 10^{-9}) \right] + 1 \right\}} \right]$$

$$\frac{v_2}{v_0} = \left[\frac{(2.5 \times 10^3) \times (\omega \times 1 \times 10^{-9})}{\left[3 \times (2.5 \times 10^3) \times (\omega \times 1 \times 10^{-9}) \right] + \left[(2.5 \times 10^3)^2 \times (j\omega^2 \times (1 \times 10^{-9})^2) \right] + \frac{1}{j}} \right]$$

$$\therefore \frac{v_2}{v_0} = \left[\frac{(2.5 \times 10^3) (\omega \times 1 \times 10^{-9})}{\left[3 \times (2.5 \times 10^3) \times (\omega \times 1 \times 10^{-9}) \right] + j \left[\left(\omega^2 \times (2.5 \times 10^3)^2 \times (1 \times 10^{-9})^2 \right) - 1 \right]} \right]$$

Step 5 of 5

From the above equation,

v_2 must be in phase with v_0 , which implies that the ratio must be purely real. Hence, the imaginary part must be zero. Setting the imaginary part equal to zero gives the oscillation frequency ω_0 as

$$\left[\omega_0^2 \times (2.5 \times 10^3)^2 \times (1 \times 10^{-9})^2 \right] - 1 = 0$$

$$\omega_0^2 \times (2.5 \times 10^3)^2 \times (1 \times 10^{-9})^2 = 1$$

$$\omega_0^2 = \frac{1}{(2.5 \times 10^3)^2 \times (1 \times 10^{-9})^2}$$

$$\omega_0 = \frac{1}{\sqrt{(2.5 \times 10^3)^2 \times (1 \times 10^{-9})^2}}$$

$$2\pi f_0 = \frac{1}{(2.5 \times 10^3) \times (1 \times 10^{-9})}$$

$$2\pi f_0 = 400 \times 10^3$$

$$f_0 = \frac{400 \times 10^3}{2\pi}$$

$$f_0 = \frac{400 \times 10^3}{2 \times 3.1416}$$

$$\therefore \boxed{f_0 = 63.66 \text{ k Hz}}$$