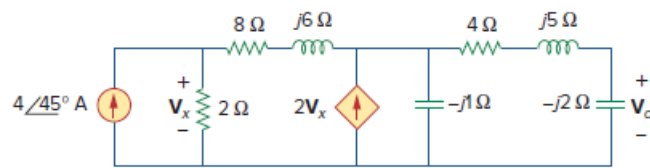


Problem

Use nodal analysis to obtain V_o in the circuit of Fig. 10.67 below.


Figure 10.67:



Step-by-step solution

Step 1 of 5

Consider the circuit shown below.

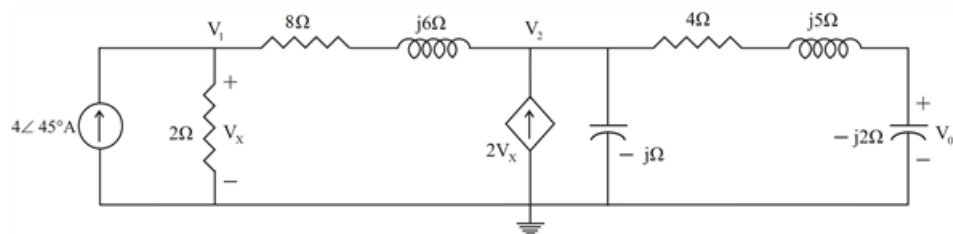

Step 2 of 5

At node 1,

$$4\angle 45^\circ = \frac{V_1}{2} + \frac{V_1 - V_2}{8 + j6}$$

$$4\angle 45^\circ = \frac{1}{2} \left[\frac{V_1}{1} + \frac{V_1 - V_2}{4 + j3} \right]$$

$$8\angle 45^\circ = V_1 \left[1 + \frac{1}{4 + j3} \right] - \frac{V_2}{4 + j3}$$

$$8\angle 45^\circ = V_1 \left[\frac{5 + j3}{4 + j3} \right] - \left(\frac{V_2}{4 + j3} \times \frac{4 - j3}{4 - j3} \right)$$

$$8\angle 45^\circ = V_1 \left[\frac{5 + j3}{4 + j3} \right] - \left(\frac{V_2(4 - j3)}{25} \right)$$

$$8\angle 45^\circ = V_1 [1.16 - j0.12] - \left(\frac{V_2(4 - j3)}{25} \right)$$

$$200\angle 45^\circ = (29 - j3)V_1 - (4 - j3)V_2 \dots \dots \dots (1)$$

Step 3 of 5

At node 2,

$$\frac{V_1 - V_2}{8 + j6} + 2V_x = \frac{V_2}{-j} + \frac{V_2}{4 + j5 - j2}$$

Where, $V_x = V_1$

$$\frac{V_1 - V_2}{8 + j6} + 2V_1 = jV_2 + \frac{V_2}{4 + j3}$$

$$V_1 \left[\frac{1}{8 + j6} + 2 \right] = V_2 \left[j + \frac{1}{4 + j3} + \frac{1}{8 + j6} \right]$$

$$V_1 \left[\frac{1 + 16 + j12}{8 + j6} \right] = V_2 \left[j + \frac{1}{2} \left(\frac{2}{4 + j3} + \frac{1}{4 + j3} \right) \right]$$

$$V_1 \left[\frac{17 + j12}{8 + j6} \right] = V_2 \left[j + \frac{1}{2} \left(\frac{3}{4 + j3} \right) \right]$$

$$V_1 \left[\frac{17 + j12}{8 + j6} \right] = V_2 \left[\left(\frac{8j - 6 + 3}{8 + j6} \right) \right]$$

$$V_1 \left[\frac{17 + j12}{8 + j6} \right] = V_2 \left[\left(\frac{-3 + j8}{8 + j6} \right) \right]$$

$$V_1 [17 + j12] = V_2 [-3 + j8]$$

$$V_1 = V_2 \left[\frac{-3 + j8}{17 + j12} \right] \dots\dots\dots (2)$$

Step 4 of 5

Substituting (2) into (1)

$$200 \angle 45^\circ = (29 - j3) \left[\frac{-3 + j8}{17 + j12} \right] V_2 - (4 - j3) V_2$$

$$200 \angle 45^\circ = [4.205 + j11.207] V_2 - (4 - j3) V_2$$

$$200 \angle 45^\circ = [(4.205 + j11.207) - (4 - j3)] V_2$$

$$200 \angle 45^\circ = [0.205 + j14.207] V_2$$

$$200 \angle 45^\circ = (14.21 \angle 89.17^\circ) V_2$$

$$\therefore V_2 = \frac{200 \angle 45^\circ}{14.21 \angle 89.17^\circ}$$

Step 5 of 5

Therefore,

$$V_0 = \left(\frac{-j2}{4+j5-j2} \right) V_2$$

$$V_0 = \left(\frac{-j2}{4+j3} \right) V_2$$

$$V_0 = (0.4 \angle -126.87^\circ) V_2$$

$$V_0 = (0.4 \angle -126.87^\circ) \times \left(\frac{200 \angle 45^\circ}{14.21 \angle 89.17^\circ} \right)$$

$$V_0 = (0.4 \angle -126.87^\circ) \times (14.07 \angle -44.17^\circ)$$

$$\therefore \boxed{V_0 = 5.628 \angle -171.04^\circ \text{ V}}$$

Or,

$$\therefore \boxed{V_0 = 5.628 \angle 189^\circ \text{ V}}$$