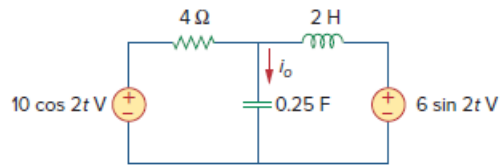


Problem

Solve for i_o in Fig. 10.73 using mesh analysis.

Figure 10.73:



Step-by-step solution

Step 1 of 6

$$\omega = 2$$

$$10 \cos(2t) \Rightarrow 10 \angle 0^\circ$$

$$6 \sin(2t) \Rightarrow 6 \angle -90^\circ$$

$$6 \angle -90^\circ = -j6$$

$$2 \text{ H} = j\omega L$$


$$j\omega L = 4j$$

$$0.25 \text{ F} \Rightarrow \frac{1}{j\omega C}$$

$$\frac{1}{j(2)\left(\frac{1}{4}\right)} = -j2$$

Step 2 of 6

The circuit is shown below.

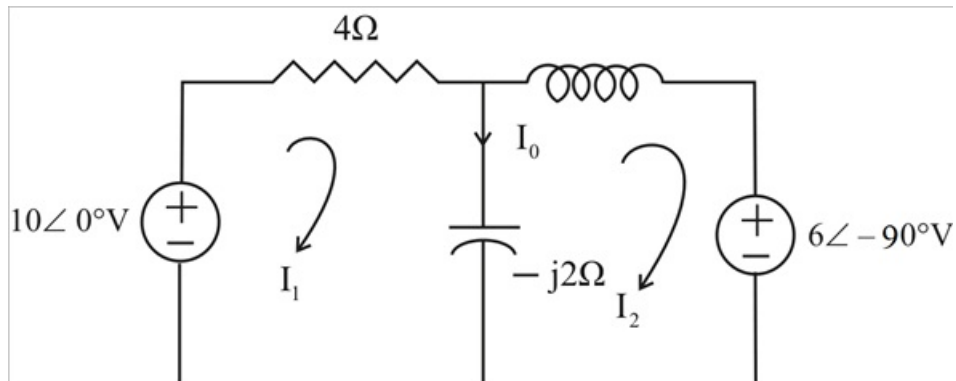

Step 3 of 6

For loop1,

$$-10 + (4 - j2)I_1 + j2I_2 = 0$$

$$5 = (2 - j)I_1 + jI_2 \dots\dots\dots (1)$$

For loop 2,

$$j2I_1 + (j4 - j2)I_2 + (-j6) = 0$$

$$j2I_1 + (j2)I_2 = j6$$

$$I_1 + I_2 = 3 \dots\dots\dots (2)$$

Step 4 of 6

In matrix form (1) & (2) become,

$$\begin{bmatrix} 2-j & j \\ 1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 3 \end{bmatrix}$$

$$\Delta = 2(1 - j)$$

$$\Delta_1 = 5 - j3$$

$$\Delta_2 = 1 - j3$$

Step 5 of 6

$$I_1 = \frac{\Delta_1}{\Delta}$$

$$I_1 = \frac{5 - j3}{2 - j2}$$

$$I_1 = 2.062 \angle 14^\circ \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta}$$

$$I_2 = \frac{1 - j3}{2 - j2}$$

$$I_2 = 1.118 \angle -26.57^\circ \text{ A}$$

Step 6 of 6

Therefore,

$$I_o = I_1 - I_2$$

$$I_o = (2.0616 \angle 14^\circ) - (1.18 \angle -26.57^\circ)$$

$$I_o = 1.414 \angle 45^\circ \text{ A}$$

$$\therefore \boxed{i_o(t) = 1.414 \cos(2t + 45^\circ) \text{ A}}$$