


Problem

Compute I in Prob. 10.15 using mesh analysis.

Step-by-step solution

Step 1 of 4

Considering the circuit below:

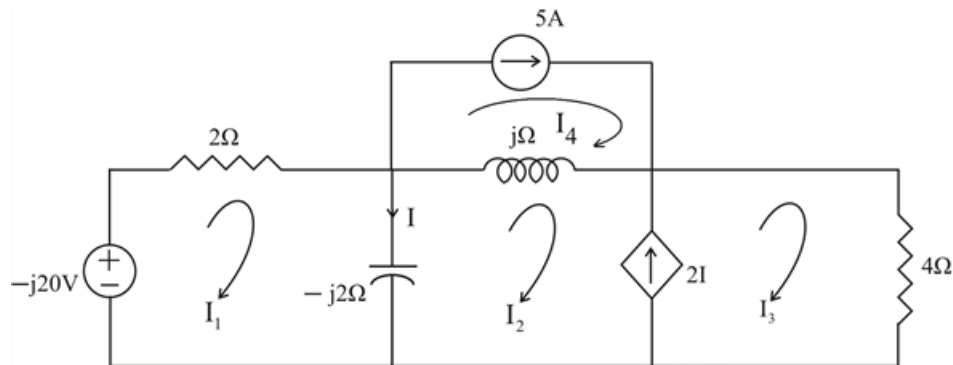

Step 2 of 4

For Mesh 1,

$$j20 + (2 - j2)I_1 + j2I_2 = 0$$

$$(1 - j)I_1 + jI_2 = -j10 \quad \dots\dots\dots (1)$$

For the Supermesh,

$$(j - j2)I_2 + j2I_1 + 4I_3 - jI_4 = 0 \quad \dots\dots\dots (2)$$

Also,

$$I_3 - I_2 = 2I$$

$$I_3 - I_2 = 2(I_1 - I_2)$$

$$I_3 = 2I_1 - I_2 \quad \dots\dots\dots (3)$$

For Mesh 4,

$$I_4 = 5 \text{ A} \quad \dots\dots\dots (4)$$

Step 3 of 4

Substituting (3) & (4) into (2),

$$(8+j2)I_1-(4+j)I_2=j5$$

Putting (1) & (5) in matrix form,

$$\begin{bmatrix} 1-j & j \\ 8+j2 & -4-j \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -j10 \\ j5 \end{bmatrix}$$

$$\Delta = -3-j5$$

$$\Delta_1 = -5+j40$$

$$\Delta_2 = -15+j85$$

Step 4 of 4

Therefore,

$$I = I_1 - I_2$$

$$I = \frac{\Delta_1 - \Delta_2}{\Delta}$$

$$I = \frac{10-j45}{-3-j5}$$

$$\therefore \boxed{I = 7.906 \angle 43.49^\circ \text{ A}}$$