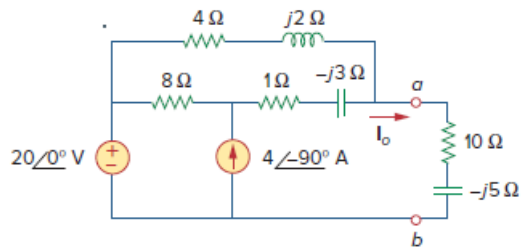


Problem

Calculate I_o in Fig. 10.30 (for Practice Prob. 10.10) using mesh analysis.

Figure 10.30:




Step-by-step solution

Step 1 of 6

Refer to Figure 10.30 in the textbook.

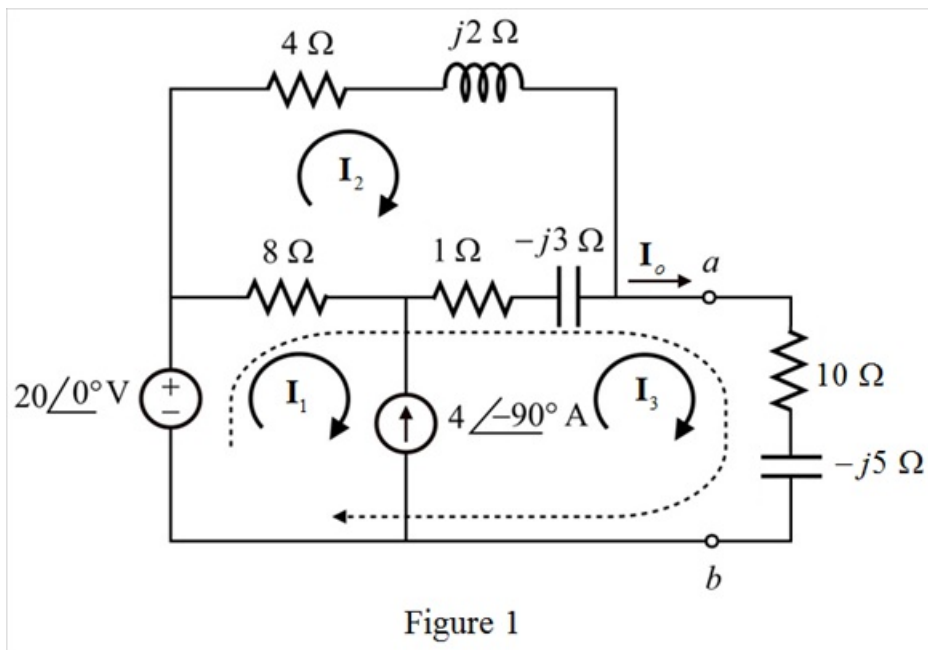Draw the modified circuit with the loop current notations.



Step 2 of 6

Apply Kirchhoff's voltage law for the mesh-2.

$$8(\mathbf{I}_2 - \mathbf{I}_1) + 4\mathbf{I}_2 + j2\mathbf{I}_2 - j3(\mathbf{I}_2 - \mathbf{I}_3) + 1(\mathbf{I}_2 - \mathbf{I}_3) = 0$$

$$8(\mathbf{I}_2 - \mathbf{I}_1) + (4 + j2)\mathbf{I}_2 + (1 - j3)(\mathbf{I}_2 - \mathbf{I}_3) = 0$$

$$-8\mathbf{I}_1 + (8 + 4 + j2 + 1 - j3)\mathbf{I}_2 - (1 - j3)\mathbf{I}_3 = 0$$

$$-8\mathbf{I}_1 + (13 - j)\mathbf{I}_2 - (1 - j3)\mathbf{I}_3 = 0 \dots\dots (1)$$

Apply Kirchhoff's voltage law for super mesh.

$$-20\angle 0^\circ + 8(\mathbf{I}_1 - \mathbf{I}_2) + 1(\mathbf{I}_3 - \mathbf{I}_2) - j3(\mathbf{I}_3 - \mathbf{I}_2) + 10\mathbf{I}_3 - j5\mathbf{I}_3 = 0$$

$$-20 + 8(\mathbf{I}_1 - \mathbf{I}_2) + (1 - j3)(\mathbf{I}_3 - \mathbf{I}_2) + (10 - j5)\mathbf{I}_3 = 0$$

$$8\mathbf{I}_1 - (8 + 1 - j3)\mathbf{I}_2 + (1 - j3 + 10 - j5)\mathbf{I}_3 = 20$$

$$8\mathbf{I}_1 - (9 - j3)\mathbf{I}_2 + (11 - j8)\mathbf{I}_3 = 20 \dots\dots (2)$$

Step 3 of 6

From the mesh-1 and mesh-3,

$$\mathbf{I}_3 - \mathbf{I}_1 = 4\angle -90^\circ$$

$$-\mathbf{I}_1 + \mathbf{I}_3 = -j4 \dots\dots (3)$$

Step 4 of 6

Solve equations (1), (2) and (3) using Cramer's rule.

$$\begin{bmatrix} -8 & (13-j) & -(1-j3) \\ 8 & -(9-j3) & (11-j8) \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 20 \\ -j4 \end{bmatrix}$$

Determine the value of Δ .

$$\begin{aligned} \Delta &= \begin{vmatrix} -8 & (13-j) & -(1-j3) \\ 8 & -(9-j3) & (11-j8) \\ -1 & 0 & 1 \end{vmatrix} \\ &= -8[-(9-j3)-0] - (13-j)[8+(11-j8)] - (1-j3)[0-(9-j3)] \\ &= 8(9-j3) + (-13+j)(19-j8) + (-1+j3)(-9+j3) \\ &= (72-j24) + (-239+j123) + (-j30) \\ \Delta &= -167 + j69 \end{aligned}$$

Step 5 of 6

Determine the value of Δ_3 .

$$\begin{aligned} \Delta_3 &= \begin{vmatrix} -8 & (13-j) & 0 \\ 8 & -(9-j3) & 20 \\ -1 & 0 & -j4 \end{vmatrix} \\ &= -8[(j4)(9-j3)-0] - (13-j)[8(-j4)+20] + 0 \\ &= -8(12+j36) + (-13+j)(20-j32) \\ &= (-96-j288) + (-228+j436) \\ \Delta_3 &= -324 + j148 \end{aligned}$$

Step 6 of 6

Determine the value of current, $\mathbf{I_o}$.

$$\mathbf{I_o = I_3}$$

$$\mathbf{I_o = \frac{\Delta_3}{\Delta}}$$

Substitute $-324 + j148$ for Δ_3 and $-167 + j69$ for Δ in the equation.

$$\mathbf{I_o = \frac{-324 + j148}{-167 + j69}}$$

$$= 1.97 - j0.0723$$

$$= 1.9713 \angle -2.10^\circ \text{ A}$$

Thus, the value of mesh current, $\mathbf{I_o}$ is $\boxed{1.9713 \angle -2.10^\circ \text{ A}}$.