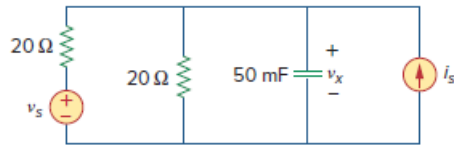


Problem

Use the superposition principle to obtain v_x in the circuit of Fig. 10.89. Let $v_s = 50 \sin 2t$ V and $i_s = 12 \cos(6t + 10^\circ)$ A.

Figure 10.89:



Step-by-step solution

Step 1 of 6

Refer to Figure 10.89 in the textbook.

The circuit operates at two different frequencies; one way to obtain a solution is to use superposition theorem, which breaks the problem into single – frequency problems.

So let,

$$v_x = v_1 + v_2 \dots\dots (1)$$

Where,

v_1 is due to the $v_s = 50 \sin(2t)$ V voltage source,

v_2 is due to the $i_s = 12 \cos(6t + 10^\circ)$ A current source.

Step 2 of 6

To find v_1 , consider the voltage source $v_s = 50 \sin(2t)$ V alone and open circuiting the current source $i_s = 12 \cos(6t + 10^\circ)$ A.

Consider the source is, $v_s = 50 \sin(2t)$ V

Convert the source into cosine form.

$$\begin{aligned} v_s &= 50 \sin(2t) \text{ V} \\ &= 50 \cos(2t - 90^\circ) \text{ V} \end{aligned}$$

Determine the capacitive reactance.

$$\begin{aligned} X_C &= \frac{1}{j\omega C} \\ &= \frac{1}{j(2)(50 \times 10^{-3})} \\ &= -j10 \, \Omega \end{aligned}$$

Re-draw the circuit diagram.

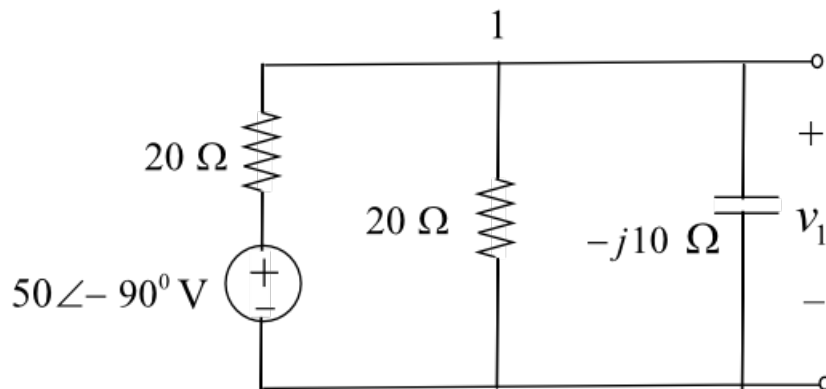


Figure 1

Step 3 of 6

Apply Kirchhoff's current law at node 1.

$$\begin{aligned} \frac{(50 \angle -90^\circ) - v_1}{20} &= \frac{v_1}{20} + \frac{v_1}{-j10} \\ (50 \angle -90^\circ) - v_1 &= v_1 + j2v_1 \\ v_1(2 + j2) &= 50 \angle -90^\circ \\ v_1 &= \frac{50 \angle -90^\circ}{2 + j2} \\ &= \frac{50 \angle -90^\circ}{2.83 \angle 45^\circ} \\ &= 17.67 \angle -135^\circ \text{ V} \end{aligned}$$

Convert the equation to time-domain form.

$$v_1 = 17.67 \cos(2t - 135^\circ) \text{ V} \dots\dots (2)$$

Step 4 of 6

To find v_2 , consider the current source $i_s = 12 \cos(6t + 10^\circ) \text{ A}$ alone and short circuiting the voltage source $v_x = 50 \sin(2t) \text{ V}$.

Determine the capacitive reactance.

$$\begin{aligned} X_C &= \frac{1}{j\omega C} \\ &= \frac{1}{j(6)(50 \times 10^{-3})} \\ &= -j3.33 \, \Omega \end{aligned}$$

Re-draw the circuit diagram.

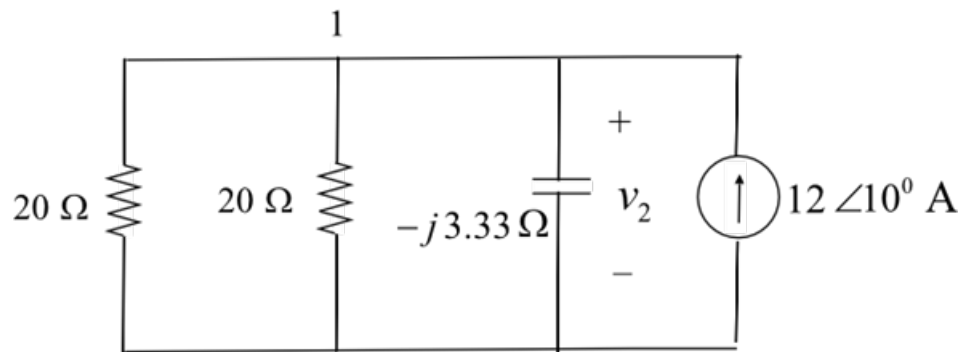


Figure 2

Step 5 of 6

Apply Kirchhoff's current law at node 1.

$$\begin{aligned} 12 \angle 10^\circ &= \frac{v_2}{-j3.33} + \frac{v_2}{20} + \frac{v_2}{20} \\ 12 \angle 10^\circ &= v_2 (0.1 + j0.3) \\ v_2 &= \frac{12 \angle 10^\circ}{0.1 + j0.3} \\ &= \frac{12 \angle 10^\circ}{0.316 \angle 71.57^\circ} \end{aligned}$$

$$v_2 = 37.95 \angle -61.57^\circ \text{ V}$$

Convert the equation to time-domain form.

$$v_2 = 37.95 \cos(6t - 61.57^\circ) \text{ V} \dots\dots (3)$$

Step 6 of 6

Substitute equation (2) and equation (3) in equation (1).

$$v_x = 17.67 \cos(2t - 135^\circ) + 37.95 \cos(6t - 61.57^\circ) \text{ V}$$

Therefore, the value of voltage v_x is,

$$\boxed{17.67 \cos(2t - 135^\circ) + 37.95 \cos(6t - 61.57^\circ) \text{ V}}.$$