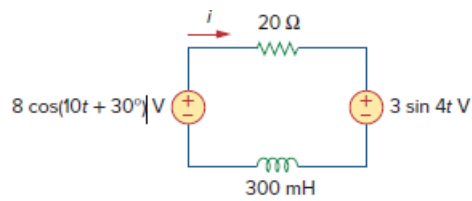


Problem

Use superposition to find $i(t)$ in the circuit of Fig. 10.90.

Figure 10.90:



Step-by-step solution

Step 1 of 7

Refer to Figure 10.90 in the textbook.

From Figure 10.90 in the textbook, the circuit operates at two different frequencies.

Consider the voltage source $8\cos(10t + 30^\circ)$ V alone and short circuiting the voltage source $3\sin(4t)$ V.

Determine the value of inductive reactance.

$$\begin{aligned} X_L &= j\omega L \\ &= j(10)(300 \times 10^{-3}) \\ &= j3 \, \Omega \end{aligned}$$

Re-draw the circuit diagram.

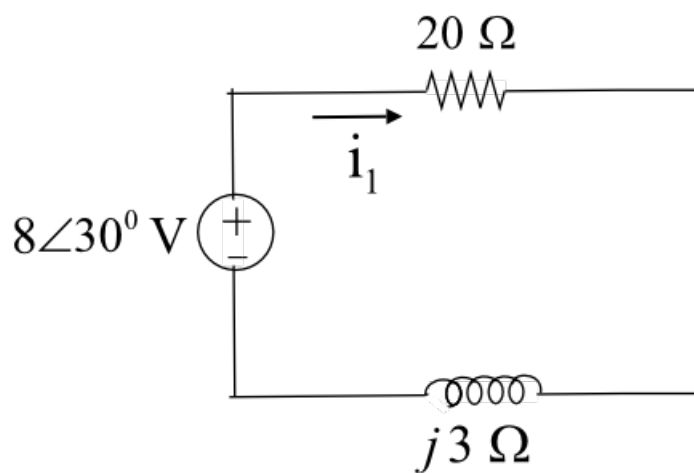


Figure 1

Step 2 of 7

Apply ohm's law to calculate the value of current, i_1 .

$$\begin{aligned} i_1 &= \frac{8\angle 30^\circ}{20 + j3} \\ &= \frac{8\angle 30^\circ}{20.22\angle 8.53^\circ} \\ &= 0.3956\angle 21.47^\circ \text{ A} \end{aligned}$$

Convert the equation to time-domain form.

$$\begin{aligned} i_1(t) &= 395.6\angle 21.47^\circ \text{ mA} \\ &= 395.6 \cos(10t + 21.47^\circ) \text{ mA} \end{aligned}$$

Step 3 of 7

Consider the voltage source $3\sin(4t)$ V alone and short circuiting the voltage source $8\cos(10t + 30^\circ)$ V.

Consider the source is, $V_s = 3\sin(4t)$ V.

Convert the source into cosine form.


$$\begin{aligned} V_s &= 3\sin(4t) \text{ V} \\ &= 3\cos(4t - 90^\circ) \text{ V} \end{aligned}$$

Determine the value of inductive reactance.

$$\begin{aligned} X_L &= j\omega L \\ &= j(4)(300 \times 10^{-3}) \\ &= j1.2 \Omega \end{aligned}$$

Re-draw the circuit diagram.

Step 4 of 7

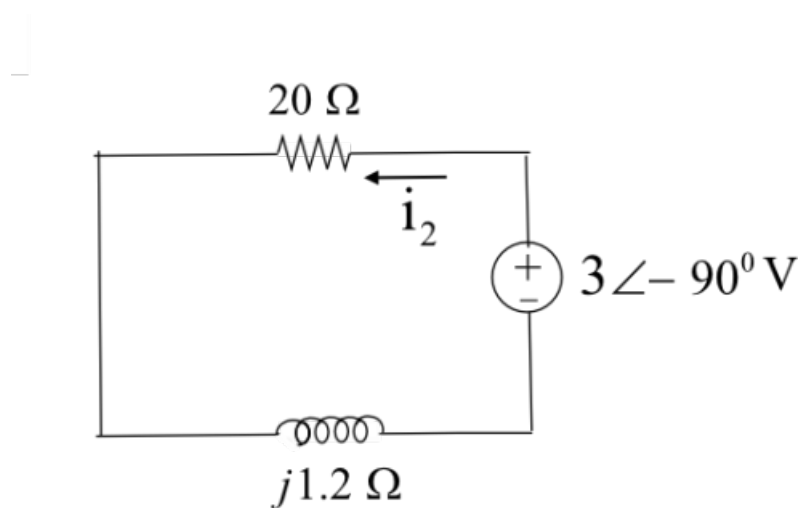

Step 5 of 7

Figure 2

Step 6 of 7

Apply ohm's law to calculate the value of current, i_2 .

$$\begin{aligned} i_2 &= \frac{3\angle -90^\circ}{20 + j1.2} \\ &= \frac{20\angle -90^\circ}{20.04\angle 3.43^\circ} \\ &= 0.1497\angle -93.43^\circ \text{ A} \end{aligned}$$

Convert the equation to time-domain form.

$$\begin{aligned} i_2(t) &= 149.7\angle -93.43^\circ \text{ mA} \\ &= 149.7 \cos(4t - 93.43^\circ) \text{ mA} \\ &= 149.7 \sin(90^\circ + 4t - 93.43^\circ) \text{ mA} \\ &= 149.7 \sin(4t - 3.43^\circ) \text{ mA} \end{aligned}$$

Step 7 of 7

Determine the value of current, $i(t)$.

$$\begin{aligned} i(t) &= i_1(t) - i_2(t) \\ &= 395.6 \cos(10t + 21.47^\circ) \text{ mA} - 149.7 \sin(4t - 3.43^\circ) \text{ mA} \\ &= 395.6 \cos(10t + 21.47^\circ) \text{ mA} + 149.7 \sin(180^\circ + 4t - 3.43^\circ) \text{ mA} \\ &= 395.6 \cos(10t + 21.47^\circ) \text{ mA} + 149.7 \sin(4t + 176.57^\circ) \text{ mA} \end{aligned}$$

Therefore, the value of current ' $i(t)$ ' is

$$\boxed{[395.6 \cos(10t + 21.47^\circ) + 149.7 \sin(4t + 176.57^\circ)] \text{ mA}}.$$