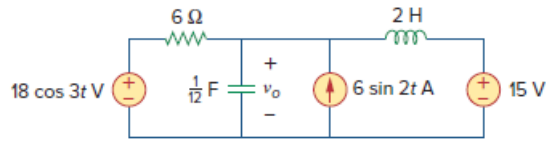


Problem

Solve for $v_o(t)$ in the circuit of Fig. 10.91 using the superposition principle.

Figure 10.91:



Step-by-step solution

Step 1 of 9

Refer to Figure 10.91 in the textbook.

The circuit is operating at three different frequencies, that is, 0 rad/s (for DC source), 2 rad/s and 3 rad/s .

Use the super position principle.

Assume that the total voltage due to three sources is,

$$v_o = v_1 + v_2 + v_3 \dots\dots (1)$$

Here,

v_1 is due to the $18 \cos(3t) \text{ V}$ voltage source,

v_2 is due to the $6 \sin 2t \text{ A}$ current source,

v_3 is due to the 15 V dc voltage source.

Step 2 of 9

Find the output voltage v_1 . Consider that the voltage source $18 \cos(3t) \text{ V}$ is acting alone and set both the sources $6 \sin 2t \text{ A}$ current source and 15 V dc voltage source to zero and transform the circuit into frequency domain.

Thus,

$$18 \cos(3t) \text{ V} = 18 \angle 0^\circ \text{ V}$$

Here, the angular frequency ω is 3 rad/s .

Determine the impedance of the inductor.

$$\begin{aligned} j\omega L &= j(3)(2) \\ &= j6 \Omega \end{aligned}$$

Determine the impedance of the capacitor.

$$\begin{aligned} \frac{1}{j\omega C} &= \frac{1}{j(3)\left(\frac{1}{12}\right)} \\ &= -j4 \Omega \end{aligned}$$

Step 3 of 9

Draw the frequency domain equivalent circuit with source $18\angle 0^\circ \text{ V}$ as shown in

Figure 1.

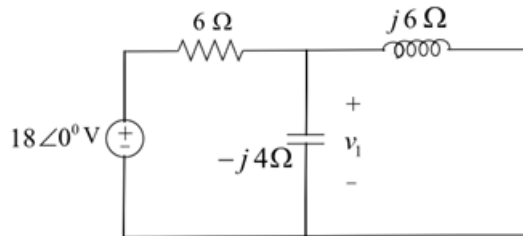


Figure 1

Step 4 of 9

Apply the Kirchhoff's current law at node, v_1 .

$$\frac{v_1 - 18\angle 0^\circ}{6} + \frac{v_1}{-j4} + \frac{v_1}{j6} = 0$$

$$v_1 \left(\frac{1}{6} + \frac{1}{-j4} + \frac{1}{j6} \right) = 3$$

$$v_1 (0.167 + j0.083) = 3$$

$$v_1 = \frac{3}{0.167 + j0.083}$$

$$= 14.4 - j7.2$$

$$= 16.099\angle -26.56^\circ \text{ V}$$

In the time domain,

$$v_1 = 16.099 \cos(3t - 26.56^\circ) \text{ V} \dots\dots (2)$$

Step 5 of 9

Find the output voltage v_2 . Consider that the current source $6\sin 2t \text{ A}$ is acting alone and set both the sources $18\cos(3t) \text{ V}$ voltage source and 15 V dc voltage source to zero and transform the circuit into frequency domain.

Thus,

$$6\sin 2t \text{ A} = 6\cos(2t - 90^\circ) \text{ A}$$

$$= 6\angle -90^\circ \text{ A}$$

Here, the angular frequency ω is 2 rad/s.

Determine the impedance of the inductor.

$$j\omega L = j(2)(2)$$

$$= j4 \Omega$$

Determine the impedance of the capacitor.

$$\frac{1}{j\omega C} = \frac{1}{j(2)\left(\frac{1}{12}\right)}$$

$$= -j6 \Omega$$

Step 6 of 9

Draw the frequency domain equivalent circuit as shown in Figure 2.

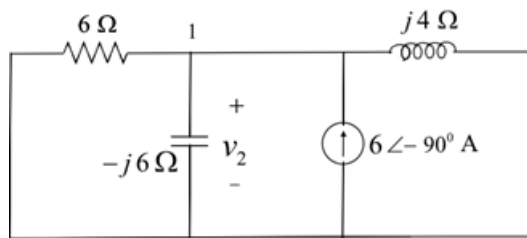


Figure 2

Step 7 of 9

Write the Kirchhoff's current law equation at node 1.

$$\begin{aligned}\frac{v_2}{6} + \frac{v_2}{-j6} + \frac{v_2}{j4} &= 6\angle -90^\circ \\ v_2(0.167 + j0.167 - j0.25) &= 6\angle -90^\circ \\ v_2(0.167 - j0.083) &= 6\angle -90^\circ \\ v_2 &= \frac{6\angle -90^\circ}{0.167 - j0.083} \\ v_2 &= \frac{6\angle -90^\circ}{0.186\angle -26.427^\circ} \\ &= 32.2\angle -63.43^\circ \text{ V}\end{aligned}$$

In the time domain,

$$v_2 = 32.2 \cos(2t - 63.43^\circ) \text{ V} \dots\dots (3)$$

Step 8 of 9

Find the output voltage v_3 . set all the sources to zero except the 15V dc source.

In the steady state condition, the capacitor acts like an open circuit and inductor acts like a short circuit.

Draw the equivalent circuit as shown in Figure 3.

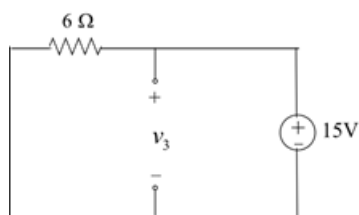


Figure 3

Step 9 of 9

From Figure 3,

$$v_3 = 15 \text{ V} \dots\dots (4)$$

Recall equation (1).

$$\begin{aligned}v_0 &= v_1 + v_2 + v_3 \\ &= 16.099 \cos(3t - 26.56^\circ) + 32.2 \cos(2t - 63.43^\circ) + 15 \text{ V}\end{aligned}$$

Therefore, the output voltage v_0 is

$$\boxed{16.099 \cos(3t - 26.56^\circ) + 32.2 \cos(2t - 63.43^\circ) + 15 \text{ V}}.$$

