

Problem

Use source transformation to find I_0 in the circuit of Prob. 10.42.

Step-by-step solution

Step 1 of 7

Given circuit is,

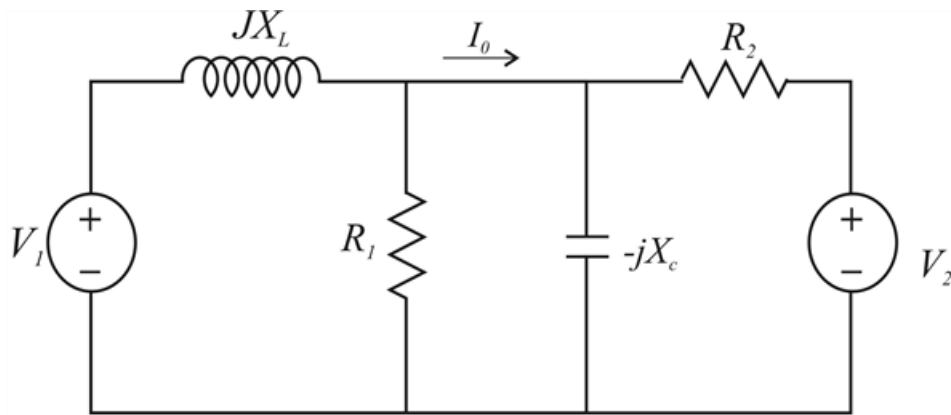


Figure-(1)

Step 2 of 7

We transform the voltage source to current source, is shown below

$$I_1 = \frac{V_1}{jX_L} \text{ and}$$

$$I_2 = \frac{V_2}{R_2}$$

Step 3 of 7

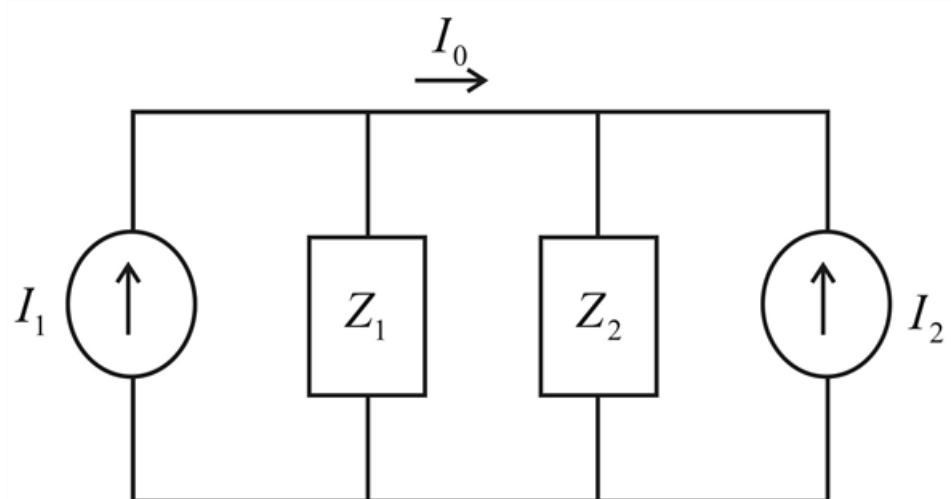


Figure-(2)

Step 4 of 7

Where,


$$Z_1 = jX_L \parallel R_1$$

$$Z_1 = \frac{jX_L R_1}{R_1 + jX_L}$$

$$Z_2 = -jX_C \parallel R_2$$

$$Z_2 = \frac{-jX_C R_2}{R_2 - jX_C}$$

We transform the current source to voltage source, is shown below.

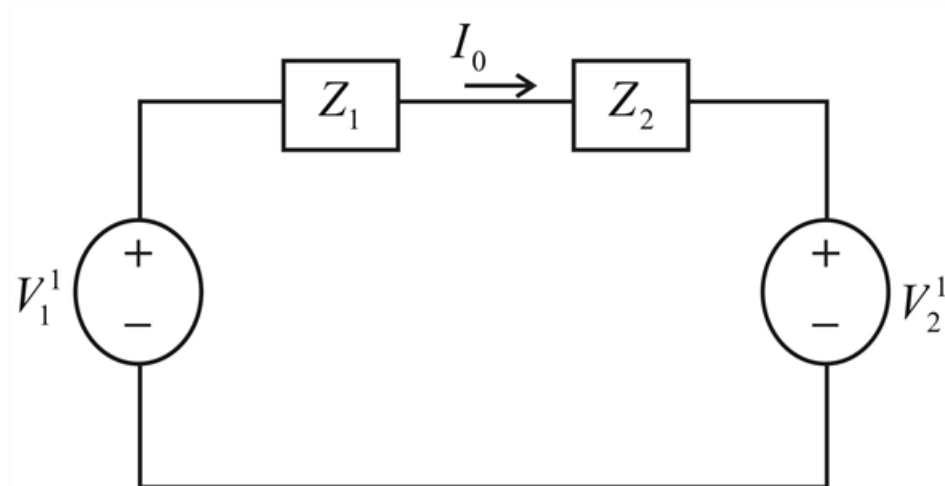Step 5 of 7**Step 6** of 7

$$V_1^1 = I_1 Z_1$$

$$V_2^1 = I_2 Z_2$$

$$V_1^1 = \frac{V_1}{jX_L} \left[\frac{jX_L R_1}{R_1 + jX_L} \right]$$

$$V_2^1 = \frac{V_2}{R_2} \left[\frac{-jX_C R_2}{R_2 - jX_C} \right]$$

Applying KVL above circuit:

$$-V_1^1 + Z_1 I_0 + Z_2 I_0 + V_2^1 = 0$$

$$I_0 (Z_1 + Z_2) = V_1^1 - V_2^1$$

$$I_0 = \frac{V_1^1 - V_2^1}{Z_1 + Z_2}$$

Step 7 of 7

$$I_0 = \frac{\frac{V_1}{jX_L} \left[\frac{jX_L R_1}{R_1 + jX_L} \right] - \frac{V_2}{R_2} \left[\frac{-jX_C R_2}{R_2 - jX_C} \right]}{\left[\frac{jX_L R_1}{R_1 + jX_C} \right] + \left[\frac{-jX_C R_2}{R_2 - jX_C} \right]}$$

$$I_0 = \frac{V_1 \left[\frac{R_1}{R_1 + jX_L} \right] - V_2 \left[\frac{-jX_C}{R_2 - jX_C} \right]}{\left[\frac{jX_L R_1}{R_1 + jX_C} \right] + \left[\frac{-jX_C R_2}{R_2 - jX_C} \right]}$$

$$I_0 = \frac{V_1 R_1 (R_2 - jX_C) + jV_2 X_C (R_1 + jX_L)}{jX_L R_1 (R_2 - jX_C) - jX_C R_2 (R_1 + jX_L)}$$

$$I_0 = \frac{(V_1 R_1 R_2 - V_2 X_L X_C) + j(V_2 R_1 X_C - V_1 R_1 X_C)}{(R_1 X_C X_L + R_2 X_C X_L) + j(X_L R_1 R_2 - X_C R_1 R_2)}$$

$$I_0 = \frac{(V_1 R_1 R_2 - V_2 X_L X_C) + jR_1 X_C (V_2 - V_1)}{X_C X_L (R_1 + R_2) + jR_1 R_2 (X_L - X_C)}$$