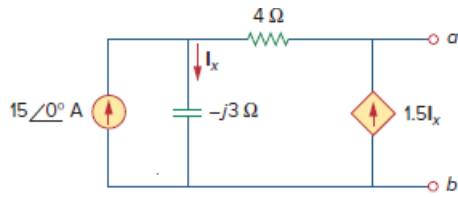


Problem

Find the Thevenin equivalent at terminals a - b of the circuit in Fig. 10.104.

Figure 10.104:



Step-by-step solution

Step 1 of 7

Refer to Figure 10.104 in the textbook.

Consider the following circuit to calculate the thevenin voltage:

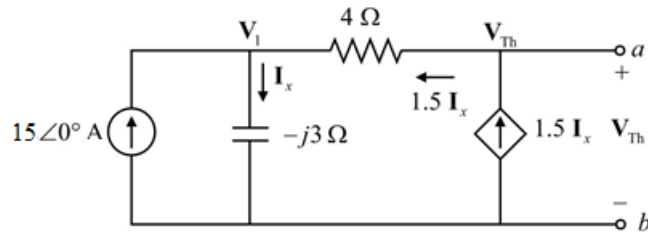


Figure 1

Step 2 of 7

Calculate the Thevenin voltage V_{Th} .

Apply Kirchhoff's current law at the node V_1 for the circuit in Figure 1.

$$-15 - 1.5I_x + I_x = 0$$

$$0.5I_x = -15$$

$$I_x = -30 \text{ A}$$

Step 3 of 7

Calculate the voltage V_1 .

$$V_1 = I_x(-j3)$$

Substitute -30 A for I_x .

$$\begin{aligned} V_1 &= (-30)(-j3) \\ &= j90 \text{ V} \end{aligned}$$

Step 4 of 7

Consider the following current for the circuit in Figure 2.

$$\frac{V_{Th} - V_1}{4} = 1.5I_x$$

$$V_{Th} - V_1 = 6I_x$$

$$V_{Th} = 6I_x + V_1$$

Substitute -30 A for I_x and $j90$ V for V_1 .

$$\begin{aligned} V_{Th} &= 6(-30) + (j90) \\ &= -180 + j90 \text{ V} \end{aligned}$$

Therefore, the Thevenin voltage V_{Th} is $-180 + j90$ V.

Step 5 of 7

Consider the following circuit to calculate the thevenin impedance:

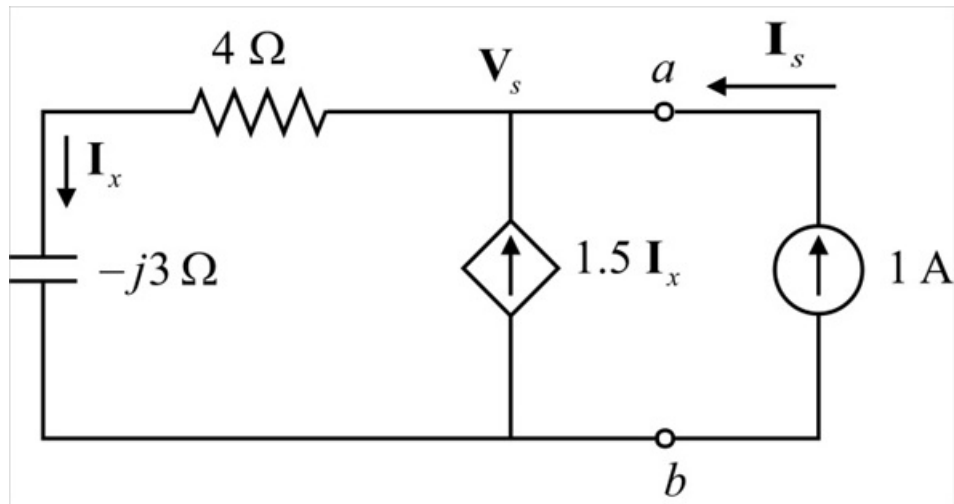


Figure 2

Step 6 of 7

Calculate the Thevenin impedance $\mathbf{Z}_{Th}$.

To calculate $\mathbf{Z}_{Th}$, we should open circuit all the independent current sources and short circuit all the independent voltage sources and consider a dummy current source $\mathbf{I}_s = 1 \text{ A}$.

Apply Kirchhoff's current law at the node $\mathbf{V}_s$ for the circuit in Figure 3.

$$\mathbf{I}_s + 1.5\mathbf{I}_x - \mathbf{I}_x = 0$$

$$0.5\mathbf{I}_x = -\mathbf{I}_s$$

Substitute 1 A for $\mathbf{I}_s$ in $0.5\mathbf{I}_x = -\mathbf{I}_s$.

$$\begin{aligned}\mathbf{I}_x &= -\frac{1}{0.5} \\ &= -2 \text{ A}\end{aligned}$$

Consider the following voltage for the circuit in Figure 3.

$$\mathbf{V}_s = (4 - j3)(\mathbf{I}_x)$$

Substitute -2 A for $\mathbf{I}_x$ in $\mathbf{V}_s = (4 - j3)(\mathbf{I}_x)$.

$$\begin{aligned}\mathbf{V}_s &= (4 - j3)(-2) \\ &= -8 + j6 \text{ V}\end{aligned}$$

Calculate the Thevenin impedance $\mathbf{Z}_{Th}$.

$$\mathbf{Z}_{Th} = \frac{\mathbf{V}_s}{\mathbf{I}_s}$$

Substitute $-8 + j6 \text{ V}$ for $\mathbf{V}_s$ and 1 A for $\mathbf{I}_s$ in $\mathbf{Z}_{Th}$.

$$\begin{aligned}\mathbf{Z}_{Th} &= \frac{-8 + j6}{1} \\ &= -8 + j6 \Omega\end{aligned}$$

Therefore, the Thevenin impedance $\mathbf{Z}_{Th}$ is $\boxed{-8 + j6 \Omega}$.

Step 7 of 7

Draw the Thevenin equivalent.

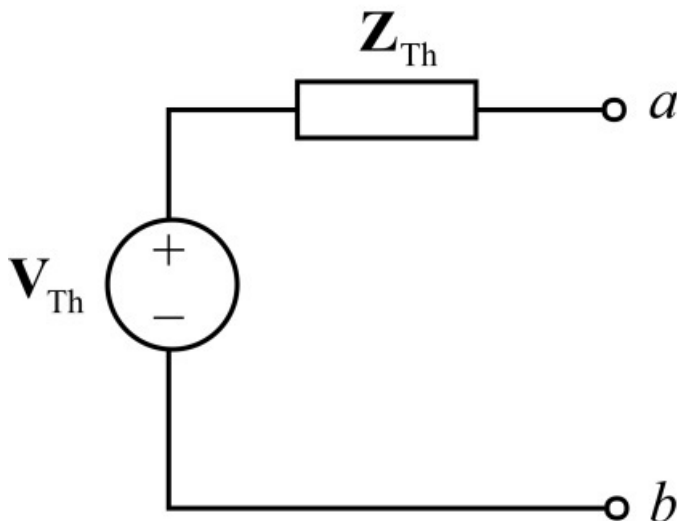


Figure 3