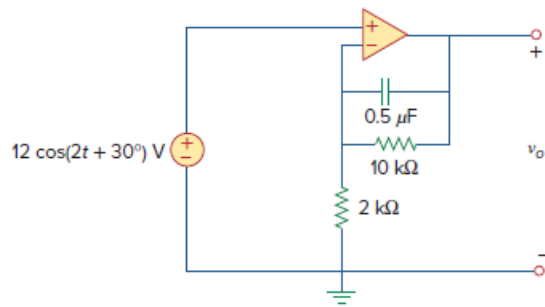


Problem

Find v_o in the op amp circuit of Fig. 10.114.

Figure 10.114:



Step-by-step solution

Step 1 of 4

Refer to Figure 10.114 in the textbook.

From the Figure 10.114, the angular frequency is, $\omega = 2 \text{ rad/s}$.

Convert the source voltage into phasor form.

$$12 \cos(2t + 30^\circ) = 12 \angle 30^\circ \text{ V}$$

Calculate the impedance of the capacitor.

$$\begin{aligned} Z_c &= \frac{1}{j\omega C} \\ &= \frac{1}{j(2)(0.5 \times 10^{-6})} \\ &= -j10^6 \Omega \end{aligned}$$

Step 2 of 4

Draw the circuit diagram in frequency domain.

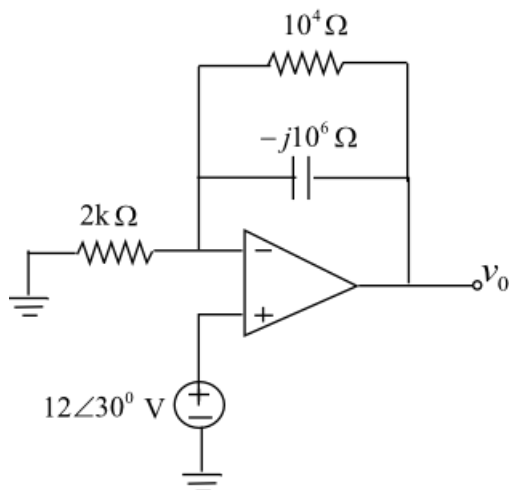


Figure 1

Step 3 of 4

From Figure 1, the feedback impedance is,

$$\begin{aligned} Z_f &= (10000) \parallel (-j10^6) \\ &= \frac{(10000)(-j10^6)}{(10000 - j10^6)} \\ &= 10000 \angle -0.057^\circ \Omega \end{aligned}$$

The input impedance is,

$$Z_i = 2000 \Omega$$

Since the circuit in Figure 1 is a non-inverting amplifier, the closed loop gain is,

$$\begin{aligned} \frac{V_o}{V_i} &= 1 + \frac{Z_f}{Z_i} \\ &= 1 + \frac{10000 \angle -0.057^\circ}{2000} \\ &= 1 + 5 \angle -0.057^\circ \\ \frac{V_o}{V_i} &= 6 \angle -0.047^\circ \dots\dots (1) \end{aligned}$$

[Comments \(1\)](#)

☐

Anonymous

why is 1 + ?

Step 4 of 4

From Figure 1, the input voltage is,

$$V_i = 12 \angle 30^\circ \text{ V}$$

From equation (1),

$$\begin{aligned} V_o &= (6 \angle -0.047^\circ) V_i \\ &= (6 \angle -0.047^\circ)(12 \angle 30^\circ) \\ &= 72 \angle 29.95^\circ \text{ V} \end{aligned}$$

In the time domain, the value of $v_o(t)$ is $v_o(t) = 72 \cos(2t + 29.95^\circ) \text{ V}$.

Therefore, the output voltage, $v_o(t)$ of the op-amp is $72 \cos(2t + 29.95^\circ) \text{ V}$.