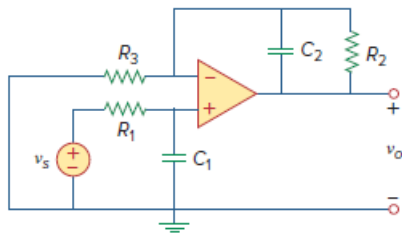


Problem

Compute the closed-loop gain V_o/V_s for the op amp circuit of Fig. 10.120.

Figure 10.120:



Step-by-step solution

Step 1 of 3

Refer to circuit diagram in figure 10.120 in the textbook.

Convert the circuit to the frequency domain.

$$C_1 \Rightarrow \frac{1}{j\omega C_1}$$

$$C_2 \Rightarrow \frac{1}{j\omega C_2}$$

Frequency domain equivalent circuit is,

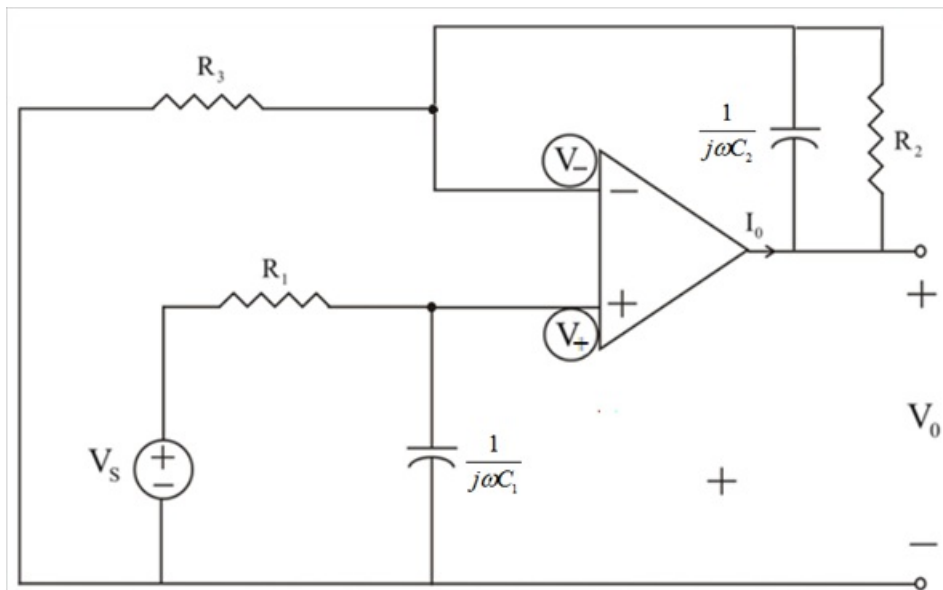


Figure 1

The voltage at non inverting terminal is equal to voltage at inverting terminal.

So, $v_+ = v_-$

Step 2 of 3

Apply Kirchhoff's current law (KCL) at non-inverting terminal.

$$\frac{v_+ - v_s}{R_1} + \frac{v_+}{j\omega C_1} = 0$$

$$\frac{v_+ - v_s}{R_1} + v_+ (j\omega C_1) = 0$$

Simplify further.

$$v_+ \left(\frac{1}{R_1} + j\omega C_1 \right) - \frac{v_s}{R_1} = 0$$

$$v_+ \left(\frac{1 + j\omega R_1 C_1}{R_1} \right) = \frac{v_s}{R_1}$$

$$v_+ (1 + j\omega R_1 C_1) = v_s$$

$$v_+ = v_s \left(\frac{1}{1 + j\omega R_1 C_1} \right)$$

$$v_- = v_s \left(\frac{1}{1 + j\omega R_1 C_1} \right) \text{ since } v_+ = v_- \dots\dots (1)$$

Step 3 of 3

Apply Kirchhoff's current law (KCL) at inverting terminal.

$$\frac{v_-}{R_3} + \frac{v_- - v_o}{j\omega C_2} + \frac{v_- - v_o}{R_2} = 0$$

$$v_- \left(\frac{1}{R_3} + j\omega C_2 + \frac{1}{R_2} \right) = v_o \left(j\omega C_2 + \frac{1}{R_2} \right)$$

$$v_- \left(\frac{R_2 + j\omega R_2 R_3 C_2 + R_3}{R_3 R_2} \right) = v_o \left(\frac{j\omega R_2 C_2 + 1}{R_2} \right)$$

$$v_- \left(\frac{R_2 + j\omega R_2 R_3 C_2 + R_3}{R_3} \right) = v_o (j\omega R_2 C_2 + 1)$$

$$v_- = v_o \left(\frac{j\omega R_2 R_3 C_2 + R_3}{R_2 + j\omega R_2 R_3 C_2 + R_3} \right)$$

From equation (1), substitute $v_s \left(\frac{1}{1 + j\omega R_1 C_1} \right)$ for v_- in the equation.

$$v_s \left(\frac{1}{1 + j\omega R_1 C_1} \right) = v_o \left(\frac{j\omega R_2 R_3 C_2 + R_3}{R_2 + j\omega R_2 R_3 C_2 + R_3} \right)$$

$$v_s \left(\frac{R_2 + j\omega R_2 R_3 C_2 + R_3}{(1 + j\omega R_1 C_1)(j\omega R_2 R_3 C_2 + R_3)} \right) = v_o$$

Rearrange the terms.

$$\frac{v_o}{v_s} = \frac{R_2 + R_3 + j\omega C_2 R_2 R_3}{(1 + j\omega R_1 C_1)(R_3 + j\omega C_2 R_2 R_3)}$$

Thus, closed loop gain $\frac{v_o}{v_s}$ of the circuit is $\boxed{\frac{R_2 + R_3 + j\omega C_2 R_2 R_3}{(1 + j\omega R_1 C_1)(R_3 + j\omega C_2 R_2 R_3)}}$.