

Problem

Solve Prob. 10.19 using *PSpice* or *MultiSim*.

Step-by-step solution

Step 1 of 2

The schematic is shown below. We insert print to print V0 in the output file. For AC sweep, we set total pts = 1, Start frequency = 0.1592 and End frequency = 0.1592. After simulation, we print out the output file which includes,

Frequency	VM(\$N_0001)	VP(\$N_0001)
$1.592 E^{-01}$	$7.684 E^{+00}$	$5.09 E^{+01}$

Which means that,

$$V_0 = 7.684 \angle 50.19^\circ \text{ V} .$$

Step 2 of 2

