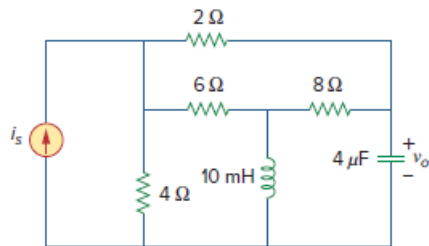


Problem

Use *PSpice* or *MultiSim* to find $v_o(t)$ in the circuit of Fig. 10.125. Let $i_s = 2 \cos(103t)$ A.

Figure 10.125:



Step-by-step solution


Step 1 of 3

The schematic is shown below:

The frequency is,

$$f = \frac{W}{2\pi} = \frac{1000}{2\pi} = 159.15$$

Step 2 of 3

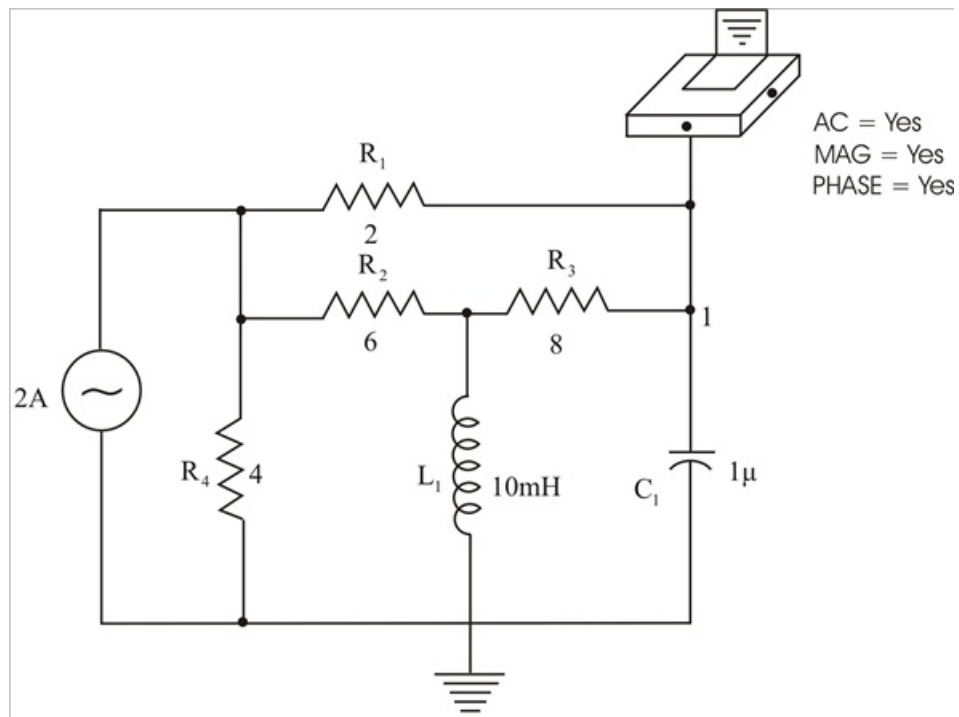

Step 3 of 3

When the circuit is saved and simulated, we obtain from the output file,

<i>Frequency</i>	<i>VM(1)</i>	<i>VP(2)</i>
$1.592 E+02$	$6.611 E+00$	$-1.592 E+02$

Thus, $V_0 = 6.611 \cos(1000t - 159.2^\circ) V$.