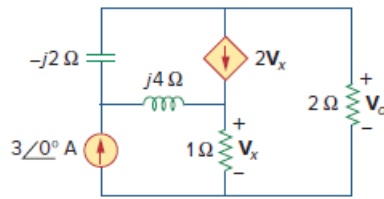


Problem

Obtain V_o in the circuit of Fig. 10.126 using *PSpice* or *MultiSim*.

Figure 10.126:



Step-by-step solution

Step 1 of 2

The schematic is shown below. We set print to print V_o in the output file. In AC sweep box, we set total pts = 1, Start frequency = 0.1592 and End frequency = 0.1592. After simulation, we obtained the output file which includes,

Frequency	$VM(\$N_0003)$	$VP(\$N_0003)$
$1.592 E^{-01}$	$1.664 E^{+00}$	$-1.464 E^{+02}$

Namely,

$$V_o = 1.664 \angle -146.4^\circ V$$

Step 2 of 2

