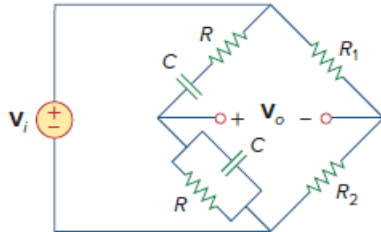


Problem

Figure 10.132 shows a Wien-bridge network. Show that the frequency at which the phase shift between the input and output signals is zero is $f = \frac{1}{2\pi} RC$, and that the necessary gain is $A_v = V_o/V_i = 3$ at that frequency.

Figure 10.132:



Step-by-step solution

Step 1 of 9

Refer to Figure 10.132 in the textbook.

The following is the impedances of the bridge network.

$$\begin{aligned} Z_3 &= R + \frac{1}{j\omega C} \\ &= \frac{1 + j\omega RC}{j\omega C} \\ Z_4 &= R \parallel \frac{1}{j\omega C} \\ &= \frac{R}{1 + j\omega RC} \end{aligned}$$

Step 2 of 9

Consider the circuit as shown in Figure 1.

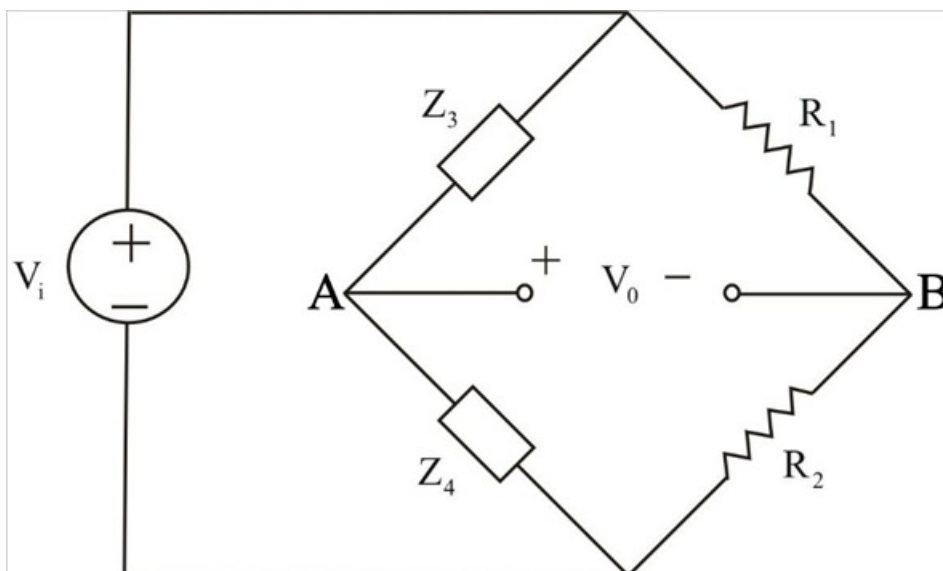


Figure 1

Step 4 of 9

Let V_A , and V_B be the voltage at point A, and B.

Determine the voltage at point A, V_A .

Apply voltage division rule in Figure 1.

$$V_A = \frac{Z_4}{Z_3 + Z_4} V_i$$

Determine the voltage at point B, V_B .

Apply voltage division rule in Figure 1.

$$V_B = \frac{R_2}{R_1 + R_2} V_i$$

Step 5 of 9

Determine the voltage V_o .

$$V_o = V_A - V_B$$

Substitute $\frac{Z_4}{Z_3 + Z_4} V_i$ for V_A , and $\frac{R_2}{R_1 + R_2} V_i$ for V_B .

$$V_o = \left(\frac{Z_4}{Z_3 + Z_4} V_i \right) - \left(\frac{R_2}{R_1 + R_2} V_i \right)$$

$$V_o = \left(\frac{Z_4}{Z_3 + Z_4} - \frac{R_2}{R_1 + R_2} \right) V_i$$

$$\frac{V_o}{V_i} = \left(\frac{Z_4}{Z_3 + Z_4} - \frac{R_2}{R_1 + R_2} \right)$$

Step 6 of 9

Substitute $\frac{1 + j\omega RC}{j\omega C}$ for Z_3 , and $\frac{R}{1 + j\omega RC}$ for Z_4 .

$$\frac{V_o}{V_i} = \frac{\left(\frac{R}{1 + j\omega RC} \right)}{\left(\frac{1 + j\omega RC}{j\omega C} \right) + \left(\frac{R}{1 + j\omega RC} \right)} - \left(\frac{R_2}{R_1 + R_2} \right)$$

$$= \frac{j\omega RC}{(1 + j\omega RC)^2 + j\omega RC} - \frac{R_2}{R_1 + R_2}$$

$$\frac{V_o}{V_i} = \frac{j\omega RC}{1 - \omega^2 R^2 C^2 + j3\omega RC} - \frac{R_2}{R_1 + R_2} \dots\dots (1)$$

Step 7 of 9

For zero phase shift between the input V_i , and output V_o , then $\frac{V_o}{V_i}$ must be purely real.

$\frac{V_o}{V_i}$ will be purely real if $(1 - \omega^2 R^2 C^2 = 0)$ in equation (1).

$$1 - \omega^2 R^2 C^2 = 0$$

$$\omega^2 R^2 C^2 = 1$$

$$\omega = \frac{1}{RC}$$

Substitute $2\pi f$ for ω .

$$2\pi f = \frac{1}{RC}$$

$$f = \frac{1}{2\pi RC}$$

Step 8 of 9

Hence, the frequency at which the phase shift between the input and output signals is zero is

$$f = \frac{1}{2\pi RC}.$$

Step 9 of 9

Determine the voltage gain A_v at frequency $f = \frac{1}{2\pi RC}$.

$$A_v = \frac{V_o}{V_i}$$

Substitute $\frac{j\omega RC}{1 - \omega^2 R^2 C^2 + j3\omega RC}$ for $\frac{V_o}{V_i}$.

$$A_v = \frac{j\omega RC}{1 - \omega^2 R^2 C^2 + j3\omega RC}$$

Substitute 0 for $(1 - \omega^2 R^2 C^2)$.

$$\begin{aligned} A_v &= \frac{j\omega RC}{j3\omega RC} \\ &= \frac{1}{3} \end{aligned}$$

Therefore, the voltage gain A_v , at the frequency f , is $\frac{1}{3}$.