

## Problem

Design a Colpitts oscillator that will operate at 50 kHz.

## Step-by-step solution

## Step 1 of 7

Consider the following data:

The operating frequency  $f_o$  is 50 kHz

The following are the conditions to design a Colpitts oscillator.

$$R_l \gg X_{C_2}$$

Assume the following data:

The values of the capacitors  $C_1$  and  $C_2$  are 20 nF.

## Step 2 of 7

Calculate the capacitance  $C_T$ .

$$C_T = \frac{C_1 C_2}{C_1 + C_2}$$

Substitute 20 nF for  $C_1$  and  $C_2$  in  $C_T = \frac{C_1 C_2}{C_1 + C_2}$

$$\begin{aligned} C_T &= \frac{(20)(20)}{20 + 20} \\ &= 10 \text{ nF} \end{aligned}$$

## Step 3 of 7

Calculate the value of the inductor  $L$ :

$$f_o = \frac{1}{2\pi\sqrt{LC_T}}$$

$$LC_T = \frac{1}{(2\pi f_o)^2}$$

$$L = \frac{1}{C_T (2\pi f_o)^2}$$

## Step 4 of 7

Substitute  $10\text{ nF}$  for  $C_T$  and  $50\text{ kHz}$  for  $f_o$  in  $L = \frac{1}{C_T (2\pi f_o)^2}$

$$\begin{aligned} L &= \frac{1}{(10 \times 10^{-9}) [2\pi (50 \times 10^3)]^2} \\ &= \frac{1}{(10 \times 10^{-9}) (98.7 \times 10^9)} \\ &= 1.013 \times 10^{-3} \\ &= 1.013\text{ mH} \end{aligned}$$

Therefore, the value of the inductor  $L$  is  $1.013\text{ mH}$ .

#### Step 5 of 7

Calculate  $X_{C_2}$

$$\begin{aligned} X_{C_2} &= \frac{1}{\omega_o C_2} \\ &= \frac{1}{2\pi f_o C_2} \end{aligned}$$

Substitute  $20\text{ nF}$  for  $C_2$  and  $50\text{ kHz}$  for  $f_o$  in  $X_{C_2} = \frac{1}{2\pi f_o C_2}$

$$\begin{aligned} X_{C_2} &= \frac{1}{2\pi (50 \times 10^3) (20 \times 10^{-9})} \\ &= 159.2\ \Omega \end{aligned}$$

#### Step 6 of 7

The value of  $R_i$  should be greater than  $X_{C_2}$  i.e.  $R_i \gg X_{C_2}$ .

Consider the value of  $R_i$  is  $20\text{ k}\Omega$

For better gain the value of the resistor  $R_f$  should be greater than or equal to  $R_i$ .

Consider the value of  $R_f$  is  $200\text{ k}\Omega$

#### Step 7 of 7

Calculate the gain of the Colpitts oscillator.

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$$

Substitute  $20 \text{ k}\Omega$  for  $R_i$  and  $200 \text{ k}\Omega$  for  $R_f$  in  $\frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$ .

$$\begin{aligned} \frac{V_o}{V_i} &= 1 + \frac{200 \times 10^3}{20 \times 10^3} \\ &= 1 + 10 \\ &= 11 \end{aligned}$$

The gain of the Colpitts oscillator is 11.

Draw the designed Colpitts oscillator.

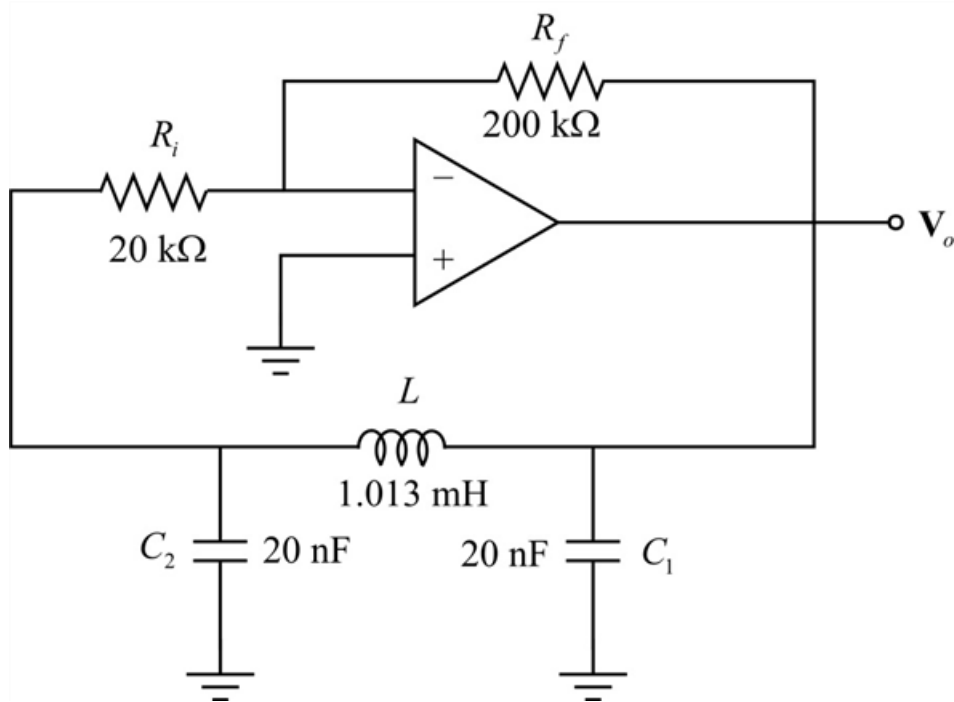


Figure 1