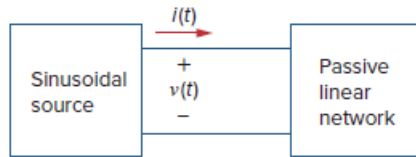


Problem

Calculate the instantaneous power and average power absorbed by the passive linear network of Fig. 11.1 if

$$v(t) = 330 \cos(10t + 20^\circ) \text{ V} \quad \text{and} \quad i(t) = 33 \sin(10t + 60^\circ) \text{ A}$$

Figure 11.1: Sinusoidal source and passive linear circuit.



Step-by-step solution

Step 1 of 3

Refer to Figure 11.1 in the textbook for linear passive network.

Consider the following data:

The sinusoidal expression for voltage is, $v(t) = 330 \cos(10t + 20^\circ) \text{ V}$

The sinusoidal expression for current is, $i(t) = 33 \sin(10t + 60^\circ) \text{ A}$

Write the current expression in terms of standard cosine function.

$$\begin{aligned} i(t) &= 33 \sin(10t + 60^\circ) \text{ A} \\ &= 33 \cos(10t + 60^\circ - 90^\circ) \text{ A} \\ &= 33 \cos(10t - 30^\circ) \text{ A} \end{aligned}$$

Step 2 of 3

Calculate the instantaneous power p absorbed by the passive linear network.

$$\begin{aligned} p &= vi \\ &= [330 \cos(10t + 20^\circ)] [33 \sin(10t + 60^\circ)] \\ &= (330)(33) \cos(10t + 20^\circ) \sin(10t + 60^\circ) \\ &= 10890 \cos(10t + 20^\circ) \sin(10t + 60^\circ) \end{aligned}$$

Apply the following trigonometry identity to the equation.

$$\cos A \sin B = \frac{1}{2} [\sin(A + B) - \sin(A - B)]$$

The following is the instantaneous power p :

$$\begin{aligned} p &= \frac{10890}{2} [\sin(10t + 20^\circ + 10t + 60^\circ) - \sin(10t + 20^\circ - 10t - 60^\circ)] \\ &= 5445 [\sin(20t + 80^\circ) - \sin(-40^\circ)] \\ &= 5445 [\sin(20t + 80^\circ) + 0.643] \\ &= 3.5 + 5.445 \sin(20t + 80^\circ) \text{ kW} \\ &= 3.5 + 5.445 \cos(20t + 80^\circ - 90^\circ) \text{ kW} \\ &= 3.5 + 5.445 \cos(20t - 10^\circ) \text{ kW} \end{aligned}$$

Therefore, the value instantaneous power p absorbed by the passive linear network is

$$\boxed{3.5 + 5.445 \cos(20t - 10^\circ) \text{ kW}}.$$

Write the expression for voltage.

$$v(t) = V_m \cos(\omega t + \theta_v) \text{ V}$$

$$v(t) = 330 \cos(10t + 20^\circ) \text{ V}$$

Write the expression for current.

$$i(t) = I_m \cos(\omega t + \theta_i) \text{ A}$$

$$i(t) = 33 \cos(10t - 30^\circ) \text{ A}$$

Calculate the average power P absorbed by the passive linear network.

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} (330)(33) \cos(20^\circ - (-30^\circ))$$

$$= \frac{1}{2} (330)(33) \cos(50^\circ)$$

$$= \frac{1}{2} (330)(33)(0.6427)$$

$$= 3499.98 \text{ W}$$

$$\approx 3.5 \text{ kW}$$

Therefore, the value of average power P absorbed by the passive linear network is 3.5 kW.