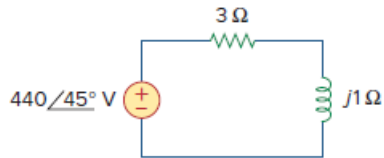


## Problem

In the circuit of Fig. 11.4, calculate the average power absorbed by the resistor and inductor. Find the average power supplied by the voltage source.

Figure 11.4:



## Step-by-step solution

## Step 1 of 3

Refer to Figure 11.4 in the text book.

Calculate the current  $\mathbf{I}$  flowing in the circuit.

$$\mathbf{I} = \frac{\mathbf{V}}{R + jX_L}$$

Substitute  $440\angle 45^\circ \text{ V}$  for  $\mathbf{V}$ ,  $3\ \Omega$  for  $R$  and  $j1\ \Omega$  for  $jX_L$ .

$$\begin{aligned}\mathbf{I} &= \frac{440\angle 45^\circ}{3 + j1} \\ &= \frac{440\angle 45^\circ}{3.162\angle 18.44^\circ} \\ &= 139.15\angle 26.56^\circ \text{ A}\end{aligned}$$

Therefore, the value of the current  $\mathbf{I}$  flowing in the circuit is,  $139.15\angle 26.56^\circ \text{ A}$ .

## Step 2 of 3

Calculate the average power  $P_R$  absorbed by the resistor.

$$P_R = \frac{1}{2} |\mathbf{I}|^2 R$$

Substitute  $139.15 \text{ A}$  for  $|\mathbf{I}|$  and  $3\ \Omega$  for  $R$ .

$$\begin{aligned}P_R &= \frac{1}{2} (139.15)^2 (3) \\ &= (19.36 \text{ k})(1.5) \\ &= 29.04 \text{ kW}\end{aligned}$$

Therefore, the value of the power  $P_R$  absorbed by the resistor is,  $29.04 \text{ kW}$ .

The value of the average power absorbed by the inductor is,  $0 \text{ W}$ .

## Step 3 of 3

Calculate the value of the average power  $P$  delivered by the voltage source.

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Substitute 139.15 A for  $I_m$ , 440 V for  $V_m$ ,  $45^\circ$  for  $\theta_v$  and  $26.56^\circ$  for  $\theta_i$ .

$$\begin{aligned} P &= \frac{1}{2} (440)(139.15) \cos(45^\circ - 26.56^\circ) \\ &= (30.61 \text{ k}) \cos(18.44^\circ) \\ &= (30.61 \text{ k})(0.9487) \\ &= 29.04 \text{ kW} \end{aligned}$$

Therefore, the value of the average power  $P$  delivered by the voltage source is, 29.04 kW