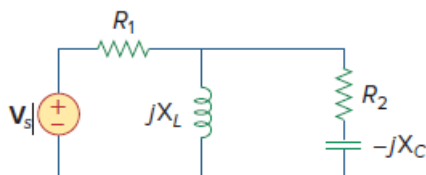


Problem

Using Fig. 11.36, design a problem to help other students better understand instantaneous and average power.

Figure 11.36:



Step-by-step solution

Step 1 of 4

Refer to Figure 11.36 in the textbook for the actual circuit.

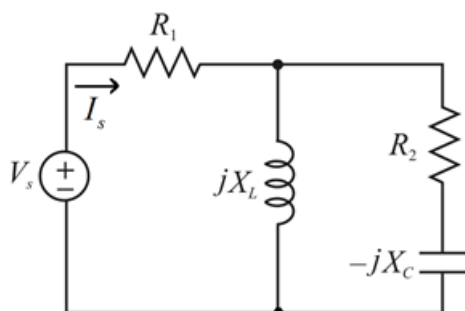


Figure 1

Step 2 of 4

Assume $v_s(t) = V_s \cos \omega t$ V

Determine the total impedance of the circuit.

R_2 , $-jX_C$ are in series and in parallel with jX_L that is in series with R_1 .

$$\begin{aligned}
 Z &= \left[(R_2 - jX_C) \parallel jX_L \right] + R_1 \\
 &= \left[\frac{(R_2 - jX_C)(jX_L)}{(R_2 - jX_C) + jX_L} \right] + R_1 \\
 &= \left[\frac{X_C X_L + jR_2 X_L}{R_2 + j(X_L - X_C)} \right] + R_1 \\
 &= \left[\frac{X_C X_L + jR_2 X_L + R_1 R_2 + jR_1 (X_L - X_C)}{R_2 + j(X_L - X_C)} \right] \\
 Z &= \left[\frac{(R_1 R_2 + X_C X_L) + j((R_2 + R_1) X_L - R_1 X_C)}{R_2 + j(X_L - X_C)} \right]
 \end{aligned}$$

Step 3 of 4

Recall the ohm's law,

$$R = \frac{V}{I}$$

Source current $I_s = \frac{V_s}{Z}$

$$I_s = \frac{V_s}{\left[\frac{(R_1 R_2 + X_C X_L) + j((R_2 + R_1)X_L - R_1 X_C)}{R_2 + j(X_L - X_C)} \right]}$$

$$= \frac{R_2 + j(X_L - X_C)}{(R_1 R_2 + X_C X_L) + j((R_2 + R_1)X_L - R_1 X_C)} V_s$$

$$I_s = \frac{\sqrt{R_2^2 + (X_L - X_C)^2} \angle \left(\tan^{-1} \left(\frac{X_L - X_C}{R_2} \right) \right)}{\sqrt{(R_1 R_2 + X_C X_L)^2 + ((R_2 + R_1)X_L - R_1 X_C)^2} \angle \left(\tan^{-1} \left(\frac{(R_2 + R_1)X_L - R_1 X_C}{R_1 R_2 + X_C X_L} \right) \right)} V_s$$

$$I_s = V_s \sqrt{\frac{R_2^2 + (X_L - X_C)^2}{(R_1 R_2 + X_C X_L)^2 + ((R_2 + R_1)X_L - R_1 X_C)^2}} \angle \left(\tan^{-1} \left(\frac{X_L - X_C}{R_2} \right) - \tan^{-1} \left(\frac{(R_2 + R_1)X_L - R_1 X_C}{R_1 R_2 + X_C X_L} \right) \right)$$

$$i_s(t) = K \cos \left[\omega t + \left(\tan^{-1} \left(\frac{X_L - X_C}{R_2} \right) - \tan^{-1} \left(\frac{(R_2 + R_1)X_L - R_1 X_C}{R_1 R_2 + X_C X_L} \right) \right) \right]$$

Here, $K = V_s \sqrt{\frac{R_2^2 + (X_L - X_C)^2}{(R_1 R_2 + X_C X_L)^2 + ((R_2 + R_1)X_L - R_1 X_C)^2}}$

Step 4 of 4

The average power delivered by the source is,

$$P = \frac{1}{2} V_s I_s \cos(\theta_v - \theta_i)$$

$$P = \frac{V_s^2}{2} \sqrt{\frac{R_2^2 + (X_L - X_C)^2}{(R_1 R_2 + X_C X_L)^2 + ((R_2 + R_1) X_L - R_1 X_C)^2}} \cos \left(\begin{matrix} 0 - \tan^{-1} \left(\frac{X_L - X_C}{R_2} \right) \\ + \tan^{-1} \left(\frac{(R_2 + R_1) X_L - R_1 X_C}{R_1 R_2 + X_C X_L} \right) \end{matrix} \right)$$

Hence, the average power delivered by the source is,

$$P = \frac{V_s^2}{2} \sqrt{\frac{R_2^2 + (X_L - X_C)^2}{(R_1 R_2 + X_C X_L)^2 + ((R_2 + R_1) X_L - R_1 X_C)^2}} \cos \left(\begin{matrix} \tan^{-1} \left(\frac{(R_2 + R_1) X_L - R_1 X_C}{R_1 R_2 + X_C X_L} \right) \\ - \tan^{-1} \left(\frac{X_L - X_C}{R_2} \right) \end{matrix} \right) \text{ W}$$

The instantaneous power is given by,

$$p(t) = v_s(t) i_s(t)$$

$$p(t) = (V_s \cos \omega t) \left(K \cos \left[\omega t + \begin{matrix} \tan^{-1} \left(\frac{X_L - X_C}{R_2} \right) \\ - \tan^{-1} \left(\frac{(R_2 + R_1) X_L - R_1 X_C}{R_1 R_2 + X_C X_L} \right) \end{matrix} \right] \right)$$

$$p(t) = K V_s \cos \omega t \cdot \cos \left[\omega t + \begin{matrix} \tan^{-1} \left(\frac{X_L - X_C}{R_2} \right) \\ - \tan^{-1} \left(\frac{(R_2 + R_1) X_L - R_1 X_C}{R_1 R_2 + X_C X_L} \right) \end{matrix} \right] \text{ W}$$

$$\text{Here, } K = V_s \sqrt{\frac{R_2^2 + (X_L - X_C)^2}{(R_1 R_2 + X_C X_L)^2 + ((R_2 + R_1) X_L - R_1 X_C)^2}}$$