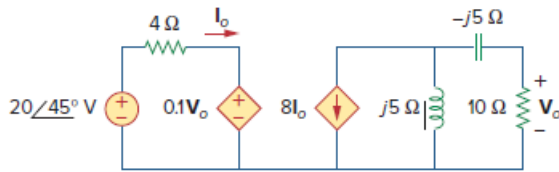


## Problem

Given the circuit of Fig. 11.39, find the average power absorbed by the 10- $\Omega$  resistor.

**Figure 11.39:**



## Step-by-step solution

## Step 1 of 3

Refer to Figure 11.39 in the text book.

Consider the expression for the output voltage  $V_o$  using current division rule.

$$\begin{aligned} V_o &= -8I_o \left( \frac{j5}{j5 - j5 + 10} \right) (10) \\ &= -I_o \left( \frac{j40}{10} \right) (10) \\ &= I_o (40 \angle -90^\circ) \end{aligned}$$

Solve for  $I_o$ .

$$\begin{aligned} I_o &= \frac{V_o}{40 \angle -90^\circ} \\ &= (0.025 \angle 90^\circ) V_o \end{aligned}$$

Therefore, the expression for the current  $I_o$  is,  $(0.025 \angle 90^\circ) V_o$ .

## Step 2 of 3

Consider the expression for the current  $I_o$ .

$$I_o = \frac{20 \angle 45^\circ - 0.1V_o}{4}$$

Substitute  $(0.025 \angle 90^\circ) V_o$  for  $I_o$ .

$$(0.025 \angle 90^\circ) V_o = \frac{20 \angle 45^\circ - 0.1V_o}{4}$$

$$(0.1 \angle 90^\circ) V_o = 20 \angle 45^\circ - 0.1V_o$$

$$(0.1 \angle 90^\circ) V_o + 0.1V_o = 20 \angle 45^\circ$$

$$(0.1 \angle 90^\circ + 0.1) V_o = 20 \angle 45^\circ$$

$$(0.1414 \angle 45^\circ) V_o = 20 \angle 45^\circ$$

$$V_o = \frac{20 \angle 45^\circ}{0.1414 \angle 45^\circ}$$

$$V_o = 141.44 \text{ V}$$

Therefore, the value of the output voltage  $V_o$  is, 141.44 V.

## Step 3 of 3

Calculate the value of the average power absorbed by the  $10\ \Omega$  resistance.

$$P = \frac{V_o^2}{2R}$$

Substitute  $141.44\text{ V}$  for  $V_o$  and  $10\ \Omega$  for  $R$ .

$$\begin{aligned} P &= \frac{(141.44)^2}{2(10)} \\ &= \frac{20\text{ k}}{20} \\ &= 1\text{ kW} \end{aligned}$$

Therefore, the value of the average power absorbed by the resistance  $P$  is, 1 kW.