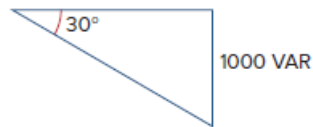


Problem

For the power triangle in Fig. 11.34(b), the apparent power is:

- (a) 2000 VA
- (b) 1000 VAR
- (c) 866 VAR
- (d) 500 VAR

Figure 11.34(b):



Step-by-step solution

Step 1 of 2

Refer to Figure 11.34 (b) in the textbook.

Draw the circuit as shown in Figure 1.

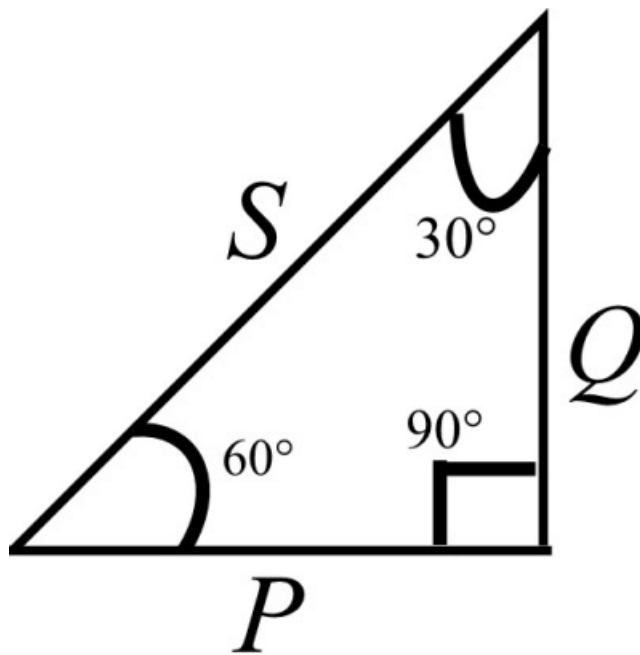


Figure 1

Step 2 of 2

Compare Figure 1 with Figure 11.34 (b).

By comparing,

The real power is $P = 1000 \text{ VAR}$.

Determine the apparent power.

Write the relation between real power and apparent power.

$$P = S \cos(\theta_v - \theta_i)$$

Replace 1000 VAR for P , 60° for $\theta_v - \theta_i$ in equation.

$$1000 = S \cos(60)$$

$$S = \frac{1000}{\cos(60)}$$

$$S = \frac{1000}{0.5}$$

$$S = 2000 \text{ VA}$$

Therefore, the apparent power is 2000 VA .

Therefore, the correct option is (a) .