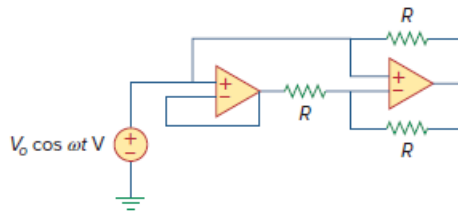


Problem

In the op amp circuit in Fig. 11.42, find the total average power absorbed by the resistors.

Figure 11.42:



Step-by-step solution

Step 1 of 1

No current flows through each of the resistor.

Hence for each resistor,

$$P = 0 \text{ W.}$$