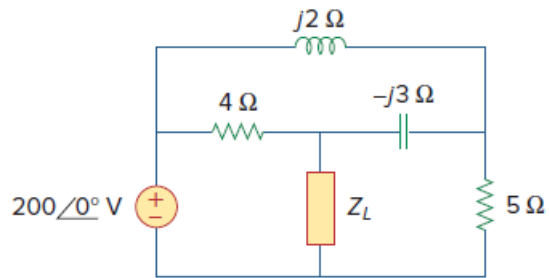


Problem

For the circuit shown in Fig. 11.44, determine the load impedance $\mathbf{Z_L}$ for maximum power transfer (to $\mathbf{Z_L}$). Calculate the maximum power absorbed by the load.

Figure 11.44:



Step-by-step solution

Step 1 of 13

Refer to circuit diagram in Figure 11.44 in the text book.

Deactivate the sources and redraw the circuit diagram as shown in Figure 1 to calculate the Thevenin's impedance.

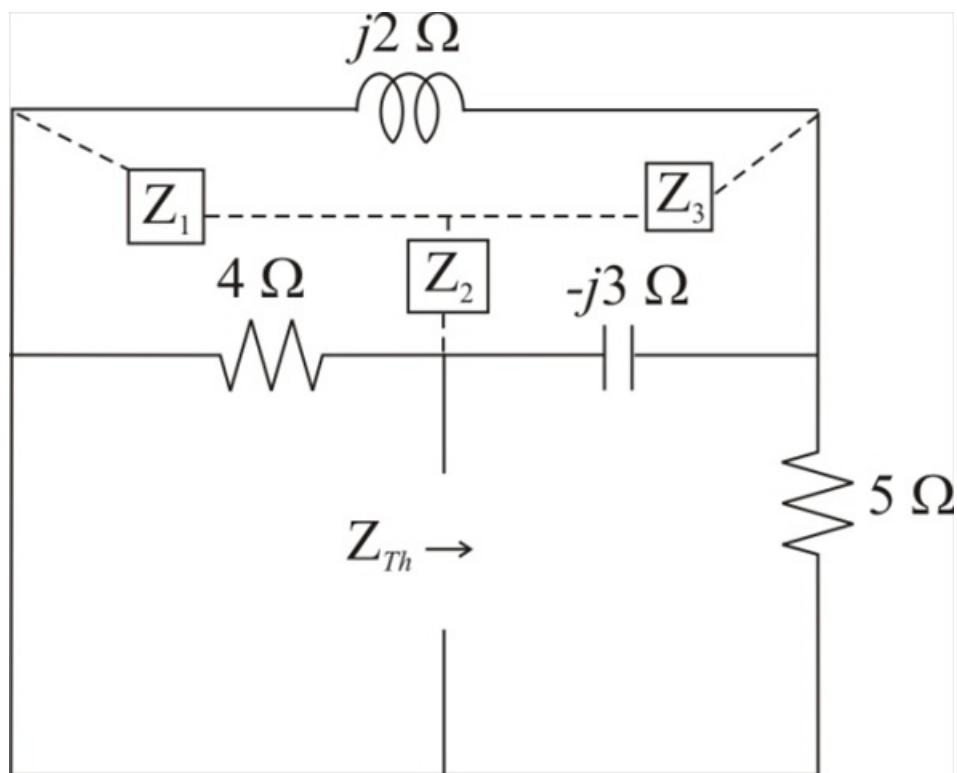


Figure 1

Step 2 of 13

Convert the delta connected to wye connection.

Calculate the value of the impedance Z_1 .

$$\begin{aligned} Z_1 &= \frac{(4)(j2)}{4 + j2 - j3} \\ &= \frac{j8}{4 - j1} \\ &= -0.471 + j1.882 \, \Omega \end{aligned}$$

Therefore, the value of the impedance Z_1 is $-0.471 + j1.882 \, \Omega$.

Step 3 of 13

Calculate the value of the impedance Z_2 .

$$\begin{aligned} Z_2 &= \frac{(4)(-j3)}{4 + j2 - j3} \\ &= \frac{-j12}{4 - j1} \\ &= 0.706 - j2.823 \, \Omega \end{aligned}$$

Therefore, the value of the impedance Z_2 is $0.706 - j2.823 \, \Omega$.

Step 4 of 13

Calculate the value of the impedance Z_3 .

$$\begin{aligned} Z_3 &= \frac{(j2)(-j3)}{4 + j2 - j3} \\ &= \frac{6}{4 - j1} \\ &= 1.412 + j0.353 \, \Omega \end{aligned}$$

Therefore, the value of the impedance Z_3 is $1.412 + j0.353 \, \Omega$.

Step 5 of 13

Redraw the circuit diagram as shown in Figure 1.

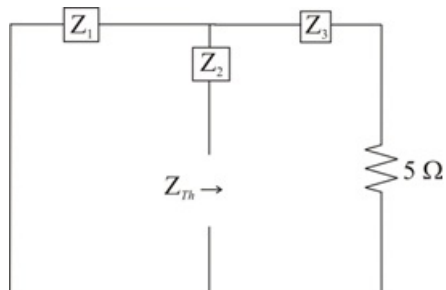


Figure 2

Step 6 of 13

Calculate the value of the Thevenin's impedance Z_{Th} .

$$Z_{Th} = Z_2 + [Z_1 \parallel (Z_3 + 5)]$$

Substitute $1.412 + j0.353 \Omega$ for Z_3 , $0.706 - j2.823 \Omega$ for Z_2 and $-0.471 + j1.882 \Omega$ for Z_1 .

$$\begin{aligned} Z_{Th} &= 0.706 - j2.823 + [(-0.471 + j1.882) \parallel (1.412 + j0.353 + 5)] \\ &= 0.706 - j2.823 + [(-0.471 + j1.882) \parallel (6.412 + j0.353)] \\ &= 0.706 - j2.823 + \frac{(-0.471 + j1.882)(6.412 + j0.353)}{(-0.471 + j1.882) + (6.412 + j0.353)} \\ &= 0.706 - j2.823 + 0.117 + j1.96 \\ &= 0.823 - j0.864 \Omega \end{aligned}$$

Therefore, the value of the Thevenin's impedance Z_{Th} is $0.823 - j0.864 \Omega$.

The value of the Thevenin's resistance R_{Th} is 0.823Ω .

Step 7 of 13

Calculate the value of the load impedance Z_L .

$$Z_L = Z_{Th}^*$$

Substitute $0.823 - j0.864 \Omega$ for Z_{Th} .

$$\begin{aligned} Z_L &= (0.823 - j0.864)^* \\ &= 0.823 + j0.864 \Omega \end{aligned}$$

Therefore, the required value of the load impedance Z_L is $0.823 + j0.864 \Omega$.

Step 8 of 13

Consider the circuit diagram shown in Figure 1 to calculate the value of the Thevenin's voltage.

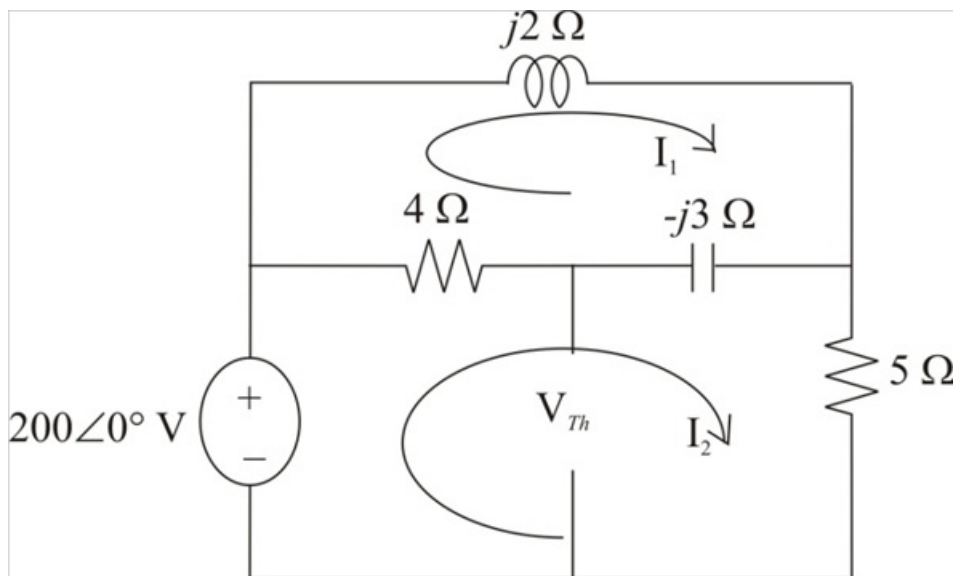


Figure 2

Step 9 of 13

Apply Kirchhoff's voltage law in Loop-1.

$$\mathbf{I}_1(j2) + (\mathbf{I}_1 - \mathbf{I}_2)(4 - j3) = 0$$

$$\mathbf{I}_1(j2 + 4 - j3) - \mathbf{I}_2(4 - j3) = 0$$

$$\mathbf{I}_1(4 - j1) = \mathbf{I}_2(4 - j3)$$

$$\mathbf{I}_1 = \left(\frac{4 - j3}{4 - j1} \right) \mathbf{I}_2 \dots\dots (1)$$

Therefore, the expression for the current $\mathbf{I}_1$ is $\mathbf{I}_2 \left(\frac{4 - j3}{4 - j1} \right)$.

Step 10 of 13

Apply Kirchhoff's voltage law in Loop-2.

$$-200\angle 0^\circ + (\mathbf{I}_2 - \mathbf{I}_1)(4 - j3) + \mathbf{I}_2(5) = 0$$

$$(\mathbf{I}_2)(4 - j3 + 5) - \mathbf{I}_1(4 - j3) = 200\angle 0^\circ$$

$$(\mathbf{I}_2)(9 - j3) - \mathbf{I}_1(4 - j3) = 200\angle 0^\circ$$

Substitute $\left(\frac{4 - j3}{4 - j1} \right) \mathbf{I}_2$ for $\mathbf{I}_1$.

$$(9 - j3)\mathbf{I}_2 - (4 - j3)\left(\frac{4 - j3}{4 - j1} \right)\mathbf{I}_2 = 200\angle 0^\circ$$

$$(9 - j3)\mathbf{I}_2 - (3.058 - j5.235)\mathbf{I}_2 = 200\angle 0^\circ$$

$$(5.94 + j2.235)\mathbf{I}_2 = 200\angle 0^\circ$$

$$\begin{aligned} \mathbf{I}_2 &= \frac{200\angle 0^\circ}{5.94 + j2.235} \\ &= 31.51\angle -20.62^\circ \text{ A} \end{aligned}$$

Therefore, the value of the current $\mathbf{I}_2$ is $31.51\angle -20.62^\circ \text{ A}$.

Step 11 of 13

Recall equation (1).

$$\mathbf{I}_1 = \left(\frac{4 - j3}{4 - j1} \right) \mathbf{I}_2$$

Substitute $31.51\angle -20.62^\circ \text{ A}$ for $\mathbf{I}_2$.

$$\begin{aligned} \mathbf{I}_1 &= \left(\frac{4 - j3}{4 - j1} \right) (31.51\angle -20.62^\circ \text{ A}) \\ &= (1.213\angle -22.83^\circ) (31.51\angle -20.62^\circ \text{ A}) \\ &= 38.21\angle -43.45^\circ \text{ A} \end{aligned}$$

Therefore, the value of the current $\mathbf{I}_1$ is $38.22\angle -43.45^\circ \text{ A}$.

Step 12 of 13

Calculate the value of the Thevenin's voltage.

$$\mathbf{V_{Th}} = 200\angle 0^\circ - 4(\mathbf{I_2} - \mathbf{I_1})$$

Substitute $38.21\angle -43.45^\circ$ A for $\mathbf{I_1}$ and $31.51\angle 20.62^\circ$ A for $\mathbf{I_2}$.

$$\begin{aligned}\mathbf{V_{Th}} &= 200\angle 0^\circ - (4)(31.51\angle 20.62^\circ - 38.21\angle -43.45^\circ) \\ &= 200\angle 0^\circ - (4)(15.28\angle 83.42^\circ) \\ &= 200\angle 0^\circ - 61.13\angle 83.42^\circ \\ &= 202.32\angle -17.46^\circ \text{ V}\end{aligned}$$

Therefore, the value of the Thevenin's voltage $\mathbf{V_{Th}}$ is $202.32\angle -17.46^\circ$ V.

Step 13 of 13

Calculate the value of the maximum power absorbed by the load.

$$P_{\max} = \frac{|\mathbf{V_{Th}}|^2}{8R_{\text{Th}}}$$

Substitute 0.823Ω for R_{Th} and 202.32 V for $|\mathbf{V_{Th}}|$.

$$\begin{aligned}P_{\max} &= \frac{(202.32 \text{ V})^2}{8(0.823 \Omega)} \\ &= \frac{40933.38}{6.584} \text{ W} \\ &= 6.217 \text{ kW}\end{aligned}$$

Therefore, the value of the maximum power $P_{\max}$ absorbed by load is 6.217 kW.