

Chapter 11, Problem 13P

Problem

The Thevenin impedance of a source is $\mathbf{Z}_{Th} = 120 + j60 \, \Omega$, while the peak Thevenin voltage is $\mathbf{V}_{Th} = 165 + j0 \, \text{V}$. Determine the maximum available average power from the source.

Step-by-step solution

Step 1 of 3

Consider the following data:

Thevenin's equivalent impedance, $\mathbf{Z}_{Th} = 120 + j60 \, \Omega$

Thevenin's equivalent voltage, $\mathbf{V}_{Th} = 165 + j0 \, \text{V}$

Step 2 of 3

The following is the load impedance for maximum power transfer:

$$\begin{aligned}\mathbf{Z}_L &= \mathbf{Z}_{Th}^* \\ &= 120 - j60 \, \Omega\end{aligned}$$

Calculate the maximum rms current $|\mathbf{I}_L|_{\text{rms}}$ delivered to load:

$$\begin{aligned}|\mathbf{I}_L|_{\text{rms}} &= \left(\frac{\mathbf{V}_{Th}}{2\mathbf{Z}_{Th}} \right) \left(\frac{1}{\sqrt{2}} \right) \\ &= \left(\frac{165}{2(120)} \right) \left(\frac{1}{\sqrt{2}} \right) \\ &= 0.486 \, \text{A}\end{aligned}$$

Step 3 of 3

Calculate the maximum available average power $\mathbf{P}_{\text{avg}}$ from the source:

$$\begin{aligned}\mathbf{P}_{\text{avg}} &= (|\mathbf{I}_L|_{\text{rms}})^2 \mathbf{Z}_{Th} \\ &= (0.486 \, \text{A})^2 (120 \, \Omega) \\ &= (0.486)^2 (120) \\ &= 28.359 \, \text{W}\end{aligned}$$

Therefore, the maximum power $\mathbf{P}_{\text{avg}}$ available from the load is 28.359 W.

[Comments \(1\)](#)



Anonymous

faster way is just taking $\mathbf{P}_{\text{avg}} = \mathbf{V}_{Th}^2 / (8 \cdot \mathbf{R}_{Th})$