

Problem

Two loads connected in parallel are respectively 3 kW at a pf of 0.75 leading and 6 kW at a pf of 0.95 lagging. Calculate the pf of the combined two loads. Find the complex power supplied by the source.

Step-by-step solution

Step 1 of 9

Consider the circuit diagram shown in Figure 1.

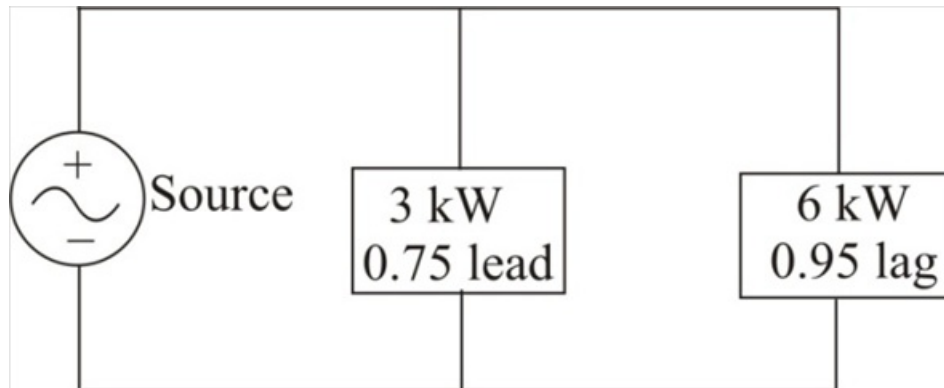


Figure 1

Step 2 of 9

Consider the expression for the reactive power Q .

$$Q = S \sin \theta$$

Substitute $\frac{P}{\cos \theta}$ for S .

$$Q = \left(\frac{P}{\cos \theta} \right) \sin \theta$$

$$= P \tan \theta$$

Therefore, the expression for the reactive power Q is, $P \tan \theta$.

Step 3 of 9

Calculate the power factor angle θ_1 at load 1.

$$\theta_1 = \cos^{-1}(0.75)$$

$$= 41.41^\circ$$

Therefore, the power factor angle θ_1 at load 1 is, 41.41° .

Step 4 of 9

Calculate the power factor angle θ_2 at load 2.

$$\begin{aligned}\theta_2 &= \cos^{-1}(0.95) \\ &= 18.2^\circ\end{aligned}$$

Therefore, the power factor angle θ_2 at load 2 is, 18.2° .

Step 5 of 9

Calculate the value of the reactive power at load 1.

$$Q_1 = P_1 \tan \theta_1$$

Substitute 3 kW for P_1 and 41.41° for θ_1 . Notice that reactive power is negative since power factor is leading.

$$\begin{aligned}Q_1 &= -(3 \text{ k}) \tan(41.41^\circ) \\ &= -(3 \text{ k})(0.8819) \\ &= -2.6457 \text{ kVAR}\end{aligned}$$

Therefore, the value of the reactive power Q_1 at load 1 is, 2.6457 kVAR .

Step 6 of 9

Calculate the value of the reactive power at load 2.

$$Q_2 = P_2 \tan \theta_2$$

Substitute 6 kW for P_2 and 18.2° for θ_2 .

$$\begin{aligned}Q_2 &= (6 \text{ k}) \tan(18.2^\circ) \\ &= (6 \text{ k})(0.3288) \\ &= 1.9728 \text{ kVAR}\end{aligned}$$

Therefore, the value of the reactive power Q_2 at load 2 is, 1.9728 kVAR .

Step 7 of 9

Calculate the value of the total complex power S_T absorbed by the two loads.

$$S_T = S_1 + S_2$$

Substitute $P_1 + jQ_1$ for S_1 and $P_2 + jQ_2$ for S_2 .

$$S_T = P_1 + jQ_1 + P_2 + jQ_2$$

Substitute 3 kW for P_1 , -2.6457 kVAR for Q_1 , 6 kW for P_2 and 1.9728 kVAR for Q_2 .

$$\begin{aligned}S_T &= 3 \text{ k} - j2.6457 \text{ k} + 6 \text{ k} + j1.9728 \text{ k} \\ &= 9 \text{ k} - j0.6729 \text{ k} \\ &= (9 - j0.6729) \text{ kVA}\end{aligned}$$

Therefore, the value of the total complex power absorbed by the two loads is,

$$(9 - j0.6729) \text{ kVA}.$$

The total power absorbed by the two loads is equal to the power supplied by the source. That is, $(9 - j0.6729) \text{ kVA}$.

The value of the total real power P_T and the total reactive power Q_T absorbed by the load is, 9 kW and 0.6729 kVAR respectively.

Step 8 of 9

Calculate the value of the apparent power absorbed by the two loads.

$$S_T = |S_T|$$

Substitute $(9 - j0.6729)$ kVA for S_T .

$$\begin{aligned} S_T &= |(9 - j0.6729) \text{ k}| \\ &= \sqrt{(9 \text{ k})^2 + (0.6729 \text{ k})^2} \\ &= \sqrt{81 + 0.4537} \text{ k} \\ &= \sqrt{81.4537} \text{ k} \end{aligned}$$

$$S_T = 9.025 \text{ kVA}$$

Therefore, the value of the apparent power S_T absorbed by the two loads is, **9.025 kVA**.

Step 9 of 9

Calculate the combined power factor pf_T of the two loads.

$$\text{pf}_T = \frac{P_T}{S_T}$$

Substitute **9 kW** for P_T and **9.025 kVA** for S_T .

$$\begin{aligned} \text{pf}_T &= \frac{9 \text{ k}}{9.025 \text{ k}} \\ &= 0.9972 \text{ leading} \end{aligned}$$

Power factor is leading since the value of the reactive power is negative.

Therefore, the value of the combined power factor pf_T is, **0.9972 leading**.