

Problem

Find the value of parallel capacitance needed to correct a load of 140 kVAR at 0.85 lagging pf to unity pf. Assume that the load is supplied by a 220-V (rms), 60-Hz line.

Step-by-step solution

Step 1 of 8

Calculate the value of the power factor angle of the load before the capacitor is connected across the load.

$$\begin{aligned}\theta_1 &= \cos^{-1}(0.85) \\ &= 31.788^\circ\end{aligned}$$

Therefore, the value of the power factor angle θ_1 is, 31.788° .

Step 2 of 8

Calculate the value of the apparent power S absorbed by the load before capacitor is connected across the load.

$$S_1 = \frac{Q_1}{\sin \theta_1}$$

Substitute 31.788° for θ_1 and 140 kVAR for Q_1 .

$$\begin{aligned}S_1 &= \frac{140 \text{ k}}{\sin 31.788^\circ} \\ &= \frac{140 \text{ k}}{0.5268} \\ &= 265.756 \text{ kVA}\end{aligned}$$

Therefore, the value of the apparent power S_1 is 265.756 kVA.

Step 3 of 8

Calculate the value of the real power P_1 .

$$P_1 = S_1 \cos \theta_1$$

Substitute 265.756 kVA for S_1 and 31.788° for θ_1 .

$$\begin{aligned}P_1 &= (265.756 \text{ k}) \cdot \cos(31.788^\circ) \\ &= (265.756 \text{ k}) \cdot (0.85) \\ &= 225.893 \text{ kW}\end{aligned}$$

Therefore, the value of the real power P_1 is 225.893 kW.

Step 4 of 8

Calculate the value of the power factor angle after the capacitor is connected across the load.

$$\begin{aligned}\theta_2 &= \cos^{-1}(1) \\ &= 0^\circ\end{aligned}$$

Therefore, the value of the power factor angle θ_2 is 0° .

Step 5 of 8

Calculate the value of the apparent power absorbed by the load after the capacitor is connected across the load.

$$S_2 = \frac{P_2}{\cos \theta_2}$$

Substitute 0° for θ_2 and 225.893 kW for P_2 since, no change is seen in the value of the real power.

$$\begin{aligned}S_2 &= \frac{225.893 \text{ k}}{\cos 0^\circ} \\ &= \frac{225.893 \text{ k}}{1} \\ &= 225.893 \text{ kVA}\end{aligned}$$

Therefore, the value of the apparent power S_2 is 225.893 kVA .

Step 6 of 8

Calculate the value of the reactive power Q_2 after the capacitor is connected across the load.

$$Q_2 = S_2 \sin \theta_2$$

Substitute 0° for θ_2 and 225.893 kVA for S_2 .

$$\begin{aligned}Q_2 &= (225.893 \text{ k}) \cdot \sin(0^\circ) \\ &= (225.893 \text{ k})(0) \\ &= 0 \text{ VAR}\end{aligned}$$

Therefore, the value of the reactive power Q_2 is 0 VAR .

Step 7 of 8

Calculate the value of the reactive power Q_c due to capacitor.

$$Q_c = Q_1 - Q_2$$

Substitute 0 VAR for Q_2 and 140 kVAR for Q_1 .

$$\begin{aligned}Q_c &= 140 \text{ k} - 0 \\ &= 140 \text{ kVAR}\end{aligned}$$

Therefore, the value of the reactive power due to capacitor Q_c is 140 kVAR .

Step 8 of 8

Calculate the value of the capacitance C

$$C = \frac{Q_c}{\omega V_{rms}^2}$$

Substitute $2\pi f$ for ω .

$$C = \frac{Q_c}{2\pi f V_{rms}^2}$$

Substitute 140 kVAR for Q_c , 60 Hz for f and 220 V for V_{rms} .

$$\begin{aligned} C &= \frac{140 \text{ k}}{2\pi(60)(220)^2} \\ &= \frac{140 \text{ k}}{2\pi(60)(48400)} \\ &= \frac{140 \text{ k}}{18246.37 \text{ k}} \\ &= 7.673 \text{ mF} \end{aligned}$$

Therefore, the value of the capacitor C is, 7.673 mF.