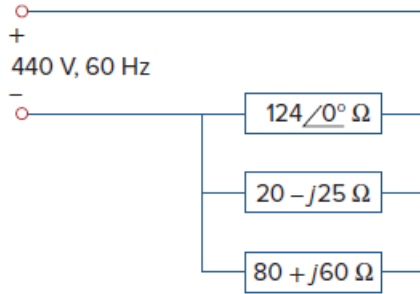


Problem

For the power system in Fig. 11.67, find: (a) the average power, (b) the reactive power, (c) the power factor. Note that 440 V is an rms value.

Figure 11.67:



Step-by-step solution

Step 1 of 5

Refer to Figure 11.67 in the text book.

Calculate the equivalent impedance Z_{eq} of the parallel connected impedance.

$$\begin{aligned} Z_{eq} &= 124\angle 0^\circ \parallel (20 - j25) \parallel (80 + j60) \\ &= \frac{(124)(20 - j25)(80 + j60)}{(124)(20 - j25) + (80 + j60)(124) + (20 - j25)(80 + j60)} \\ &= \frac{384400 - j99200}{2480 - j3100 + 3100 - j800 + 9920 + j7440} \\ &= \frac{384400 - j99200}{15500 + j3540} \end{aligned}$$

$$\begin{aligned} Z_{eq} &= 22.181 - j11.466 \\ &= 24.969\angle -27.336^\circ \Omega \end{aligned}$$

Therefore, the value of the equivalent impedance Z_{eq} is $24.969\angle -27.336^\circ \Omega$.

Step 2 of 5

Calculate the value of the current I_{rms} flowing in the circuit.

$$I_{rms} = \frac{440}{Z_{eq}}$$

Substitute $24.969\angle -27.336^\circ \Omega$ for Z_{eq} .

$$\begin{aligned} I_{rms} &= \frac{440}{24.969\angle -27.336^\circ} \\ &= 17.622\angle 27.336^\circ \text{ A rms} \end{aligned}$$

Therefore, the value of the current I_{rms} flowing in the circuit is $17.622\angle 27.336^\circ \text{ A rms}$.

Step 3 of 5

Calculate the value of the average power P .

$$P = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$

Substitute 17.622 A rms for I_{rms} , 440 V rms for V_{rms} , 0° for θ_v and 27.336° for θ_i .

$$\begin{aligned} P &= (440)(17.622) \cos(0 - 27.336) \\ &= (7753.68) \cos(-27.336) \\ &= (7753.68)(0.8883) \\ &= 6.89 \text{ kW} \end{aligned}$$

Therefore, the value of the average power P is, 6.89 kW.

Step 4 of 5

Calculate the value of the reactive power Q .

$$Q = V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)$$

Substitute 17.622 A rms for I_{rms} , 440 V rms for V_{rms} , 0° for θ_v and 27.336° for θ_i .

$$\begin{aligned} Q &= (440)(17.622) \sin(0 - 27.336) \\ &= (7753.68) \sin(-27.336) \\ &= (7753.68)(-0.4592) \\ &= -3.56 \text{ kVAR} \end{aligned}$$

Therefore, the value of the reactive power Q is, -3.56 kVAR.

Step 5 of 5

Calculate the value of the power factor pf.

$$\text{pf} = \cos(\theta_v - \theta_i)$$

Substitute 0° for θ_v and 27.336° for θ_i .

$$\begin{aligned} \text{pf} &= \cos(0 - 27.336) \\ &= \cos(-27.336) \\ &= 0.8883 \text{ leading} \end{aligned}$$

Power factor is leading since reactive power is negative.

Therefore, the value of the power factor pf is, 0.8883.