

Problem

For the following voltage and current phasors, calculate the complex power, apparent power, real power, and reactive power. Specify whether the pf is leading or lagging.

(a) $\mathbf{V} = 220\angle 30^\circ \text{ V rms}, \mathbf{I} = 0.5\angle 60^\circ \text{ A rms}$

(b) $\mathbf{V} = 250\angle -10^\circ \text{ V rms},$
 $\mathbf{I} = 6.2\angle -25^\circ \text{ A rms}$

(c) $\mathbf{V} = 120\angle 0^\circ \text{ V rms}, \mathbf{I} = 2.4\angle -15^\circ \text{ A rms}$

(d) $\mathbf{V} = 160\angle 45^\circ \text{ V rms}, \mathbf{I} = 8.5\angle 90^\circ \text{ A rms}$

Step-by-step solution

Step 1 of 14

(a)

Write the phasor values of voltage and current.

$$\begin{aligned}\mathbf{V} &= V_{\text{rms}} \angle \theta_v \\ &= 220\angle 30^\circ \text{ V rms}\end{aligned}$$

$$\begin{aligned}\mathbf{I} &= I_{\text{rms}} \angle \theta_i \\ &= 0.5\angle 60^\circ \text{ A rms}\end{aligned}$$

Determine the complex power.

$$\begin{aligned}\mathbf{S} &= \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* \\ &= (220\angle 30^\circ)(0.5\angle 60^\circ)^* \\ &= (220\angle 30^\circ)(0.5\angle -60^\circ) \\ &= 110\angle -30^\circ \text{ VA} \\ &= 95.26 - j55 \text{ VA}\end{aligned}$$

Therefore, the complex power is $\boxed{110\angle -30^\circ \text{ VA}}$.

Determine the apparent power.

$$\begin{aligned}S &= |\mathbf{S}| \\ &= |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| \\ &= (220)(0.5) \\ &= 110 \text{ VA}\end{aligned}$$

Therefore, the apparent power is $\boxed{110 \text{ VA}}$.

Step 2 of 14

Determine the real power.

$$\begin{aligned}P &= \operatorname{Re}(\mathbf{S}) \\&= S \cos(\theta_v - \theta_i) \\&= 110 \cos(30^\circ - 60^\circ) \\&= 95.26 \text{ W}\end{aligned}$$

Therefore, the real power is **95.26 W**.

Determine the reactive power.

$$\begin{aligned}Q &= \operatorname{Im}(\mathbf{S}) \\&= S \sin(\theta_v - \theta_i) \\&= 110 \sin(30^\circ - 60^\circ) \\&= -55 \text{ VAR}\end{aligned}$$

Therefore, the reactive power is **-55 VAR**.

Step 3 of 14

Determine the power factor.

$$\begin{aligned}\text{pf} &= \cos(\theta_v - \theta_i) \\&= \cos(30^\circ - 60^\circ) \\&= 0.866\end{aligned}$$

Since the reactive power is negative, the power factor is **0.866 leading**.

Step 4 of 14

(b)

Write the phasor values of voltage and current.

$$\begin{aligned}\mathbf{V} &= V_{\text{rms}} \angle \theta_v \\&= 250 \angle -10^\circ \text{ V rms} \\ \mathbf{I} &= I_{\text{rms}} \angle \theta_i \\&= 6.2 \angle -25^\circ \text{ A rms}\end{aligned}$$

Determine the complex power.

$$\begin{aligned}\mathbf{S} &= \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* \\&= (250 \angle -10^\circ)(6.2 \angle -25^\circ)^* \\&= (250 \angle -10^\circ)(6.2 \angle 25^\circ) \\&= 1550 \angle 15^\circ \text{ VA} \\&= 1497.18 + j401.17 \text{ VA}\end{aligned}$$

Therefore, the complex power is **1550∠15° VA**.

Determine the apparent power.

$$\begin{aligned}S &= |\mathbf{S}| \\&= |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| \\&= (250)(6.2) \\&= 1550 \text{ VA}\end{aligned}$$

Therefore, the apparent power is **1550 VA**.

Step 5 of 14

Determine the real power.

$$\begin{aligned}P &= \operatorname{Re}(\mathbf{S}) \\&= S \cos(\theta_v - \theta_i) \\&= 1550 \cos(-10^\circ + 25^\circ) \\&= 1497.18 \text{ W}\end{aligned}$$

Therefore, the real power is **1497.18 W**.

Step 6 of 14

Determine the reactive power.

$$\begin{aligned}Q &= \operatorname{Im}(\mathbf{S}) \\&= S \sin(\theta_v - \theta_i) \\&= 1550 \sin(-10^\circ + 25^\circ) \\&= 401.17 \text{ VAR}\end{aligned}$$

Therefore, the reactive power is **401.17 VAR**.

Step 7 of 14

Determine the power factor.

$$\begin{aligned}\text{pf} &= \cos(\theta_v - \theta_i) \\&= \cos(-10^\circ + 25^\circ) \\&= \cos(15^\circ) \\&= 0.966\end{aligned}$$

Since the reactive power is positive, the power factor is **0.966 lagging**.

Step 8 of 14

(c)

Write the phasor values of voltage and current.

$$\begin{aligned}\mathbf{V} &= V_{\text{rms}} \angle \theta_v \\ &= 120 \angle 0^\circ \text{ V rms}\end{aligned}$$

$$\begin{aligned}\mathbf{I} &= I_{\text{rms}} \angle \theta_i \\ &= 2.4 \angle -15^\circ \text{ A rms}\end{aligned}$$

Determine the complex power.

$$\begin{aligned}\mathbf{S} &= \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* \\ &= (120 \angle 0^\circ)(2.4 \angle -15^\circ)^* \\ &= (120 \angle 0^\circ)(2.4 \angle 15^\circ) \\ &= 288 \angle 15^\circ \text{ VA} \\ &= 278.19 + j74.54 \text{ VA}\end{aligned}$$

Therefore, the complex power is $288 \angle 15^\circ \text{ VA}$.

Determine the apparent power.

$$\begin{aligned}S &= |\mathbf{S}| \\ &= |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| \\ &= (120)(2.4) \\ &= 288 \text{ VA}\end{aligned}$$

Therefore, the apparent power is 288 VA .

Step 9 of 14

Determine the real power.

$$\begin{aligned}P &= \text{Re}(\mathbf{S}) \\ &= S \cos(\theta_v - \theta_i) \\ &= 288 \cos(0^\circ + 15^\circ) \\ &= 278.19 \text{ W}\end{aligned}$$

Therefore, the real power is 278.19 W .

Determine the reactive power.

$$\begin{aligned}Q &= \text{Im}(\mathbf{S}) \\ &= S \sin(\theta_v - \theta_i) \\ &= 288 \sin(0^\circ + 15^\circ) \\ &= 74.54 \text{ VAR}\end{aligned}$$

Therefore, the reactive power is 74.54 VAR .

Step 10 of 14

Determine the power factor.

$$\begin{aligned}\text{pf} &= \cos(\theta_v - \theta_i) \\ &= \cos(0^\circ + 15^\circ) \\ &= \cos(15^\circ) \\ &= 0.966\end{aligned}$$

Since the reactive power is positive, the power factor is **0.966 lagging**.

Step 11 of 14

(d)

Write the phasor values of voltage and current.

$$\begin{aligned}\mathbf{V} &= V_{\text{rms}} \angle \theta_v \\ &= 160 \angle 45^\circ \text{ V rms}\end{aligned}$$

$$\begin{aligned}\mathbf{I} &= I_{\text{rms}} \angle \theta_i \\ &= 8.5 \angle 90^\circ \text{ A rms}\end{aligned}$$

Determine the complex power.

$$\begin{aligned}\mathbf{S} &= \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* \\ &= (160 \angle 45^\circ)(8.5 \angle 90^\circ)^* \\ &= (160 \angle 45^\circ)(8.5 \angle -90^\circ) \\ &= 1360 \angle -45^\circ \text{ VA} \\ &= 961.66 - j961.66 \text{ VA}\end{aligned}$$

Therefore, the complex power is $\boxed{1360 \angle -45^\circ \text{ VA}}$.

Step 12 of 14

Determine the apparent power.

$$\begin{aligned}S &= |\mathbf{S}| \\ &= |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| \\ &= (160)(8.5) \\ &= 1360 \text{ VA}\end{aligned}$$

Therefore, the apparent power is $\boxed{1360 \text{ VA}}$.

Step 13 of 14

Determine the real power.

$$\begin{aligned}P &= \text{Re}(\mathbf{S}) \\ &= S \cos(\theta_v - \theta_i) \\ &= 1360 \cos(45^\circ - 90^\circ) \\ &= 961.66 \text{ W}\end{aligned}$$

Therefore, the real power is $\boxed{961.66 \text{ W}}$.

Determine the reactive power.

$$\begin{aligned}Q &= \text{Im}(\mathbf{S}) \\ &= S \sin(\theta_v - \theta_i) \\ &= 1360 \sin(45^\circ - 90^\circ) \\ &= -961.66 \text{ VAR}\end{aligned}$$

Therefore, the reactive power is $\boxed{-961.66 \text{ VAR}}$.

Step 14 of 14

Determine the power factor.

$$\begin{aligned}\text{pf} &= \cos(\theta_v - \theta_i) \\ &= \cos(45^\circ - 90^\circ) \\ &= 0.707\end{aligned}$$

Since the reactive power is negative, the power factor is **0.707 leading**.